

**Lecture 20 –
 Introduction to Synchronous Digital Systems**

2004-10-15




Lecturer PSOE Dan Garcia
www.cs.berkeley.edu/~ddgarcia

Great new PC HW! →
 OQO model 01 is the
 new, lightest, coolest fully-
 functional PC on the block. 1GHz,
 20GB drive, 256MB RAM, wireless,
 color display, thumb keyboard
 which slides out. Small & light!



What are “Machine Structures”?

 

Coordination of many *levels of abstraction*

We'll investigate lower abstraction layers!
 (contract between HW & SW)



Below the Program

• High-level language program (in C)

```
swap int v[], int k){
    int temp;
    temp = v[k];
    v[k] = v[k+1];
    v[k+1] = temp;
}
```

C compiler

• Assembly language program (for MIPS)

```
swap: sll $2, $5, 2
      add $2, $4, $2
      lw $15, 0($2)
      lw $16, 4($2)
      sw $16, 0($2)
      sw $15, 4($2)
      jr $31
```

assembler

• Machine (object) code (for MIPS)

```
000000 000000 00101 000100000100000000
000000 00100 00010 0001000000100000 . . .
```



Logic Design

• Next 2 weeks: we'll study how a modern processor is built starting with basic logic elements as building blocks.

• Why study logic design?

- Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
- Background for more detailed hardware courses (CS 150, CS 152)



Logic Gates

• Basic building blocks are logic *gates*.


- In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
- Can build gates with transistors and resistors

• Then found theoretical basis for design


- Can represent and reason about gates with truth tables and Boolean algebra
- Assume know truth tables and Boolean algebra from a math or circuits course.
- Section B.2 in the textbook has a review




Physical Hardware

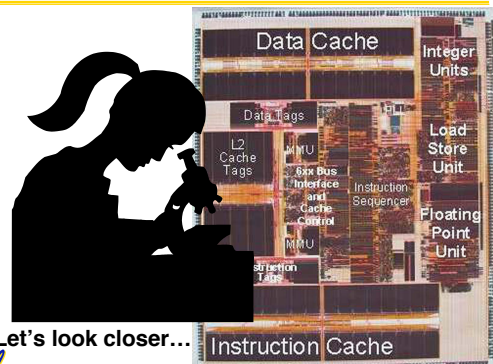


Gate-level view vs. Block diagram

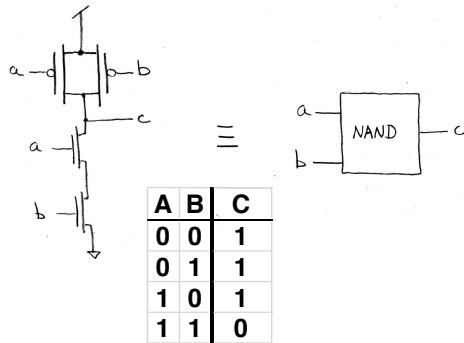


Signals and Waveforms: Clocks

 



Signals and Waveforms: Adders

 

Signals and Waveforms: Grouping

 

Signals and Waveforms: Circuit Delay

  


Combinational Logic

- Complex logic blocks are built from basic AND, OR, NOT building blocks we'll see shortly.
- A **combinational** logic block is one in which the output is a function only of its current input.
- Combinational logic **cannot have memory** (e.g., a register is not a combinational unit).



Circuits with STATE (e.g., register)

 

Administrivia

- Midterm coming up on Monday @ 7pm in 1 Pimintel. Heard this enough yet?



Peer Instruction

- A. SW can peek at HW (past ISA abstraction boundary) for optimizations
- B. SW can depend on particular HW implementation of ISA
- C. Timing diagrams serve as a critical debugging tool in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	FTT
8:	TTT



And in conclusion...

- ISA is very important abstraction layer
 - Contract between HW and SW
- Basic building blocks are logic gates
- Clocks control pulse of our circuits
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types
 - Stateless Combinational Logic (&,!,~)
 - State circuits (e.g., registers)

