

inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**

## Lecture 20 – Introduction to Synchronous Digital Systems




**2004-10-15**

**Lecturer PSOE Dan Garcia**

[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)

**Great new PC HW! ⇒**

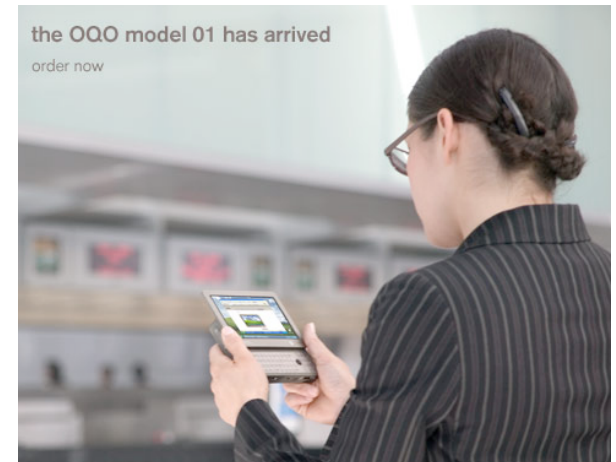**OQO model 01 is the new, lightest, coolest fully-functional PC on the block. 1GHz, 20GB drive, 256MB RAM, wireless, color display, thumb keyboard which slides out. Small & light!**




the OQO model 01 has arrived  
order now

[oqo.com](http://oqo.com)



# What are “Machine Structures”?

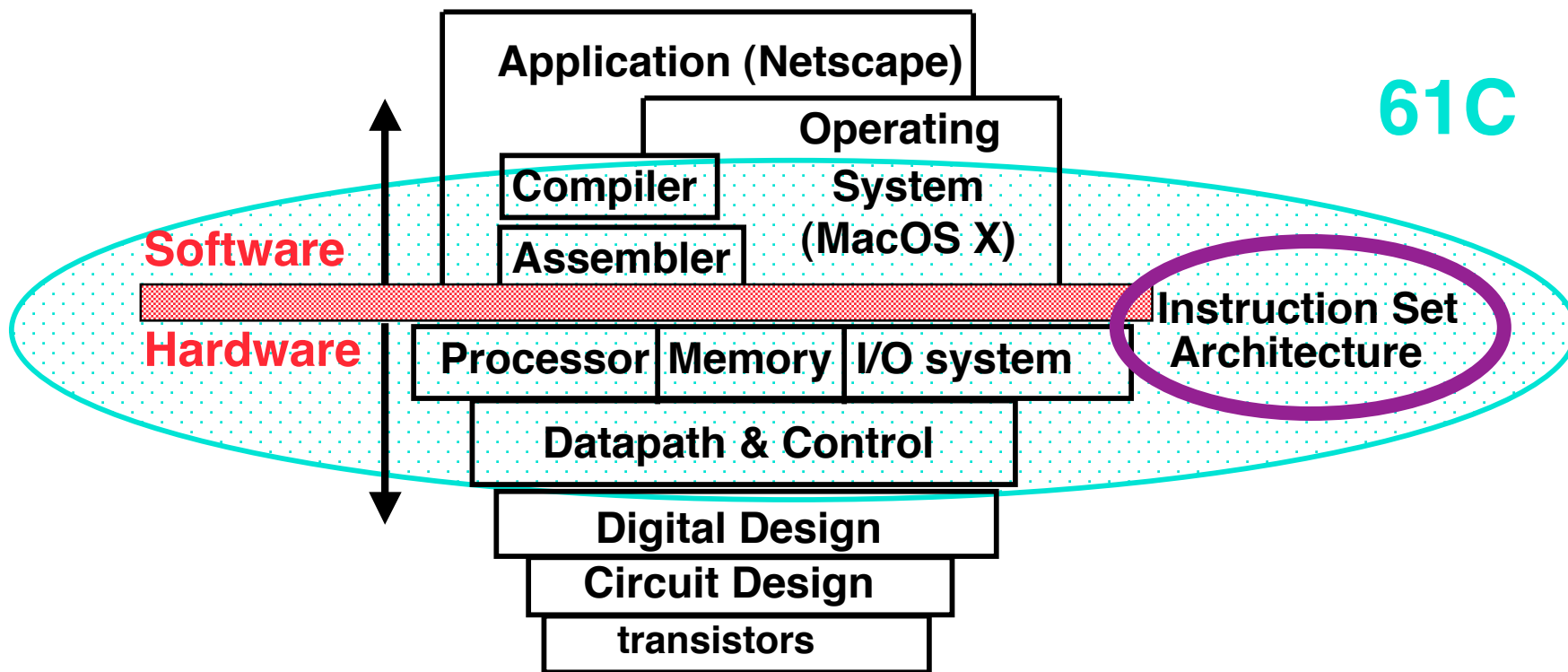

Coordination of many *levels of abstraction*


We'll investigate lower abstraction layers!  
(contract between HW & SW)


 
# Below the Program


- High-level language program (in C)

```
swap int v[], int k){  
    int temp;  
    temp = v[k];  
    v[k] = v[k+1];  
    v[k+1] = temp;  
}
```




- Assembly language program (for MIPS)
 
```
swap: sll    $2, $5, 2  
      add    $2, $4, $2  
      lw     $15, 0($2)  
      lw     $16, 4($2)  
      sw     $16, 0($2)  
      sw     $15, 4($2)  
      jr     $31
```



- Machine (object) code (for MIPS)
 
```
000000 00000 00101 00010000010000000  
000000 00100 00010 00010000000100000 . . .
```



# Logic Design

---

- **Next 2 weeks: we'll study how a modern processor is built starting with basic logic elements as building blocks.**
- **Why study logic design?**
  - **Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)**
  - **Background for more detailed hardware courses (CS 150, CS 152)**




# Logic Gates

---

- **Basic building blocks are logic *gates*.**
  - In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
  - Can build gates with transistors and resistors
- **Then found theoretical basis for design**
  - Can represent and reason about gates with truth tables and Boolean algebra
  - Assume know truth tables and Boolean algebra from a math or circuits course.
  - Section B.2 in the textbook has a review




# Physical Hardware

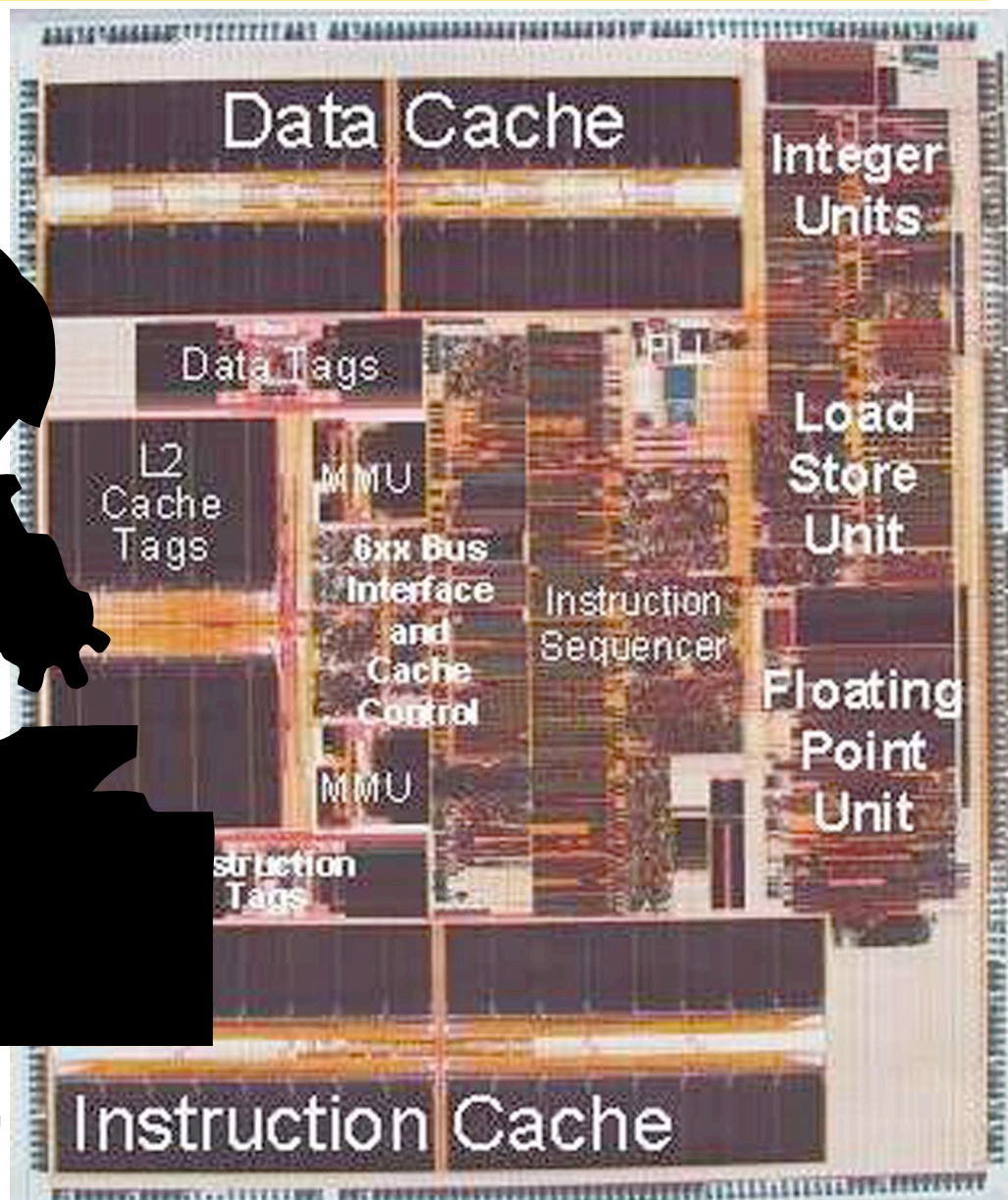


Let's look closer...



# Gate-level view vs. Block diagram

 


≡

 

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0



# Signals and Waveforms: Clocks

---

 




# Signals and Waveforms: Adders

 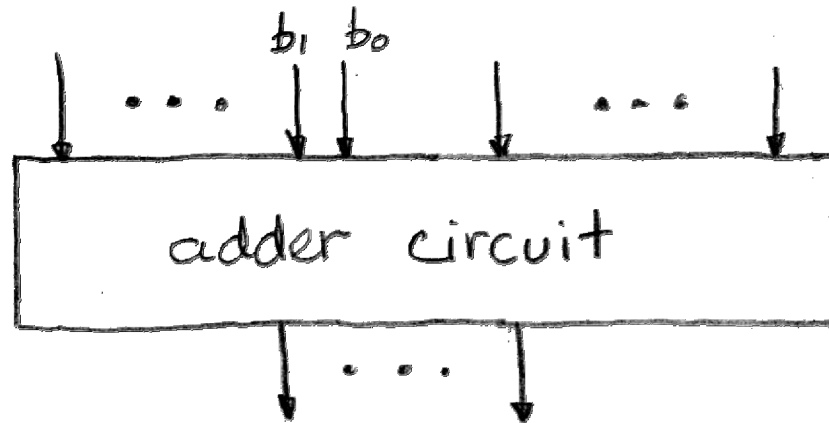

# Signals and Waveforms: Grouping

$x_3$   $x_2$   $x_1$   $x_0$   
↓ ↓ ↓ ↓


 


# Signals and Waveforms: Circuit Delay



$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

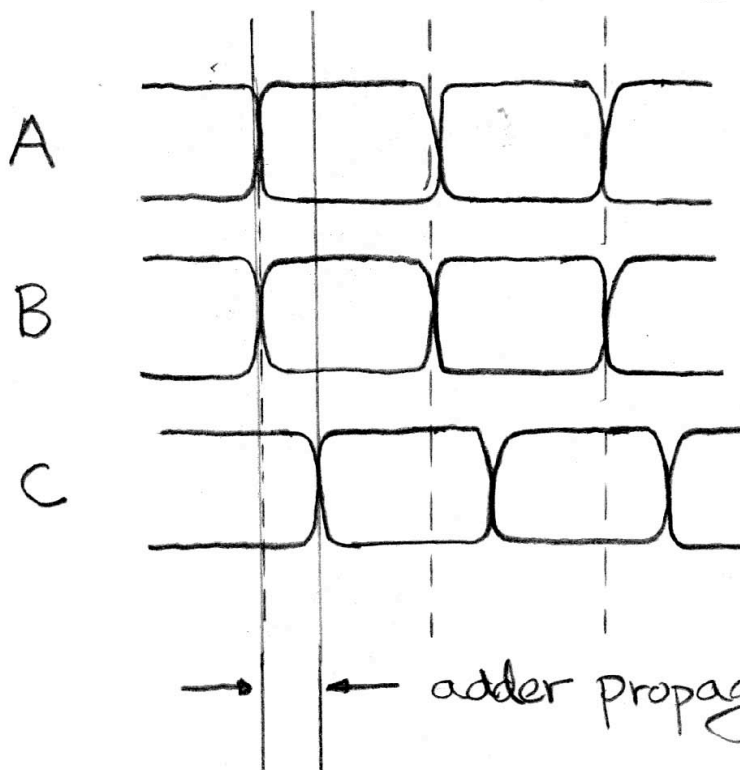 

→ ← adder propagation delay



# Combinational Logic


---

- Complex logic blocks are built from basic AND, OR, NOT building blocks we'll see shortly.
- A *combinational* logic block is one in which the output is a function only of its current input.
- Combinational logic **cannot have memory** (e.g., a register is not a combinational unit).



# Circuits with STATE (e.g., register)

---

 

# Administrivia

---

- **Midterm coming up on Monday @ 7pm in 1 Pimintel. Heard this enough yet?**



# Peer Instruction

---

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	<b>FFF</b>
2:	<b>FFT</b>
3:	<b>FTF</b>
4:	<b>FTT</b>
5:	<b>TFF</b>
6:	<b>TFT</b>
7:	<b>TF</b>
8:	<b>TTT</b>



## And in conclusion...

---

- **ISA is very important abstraction layer**
  - **Contract between HW and SW**
- **Basic building blocks are logic *gates***
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types**
  - **Stateless Combinational Logic (&,!,~)**
  - **State circuits (e.g., registers)**

