

**Lecture 21 –  
 State Elements: Circuits That Remember**

2004-10-18



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

**We whomp UCLA!** →

After outplaying the #1-ranked team, we come back at our homecoming game and beat UCLA (ex-powerhouse) 45-28. Arrington rushes for 205 yards. 550 yards total! At AZ next week. We're ranked 7<sup>th</sup>!



CS 61C L21 State Elements: CircuitsThat Remember (1)

calbears.com Garcia, Fall 2004 © UCB

**Review...**


- ISA is very important abstraction layer
  - Contract between HW and SW
- Basic building blocks are logic *gates*
- Clocks control pulse of our circuits
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types
  - Stateless Combinational Logic (&,!,~), in which **output is function of input only**
  - State circuits (e.g., registers)



CS 61C L21 State Elements: CircuitsThat Remember (2)

Garcia, Fall 2004 © UCB

**Accumulator Example**

 


**Want:**  $S=0$ ; for  $i$  from 0 to  $n-1$   
 $S = S + X_i$



CS 61C L21 State Elements: CircuitsThat Remember (3)

Garcia, Fall 2004 © UCB

**First try...Does this work?**

 

**Nope!**


- Reason #1... What is there to control the next iteration of the 'for' loop?
- Reason #2... How do we say: 's=0'?




CS 61C L21 State Elements: CircuitsThat Remember (4)

Garcia, Fall 2004 © UCB

**Second try...How about this? Yep!**

 


**Rough timing...**

 

CS 61C L21 State Elements: CircuitsThat Remember (5)

Garcia, Fall 2004 © UCB

 **Register Details...What's in it anyway?**




- $n$  instances of a **"Flip-Flop"**, called that because the output flips and flops betw. 0,1
- D is "data"
- Q is "output"
- Also called "d-q Flip-Flop", "d-type Flip-Flop"



CS 61C L21 State Elements: CircuitsThat Remember (6)

Garcia, Fall 2004 © UCB
 
### What's the timing of a Flip-flop? (1/2)




- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."



CS 61C L21 State Elements: CircuitsThat Remember (7)

Garcia, Fall 2004 © UCB
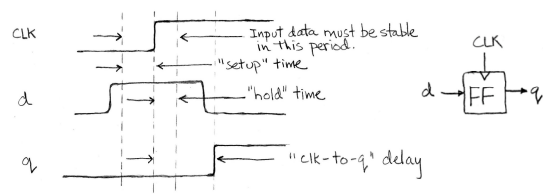
### What's the timing of a Flip-flop? (2/2)




- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."



CS 61C L21 State Elements: CircuitsThat Remember (8)

Garcia, Fall 2004 © UCB

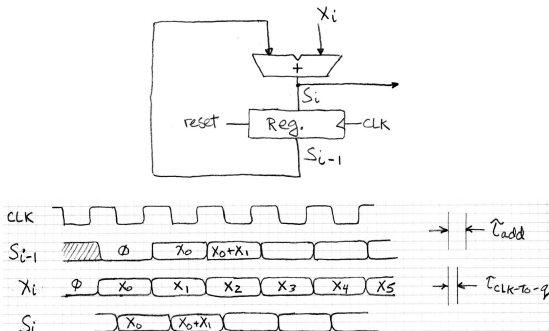
### Accumulator Revisited (proper timing 1/2)



CS 61C L21 State Elements: CircuitsThat Remember (10)

Garcia, Fall 2004 © UCB

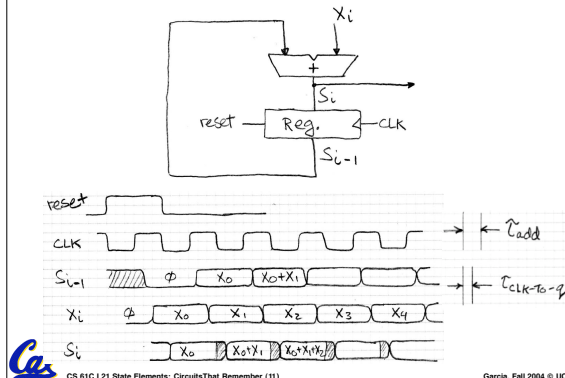
### Accumulator Revisited (proper timing 2/2)



CS 61C L21 State Elements: CircuitsThat Remember (11)

Garcia, Fall 2004 © UCB

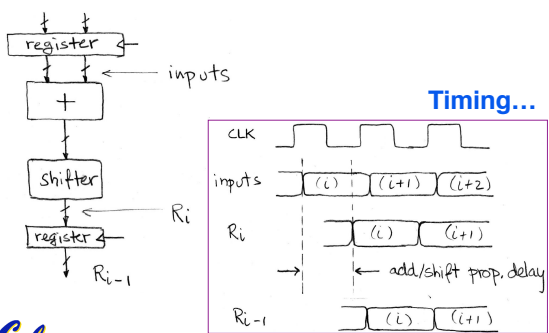
### Pipelining to improve performance (1/2)



CS 61C L21 State Elements: CircuitsThat Remember (12)

Garcia, Fall 2004 © UCB

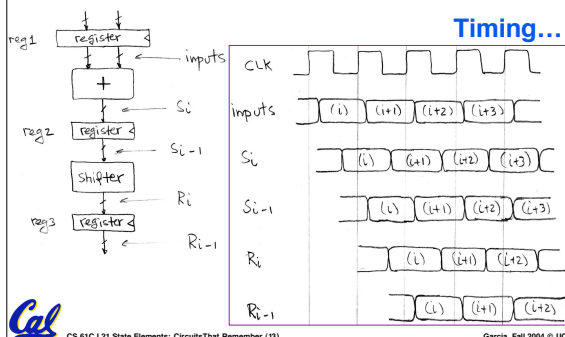
### Pipelining to improve performance (2/2)



CS 61C L21 State Elements: CircuitsThat Remember (13)

Garcia, Fall 2004 © UCB


## Finite State Machines Introduction

 


CS 61C L21 State Elements: CircuitsThat Remember (14)

Garcia, Fall 2004 © UCB
 
## Finite State Machine Example: 3 ones...



Draw the FSM...

 

Truth table...


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1



CS 61C L21 State Elements: CircuitsThat Remember (15)

Garcia, Fall 2004 © UCB


## Hardware Implementation of FSM

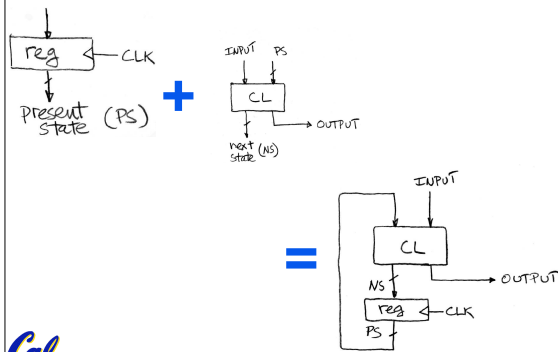

CS 61C L21 State Elements: CircuitsThat Remember (16)

Garcia, Fall 2004 © UCB

## General Model for Synchronous Systems

 

CS 61C L21 State Elements: CircuitsThat Remember (17)

Garcia, Fall 2004 © UCB

## Peer Instruction

- HW feedback akin to SW recursion
- We can implement a D-Q flipflop as simple CL (And, Or, Not gates)
- You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TFE
8:	TTT



CS 61C L21 State Elements: CircuitsThat Remember (18)

Garcia, Fall 2004 © UCB

## "And In conclusion..."

- We use **feedback** to maintain state
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
  - Setup and Hold times important
- We pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
  - You'll see them in HW classes (150,152) & 164



CS 61C L21 State Elements: CircuitsThat Remember (20)

Garcia, Fall 2004 © UCB