

**Lecture 21 –
State Elements: Circuits That Remember**




2004-10-18

Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

We whomp UCLA! ⇒

 **After outplaying the
#1-ranked team, we come back at our
homecoming game and beat UCLA
(ex-powerhouse) 45-28. Arrington
rushes for 205 yards. 550 yards total!**



At AZ next week. We're ranked 7th!

calbears.com


Garcia, Fall 2004 © UCB

Review...

- **ISA is very important abstraction layer**
 - **Contract between HW and SW**
- **Basic building blocks are logic *gates***
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types**
 - **Stateless Combinational Logic (&,!,~), in which *output is function of input only***
 - **State circuits (e.g., registers)**




Accumulator Example

 

Want: $S=0$; for i from 0 to $n-1$
 $S = S + X_i$

First try...Does this work?

 


Nope!

Reason #1... What is there to control the next iteration of the 'for' loop?


Reason #2... How do we say: 's=0'?




Second try...How about this? Yep!

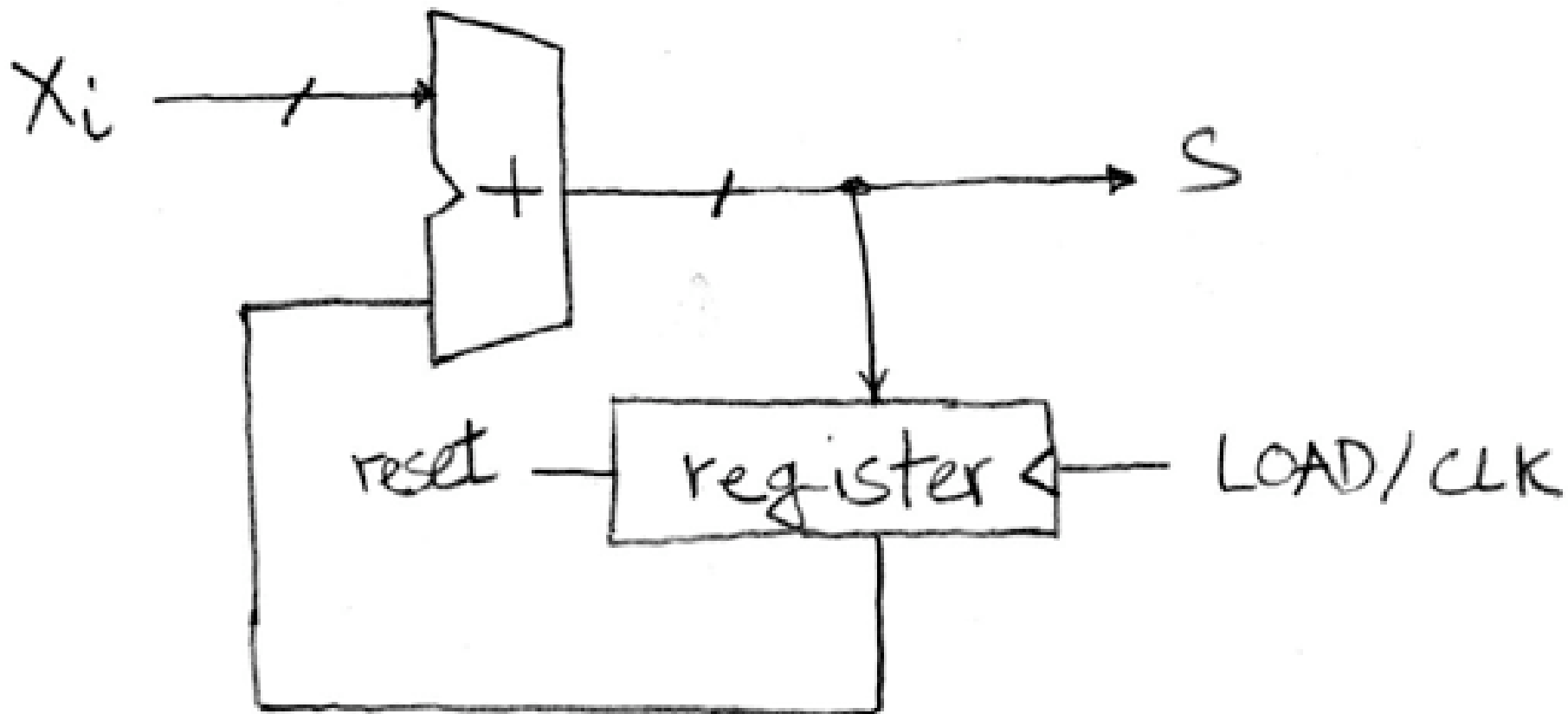

Rough timing...

 


Register Details...What's in it anyway?

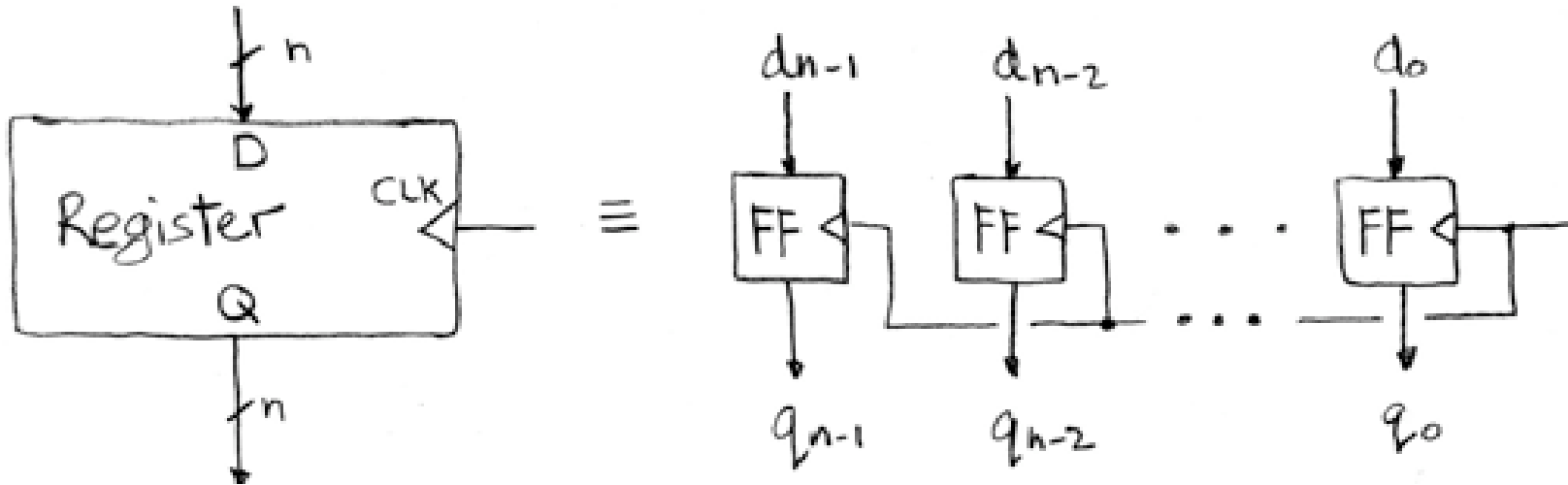

- n instances of a “Flip-Flop”, called that because the output flips and flops betw. 0,1
- D is “data”
- Q is “output”
- Also called “d-q Flip-Flop”, “d-type Flip-Flop”




What's the timing of a Flip-flop? (1/2)

 


- **Edge-triggered d-type flip-flop**

- This one is “positive edge-triggered”

 

- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”

What's the timing of a Flip-flop? (2/2)

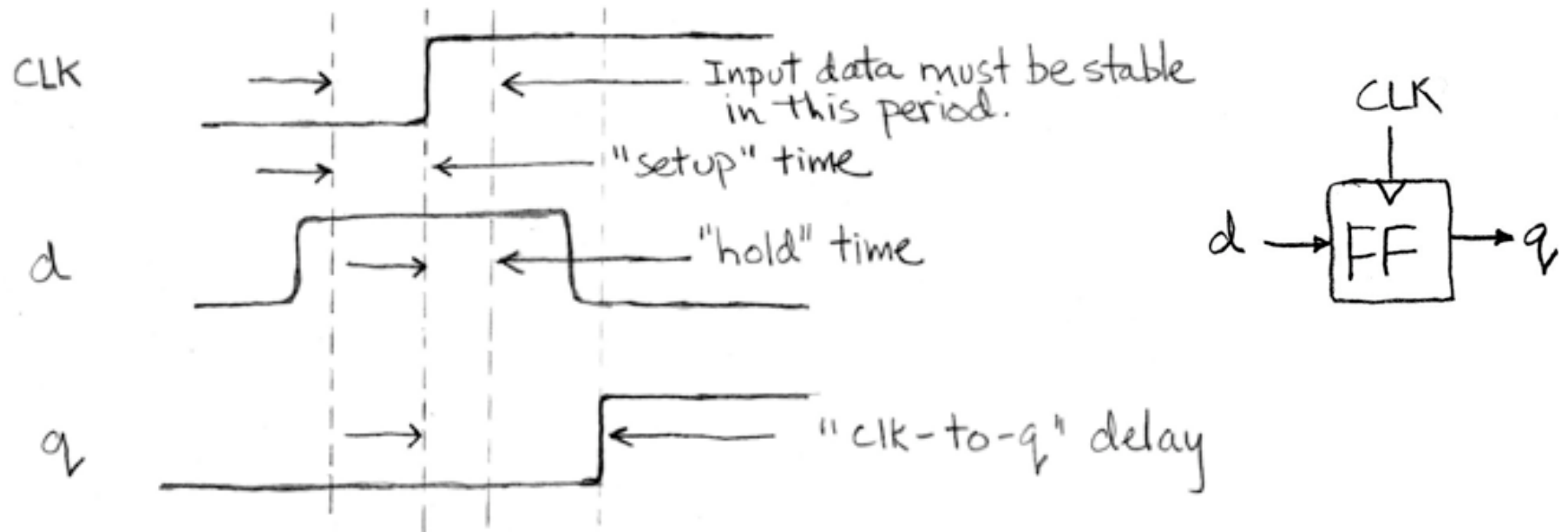

- **Edge-triggered d-type flip-flop**

- This one is "positive edge-triggered"





- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."

Administrivia



- **Midterm tonight!**
 - **1 Pimintel 7pm-10pm**



  
Accumulator Revisited (proper timing 1/2)



  
Accumulator Revisited (proper timing 2/2)



Pipelining to improve performance (1/2)


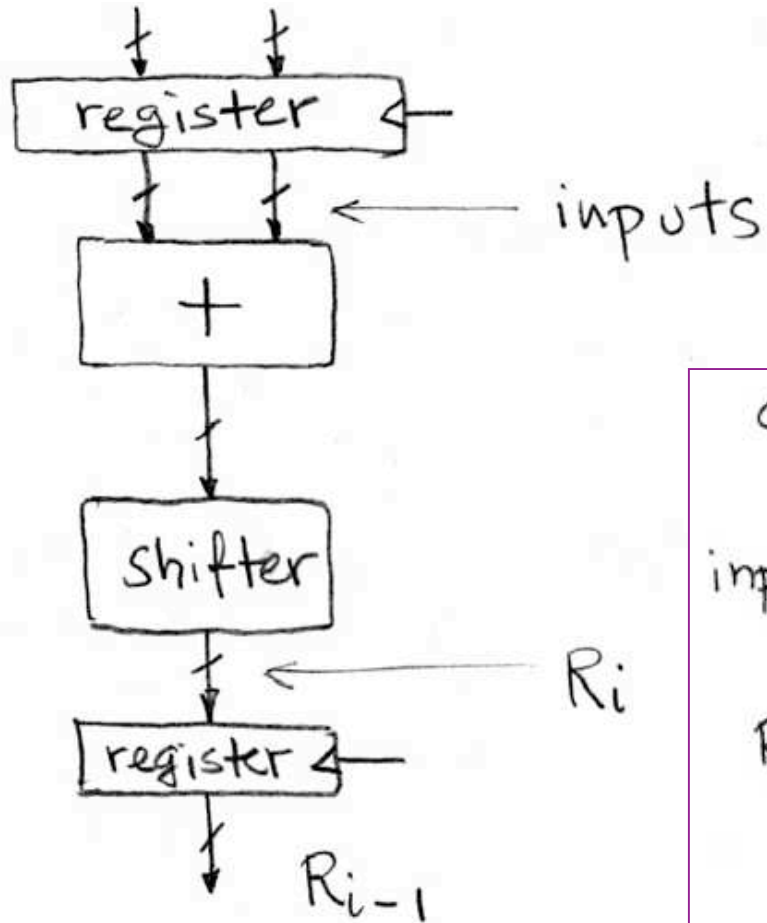


Timing...

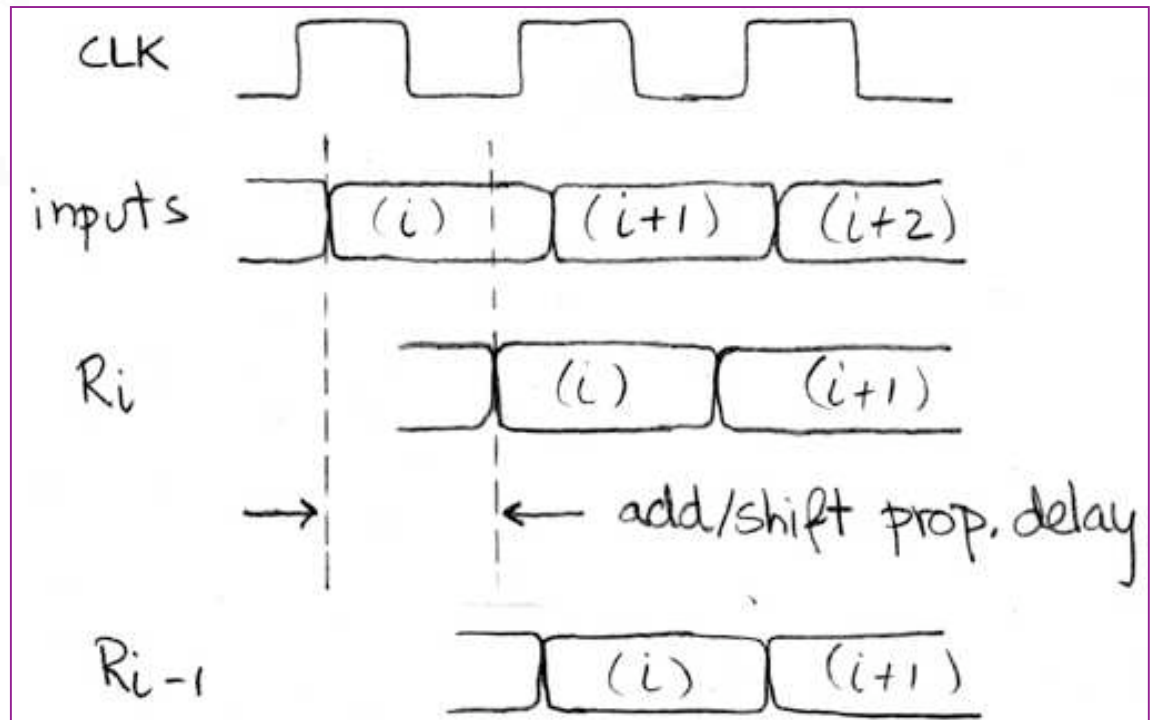


Pipelining to improve performance (2/2)


Timing...

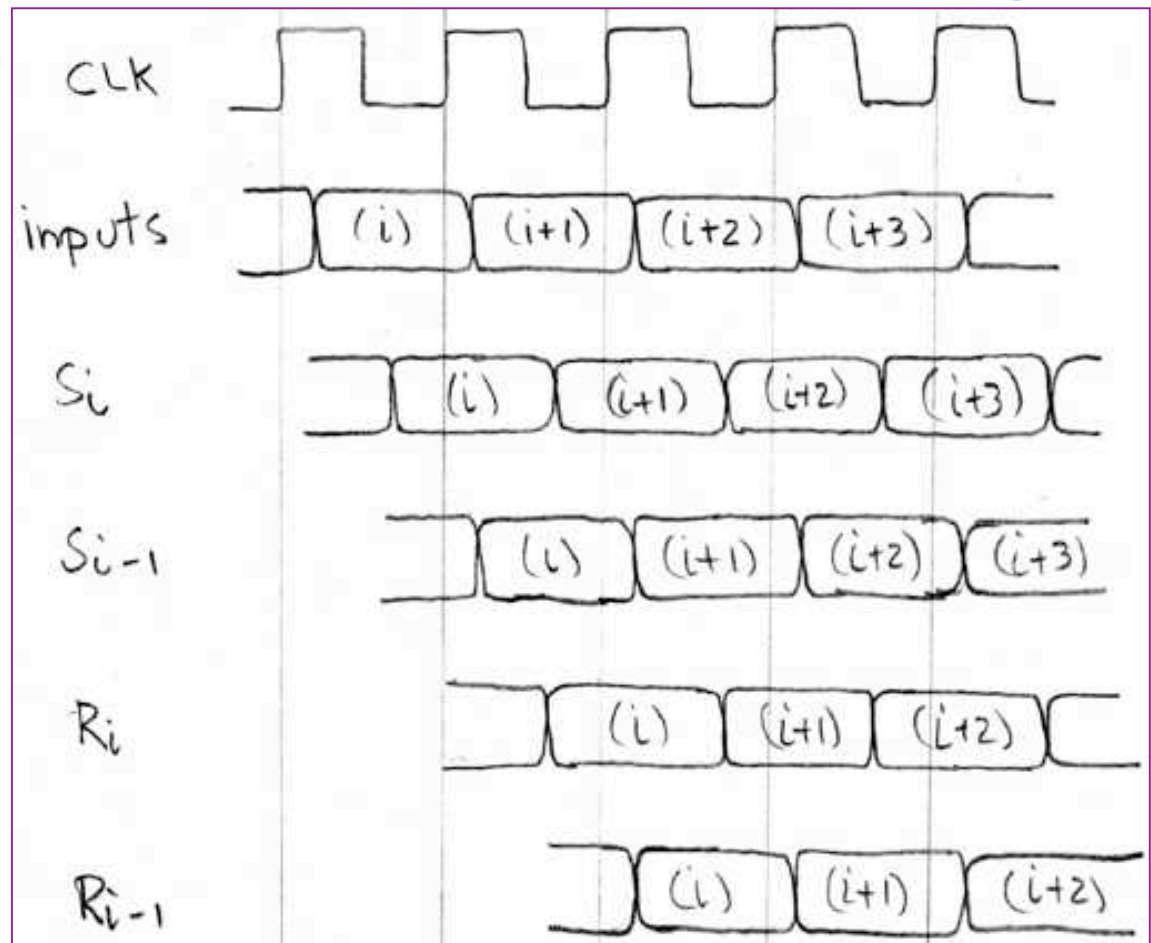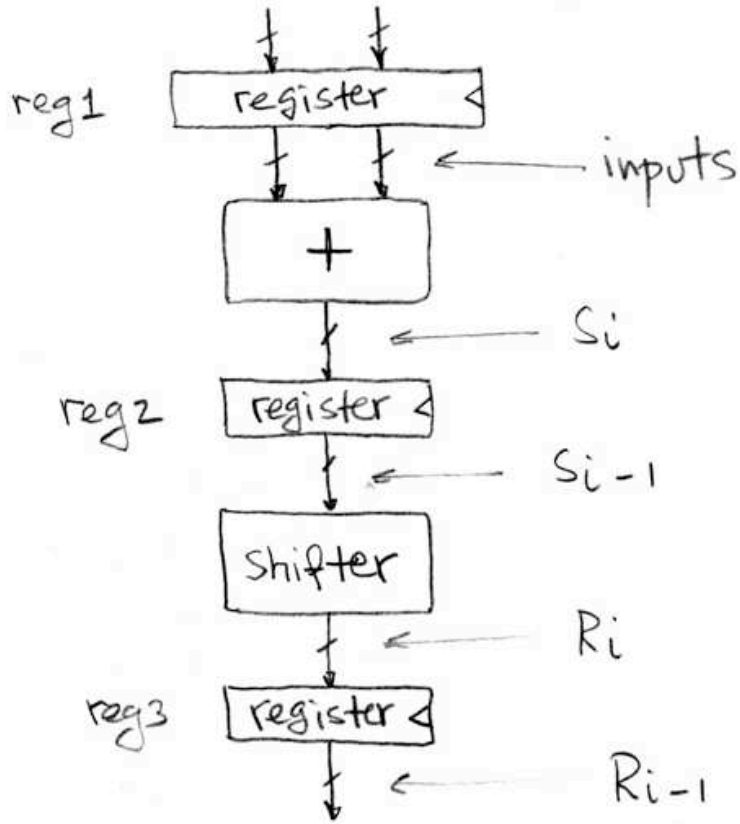


Finite State Machines Introduction

 

Finite State Machine Example: 3 ones...

 

Draw the FSM...

 


Truth table...


| PS | Input | NS | Output |
|----|-------|----|--------|
| 00 | 0 | 00 | 0 |
| 00 | 1 | 01 | 0 |
| 01 | 0 | 00 | 0 |
| 01 | 1 | 10 | 0 |
| 10 | 0 | 00 | 0 |
| 10 | 1 | 00 | 1 |



Hardware Implementation of FSM

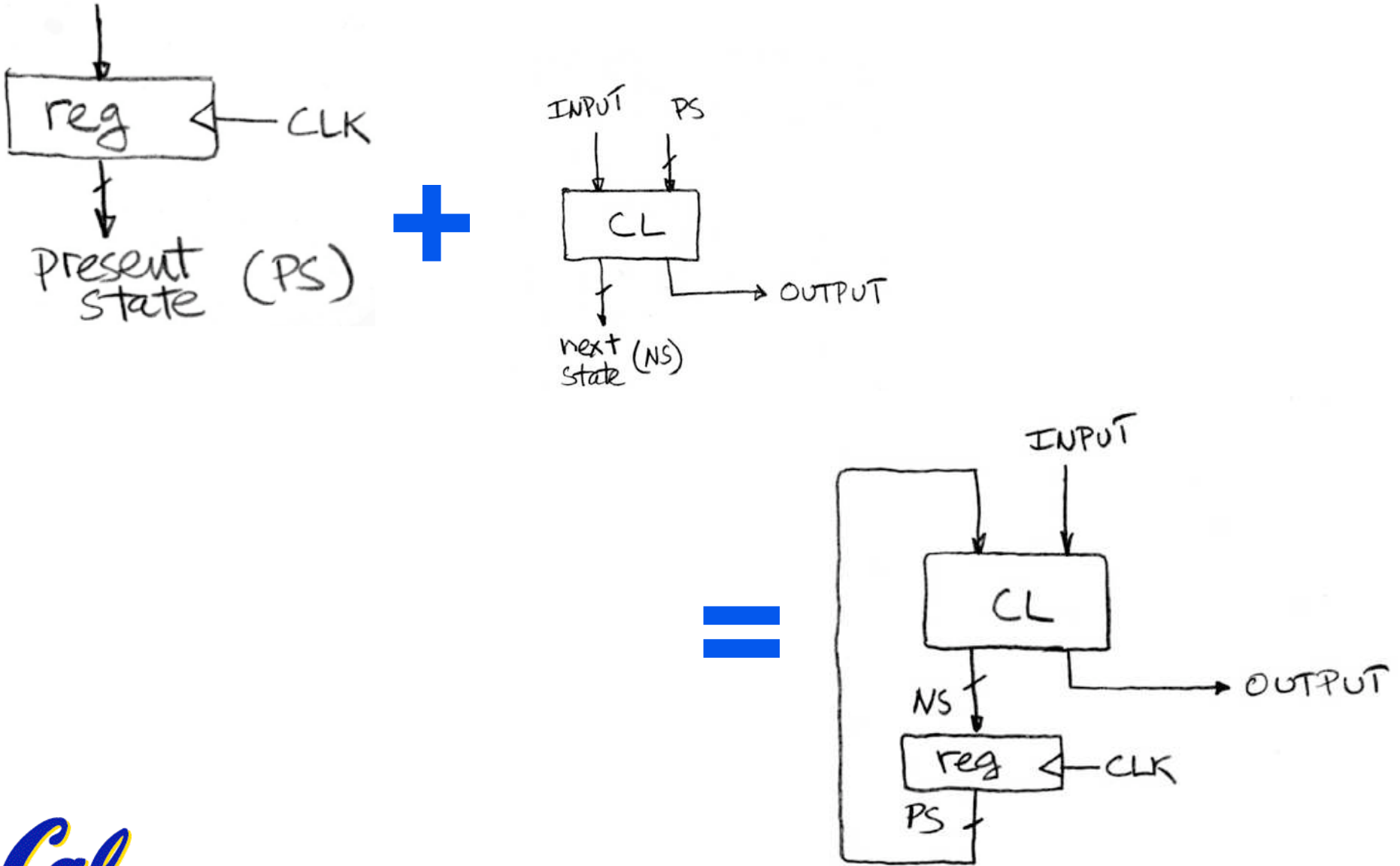

General Model for Synchronous Systems

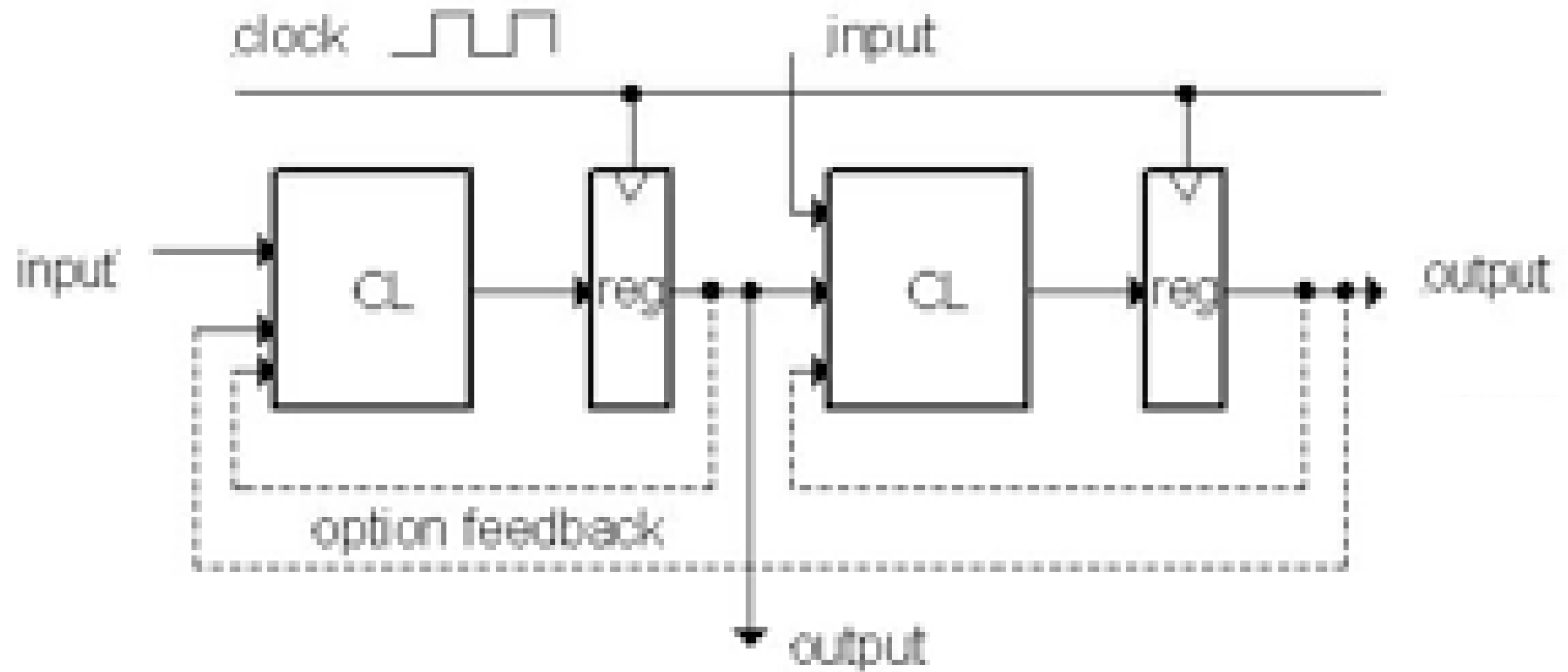

Peer Instruction

- A. HW feedback akin to SW recursion**
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

| | ABC |
|----|------------|
| 1: | FFF |
| 2: | FFT |
| 3: | FTF |
| 4: | FTT |
| 5: | TFF |
| 6: | TFT |
| 7: | TF |
| 8: | TTT |

Peer Instruction Answer



“And In conclusion...”

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
 - Setup and Hold times important
- We pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
 - You’ll see them in HW classes (150,152) & 164

