

inst.eecs.berkeley.edu/~cs61c
CS61C : Machine Structures

**Lecture 22 –
Representations of Combinatorial Logic Circuits**



2004-10-20

Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

E-voting talk today ⇒

**At 4pm in 306 Soda SU Prof.
David Dill will give a talk about
important issues in electronic voting.
This affects us all! Get there early...**



**www.verifiedvoting.org
votingintegrity.com**

Review...

- **We use feedback to maintain state**
- **Register files used to build memories**
- **D-FlipFlops used for Register files**
- **Clocks usually tied to D-FlipFlop load**
 - **Setup and Hold times important**
- **Pipeline big-delay CL for faster clock**
- **Finite State Machines extremely useful**
 - **You'll see them again in 150, 152 & 164**




Representations of CL Circuits...

- **Truth Tables**
- **Logic Gates**
- **Boolean Algebra**



Truth Tables

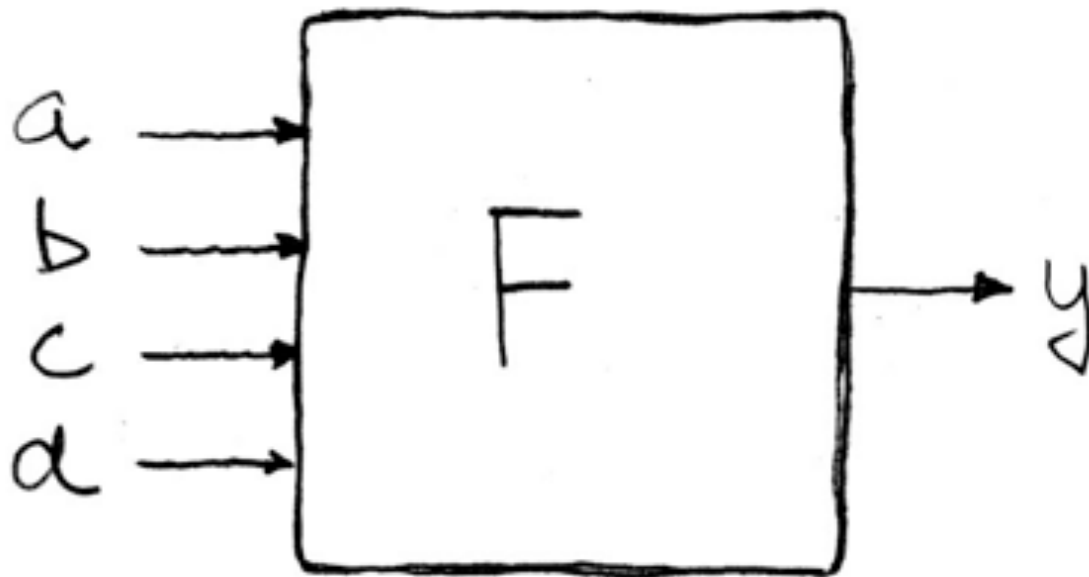


a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

TT Example #1: 1 iff one (not both) $a, b=1$

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



TT Example #2: 2-bit adder

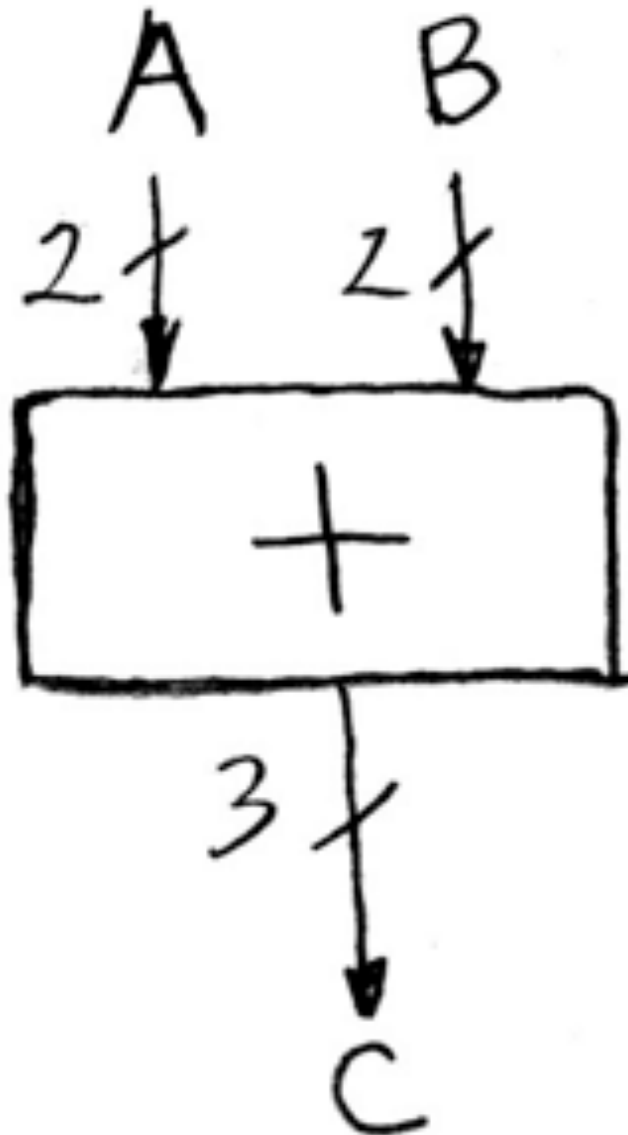

A	B	C
a_1a_0	b_1b_0	$c_2c_1c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How
Many
Rows?



TT Example #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

**How
Many
Rows?**




TT Example #3: 3-input majority circuit


a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1




Logic Gates (1/2)

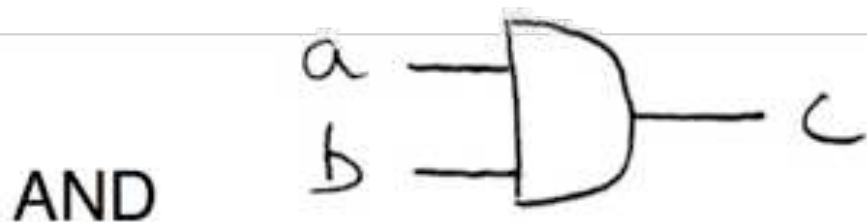

ab	c
00	0
01	0
10	0
11	1

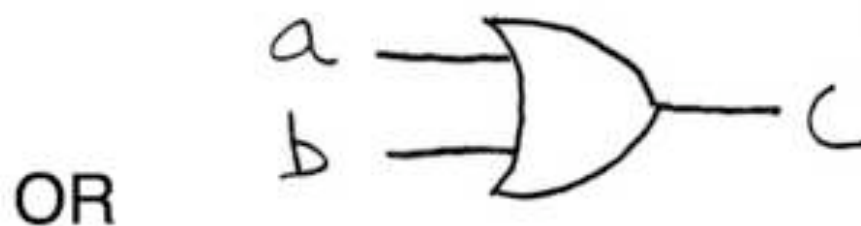

ab	c
00	0
01	1
10	1
11	1

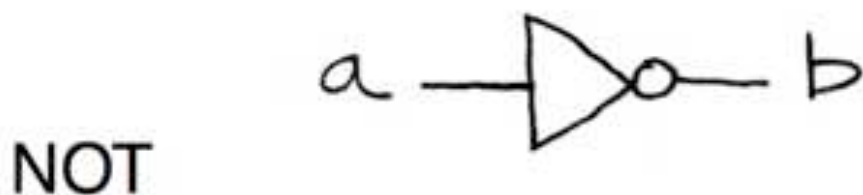


a	b
0	1
1	0

And vs. Or review – Dan’s mnemonic

AND Gate


Symbol

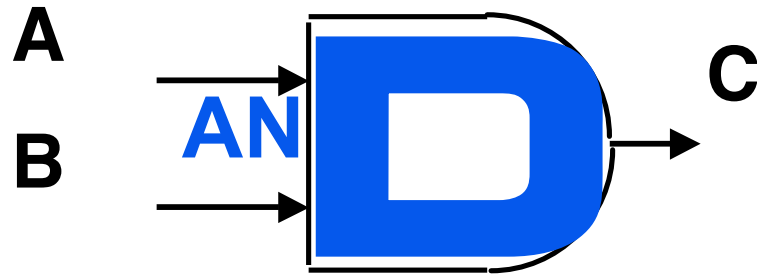


Definition

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


Logic Gates (2/2)

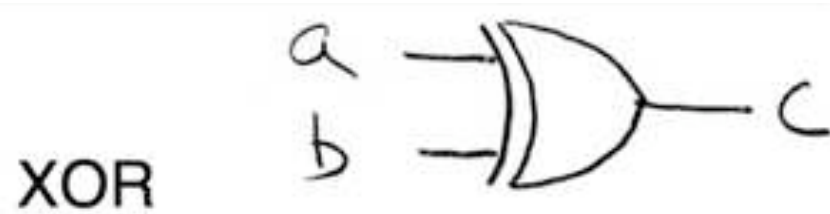

ab	c
00	0
01	1
10	1
11	0

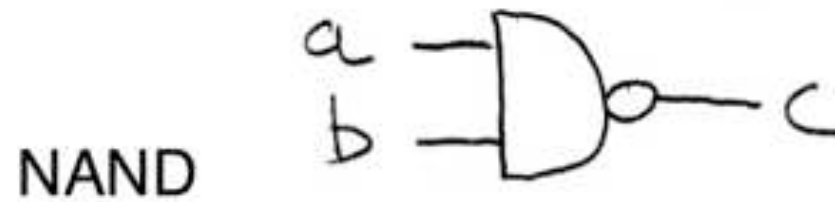

ab	c
00	1
01	1
10	1
11	0

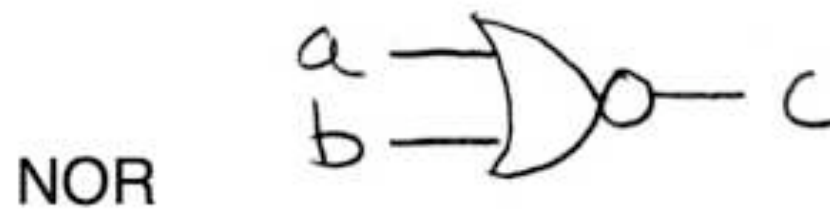

ab	c
00	1
01	0
10	0
11	0



2-input gates extend to n-inputs


- **N-input XOR is the only one which isn't so obvious**
- **It's simple: XOR is a 1 iff the # of 1s at its input is odd \Rightarrow**

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




Truth Table \Rightarrow Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

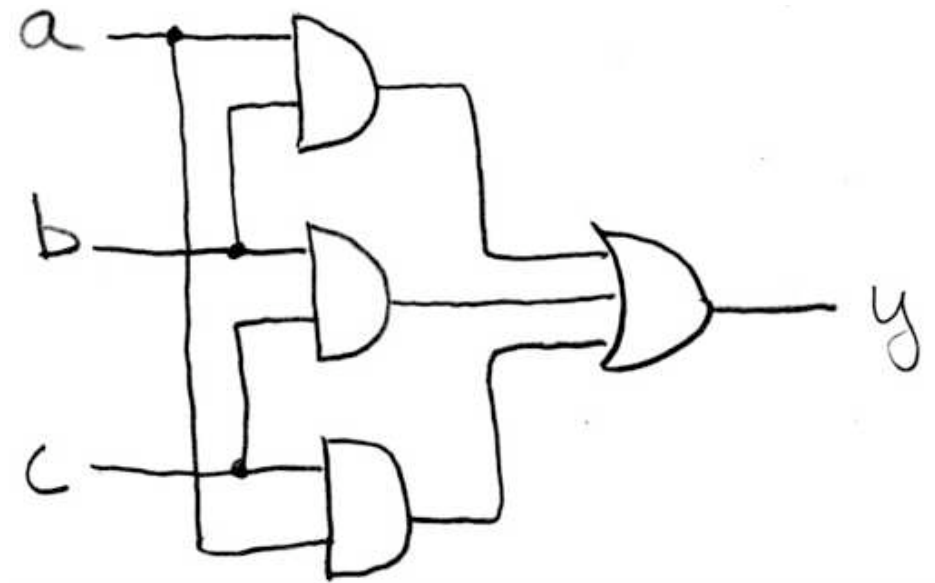


Truth Table \Rightarrow Gates (e.g., FSM circ.)


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

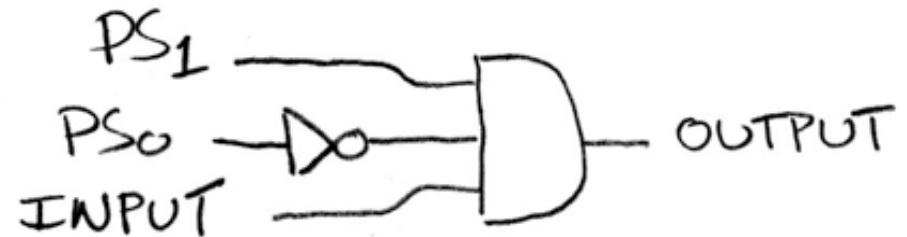

or equivalently...

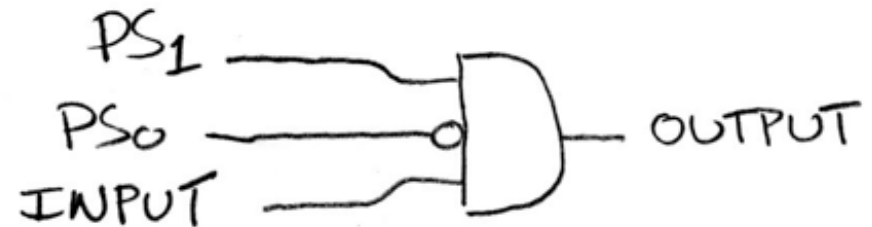


Boolean Algebra

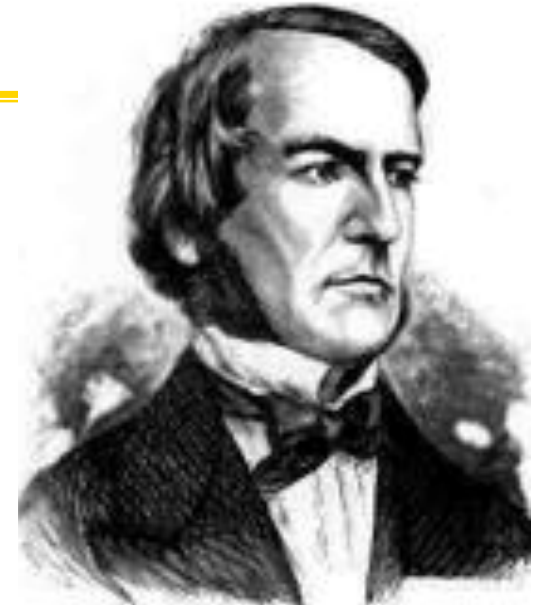

- **George Boole, 19th Century mathematician**
 - **Developed a mathematical system (algebra) involving logic**
 - later known as “Boolean Algebra”
 - **Primitive functions: AND, OR and NOT**
 - **The power of BA is there’s a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA**
- + means OR, • means AND, \bar{x} means NOT**



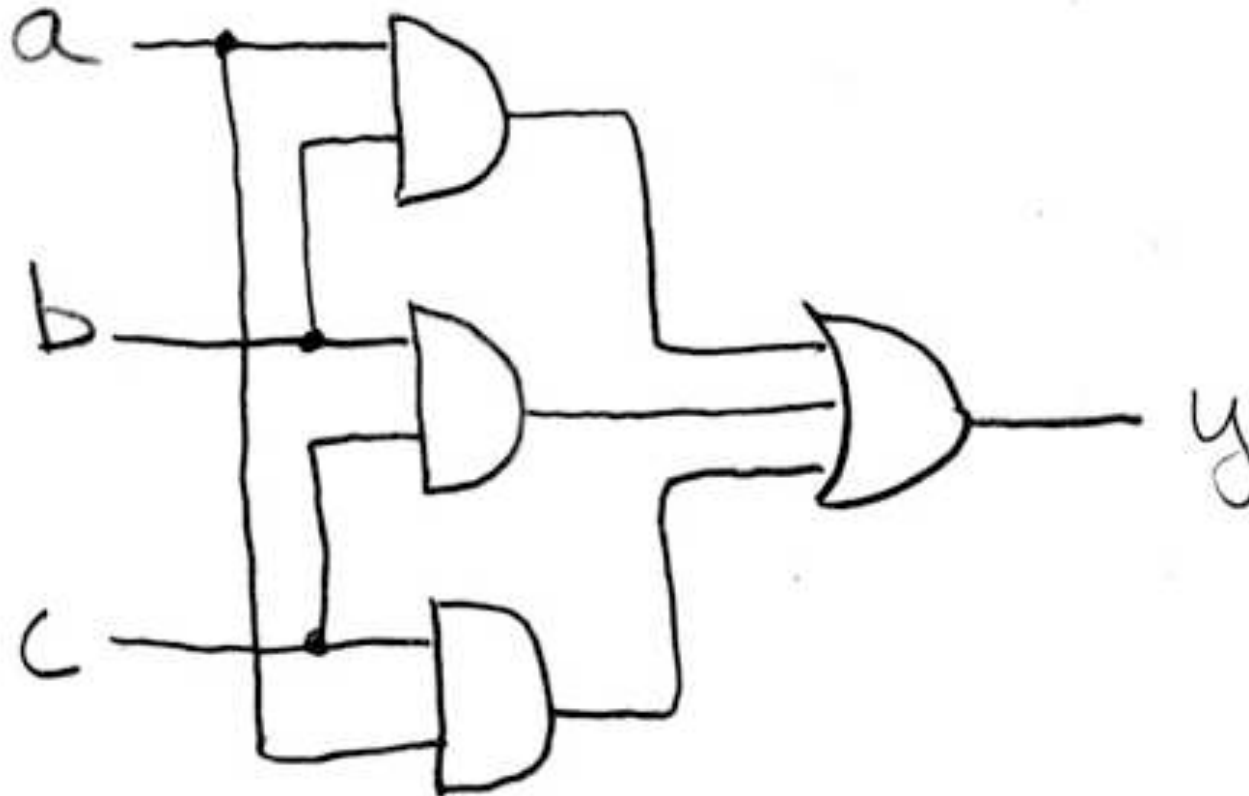Boolean Algebra (e.g., for majority fun.)




$$y = a \cdot b + a \cdot c + b \cdot c$$


$$y = ab + ac + bc$$

Boolean Algebra (e.g., for FSM)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

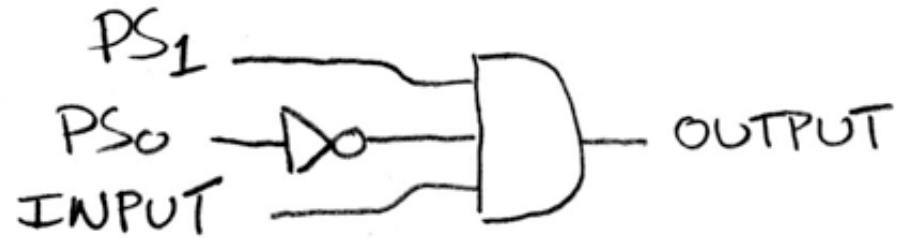


or equivalently...

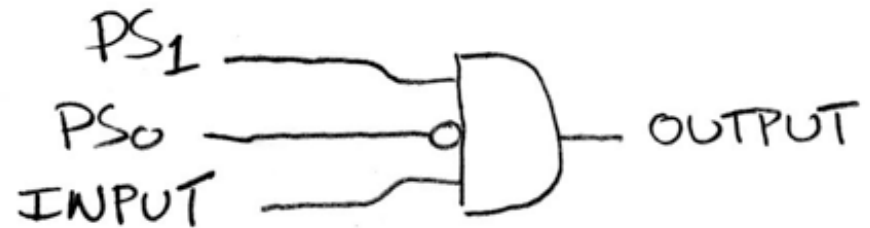

$$y = PS_1 \cdot \overline{PS_0} \cdot \text{INPUT}$$

BA: Circuit & Algebraic Simplification

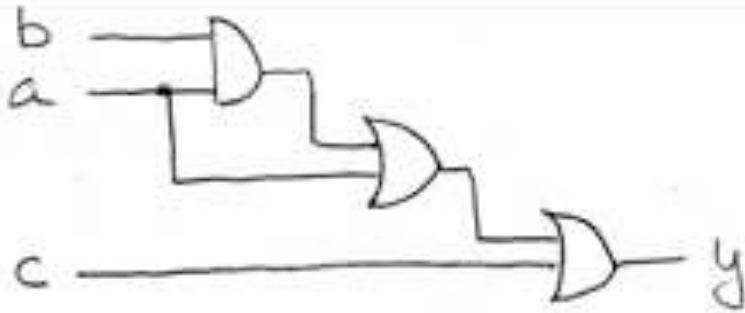


original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

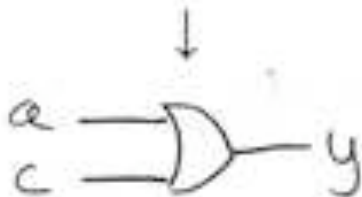

simplified circuit

**BA also great for
circuit verification
Circ X = Circ Y?
use BA to prove!**

Laws of Boolean Algebra

$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + x = x$	$(x + y)x = x$	uniting theorem
$\overline{x \cdot y} = \bar{x} + \bar{y}$	$\overline{(x + y)} = \bar{x} \cdot \bar{y}$	DeMorgan's Law



Boolean Algebraic Simplification Example

$$\begin{aligned}y &= ab + a + c \\ &= a(b + 1) + c && \text{distribution, identity} \\ &= a(1) + c && \text{law of 1's} \\ &= a + c && \text{identity}\end{aligned}$$



Canonical forms (1/2)

	abc	y
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1
$\bar{a} \cdot \bar{b} \cdot c$	001	1
	010	0
	011	0
$a \cdot \bar{b} \cdot \bar{c}$	100	1
	101	0
$a \cdot b \cdot \bar{c}$	110	1
	111	0




**Sum-of-products
(ORs of ANDs)**

Canonical forms (2/2)

$$\begin{aligned}y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\ &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) \\ &= \bar{a}\bar{b}(1) + a\bar{c}(1) \\ &= \bar{a}\bar{b} + a\bar{c}\end{aligned}$$

distribution
complementarity
identity

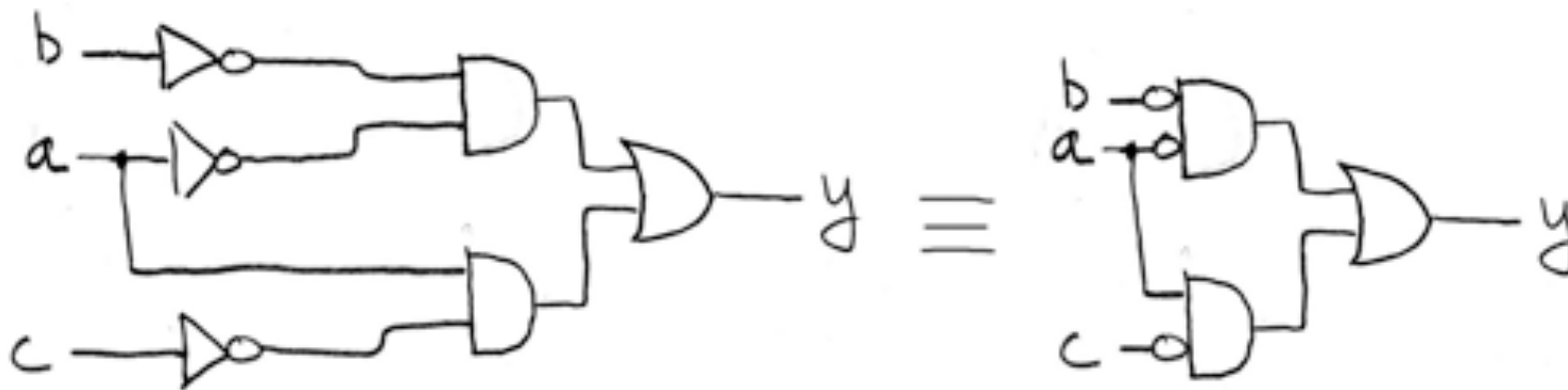

Peer Instruction

- A. $(a+b) \cdot (\bar{a}+b) = b$
- B. N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND
- C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT

“And In conclusion...”

- Use this table and techniques we learned to transform from 1 to another

