

inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**

## Lecture 26 – Single Cycle CPU Datapath, with Verilog

**2004-10-29**



**Lecturer PSOE Dan Garcia**

[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)

**Halloween plans?** ⇒ Try the Castro!

Sun 2004-10-31,  
from 7pm-mid  
(\$3 donation)

go at least  
once...




CS61C L26 Single Cycle CPU Datapath, with Verilog (1)




[halloweeninthecastro.com](http://halloweeninthecastro.com)

Garcia, Fall 2004 © UCB

# Anatomy: 5 components of any Computer

 

This week  
and next

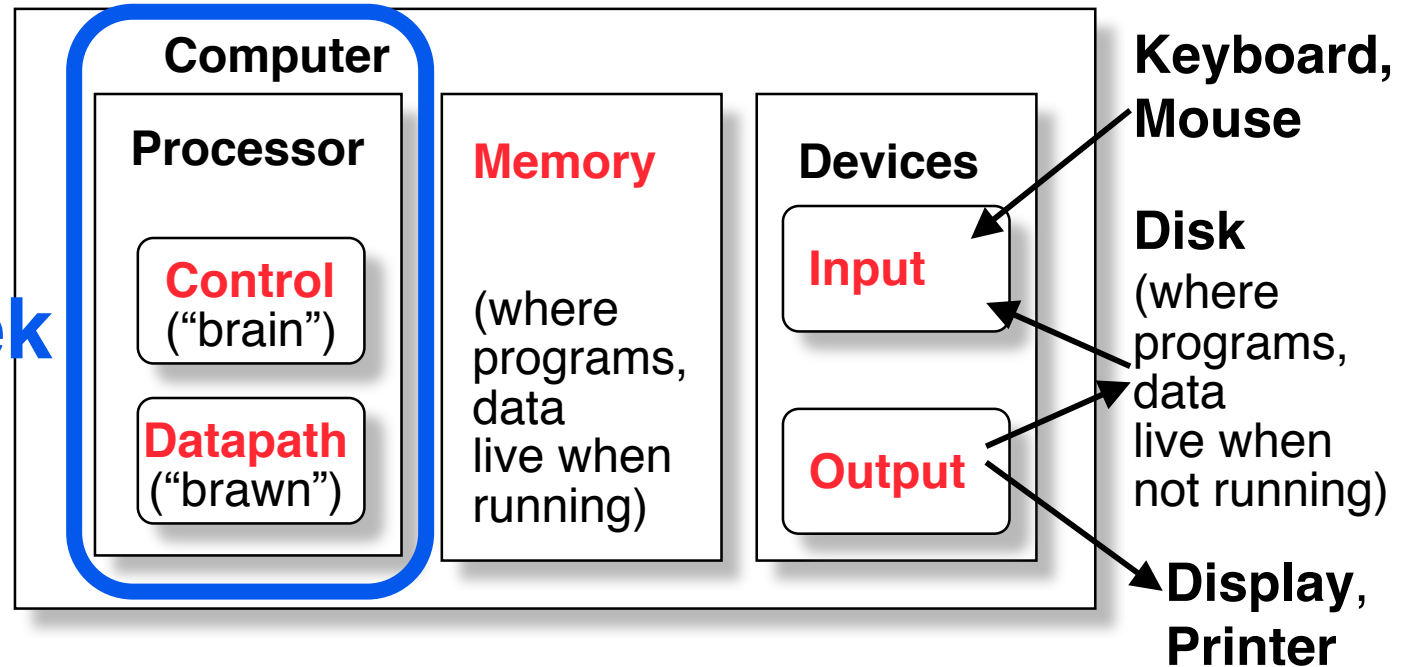

# Outline of Today's Lecture

---

- **Design a processor: step-by-step**
- **Requirements of the Instruction Set**
- **Hardware components that match the instruction set requirements**




# How to Design a Processor: step-by-step

- **1. Analyze instruction set architecture (ISA)**  
**=> datapath requirements**
  - meaning of each instruction is given by the *register transfers*
  - datapath must include storage element for ISA registers
  - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic


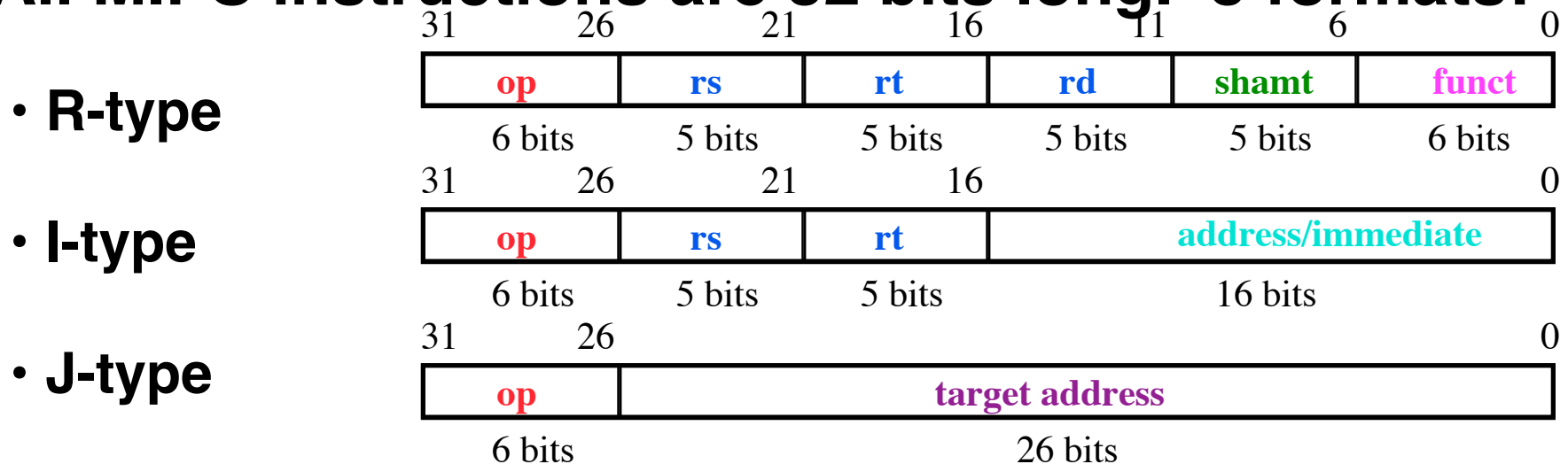
# Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:




- The different fields are:
  - **op**: operation (“opcode”) of the instruction
  - **rs, rt, rd**: the source and destination register specifiers
  - **shamt**: shift amount
  - **funct**: selects the variant of the operation in the “op” field
  - **address / immediate**: address offset or immediate value
  - **target address**: target address of jump instruction




# Step 1a: The MIPS-lite Subset for today


## • ADDU and SUBU

 

## • OR Immediate:

 


## • LOAD and STORE Word

 

`• sw rt,rs,imm16`

## • BRANCH:

 



# Step 1: Requirements of the Instruction Set

---

- **Memory (MEM)**
  - instructions & data
- **Registers (R: 32 x 32)**
  - read RS
  - read RT
  - Write RT or RD
- **PC**
- **Extender (sign extend)**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**





## Step 2: Components of the Datapath

---

- **Combinational Elements**
- **Storage Elements**
  - Clocking methodology



# 16-bit Sign Extender for MIPS Interpreter

---

```
// Sign extender from 16- to 32-bits.
module signExtend (in,out);
    input    [15:0] in;
    output   [31:0] out;
    reg      [31:0] out;

    out = { in[15], in[15], in[15], in[15],
            in[15], in[15], in[15], in[15],
            in[15], in[15], in[15], in[15],
            in[15], in[15], in[15], in[15],
            in[15:0] };
endmodule // signExtend
```



## 2-bit Left shift for MIPS Interpreter

---


```
// 32-bit Shift left by 2
module leftShift2 (in,out);
    input [31:0] in;
    output [31:0] out;
    reg [31:0] out;

    out = { in[29:0], 1'b0, 1'b0 };
endmodule // leftShift2
```




# Combinational Logic Elements (Building Blocks)


## • Adder

 

## • MUX

 

## • ALU

 

# Verilog 32-bit Adder for MIPS Interpreter

---

```
//Behavioral model of 32-bit adder.  
module add32 (S,A,B);  
    input    [31:0] A,B;  
    output   [31:0] S;  
    reg      [31:0] S;  
  
    always @ (A or B)  
        S = A + B;  
endmodule // add32
```



# Verilog 32-bit Register for MIPS Interpreter

---

```
// Behavioral model of 32-bit wide
// 2-to-1 multiplexor.
module mux32 (in0,in1,select,out) ;
    input [31:0] in0,in1;
    input      select;
    output [31:0] out;
    reg [31:0] out;

    always @ (in0 or in1 or select)
        if (select) out=in1;
        else      out=in0;

endmodule // mux32
```



# ALU Needs for MIPS-lite + Rest of MIPS

---

- Addition, subtraction, logical OR, ==:

```
ADDU R[rd] = R[rs] + R[rt]; ...
```

```
SUBU R[rd] = R[rs] - R[rt]; ...
```

```
ORI R[rt] = R[rs] |  
zero_ext(Imm16) ...
```

```
BEQ if ( R[rs] == R[rt] ) ...
```

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND,  
Set Less Than (1 if  $A < B$ , 0 otherwise)



• Behavioral ALU follows chap 5

# Verilog ALU for MIPS Interpreter (1/3)

---

```
// Behavioral model of ALU:  
// 8 functions and "zero" flag,  
// A is top input, B is bottom
```

```
module ALU (A,B,control,zero,result) ;  
    input    [31:0]  A, B;  
    input    [2:0]   control;  
    output   zero; // used for beq,bne  
    output  [31:0]  result;  
  
    reg      zero;  
    reg [31:0] result, C;  
    always @ (A or B or control) ...
```





## Verilog ALU for MIPS Interpreter (2/3)

---

```
reg [31:0]      result, C;
always @ (A or B or control)
  begin
case (control)
3'b000: // AND
  result=A&B;
3'b001: // OR
  result=A|B;
3'b010: // add
  result=A+B;
3'b110: // subtract
  result=A-B; // Documents bugs below
3'b111: // set on less than
  // old version (fails if A is
  // negative and B is positive)
  // result = (A<B)? 1 : 0; wrong
  // Why did it fail?
```



## Verilog ALU for MIPS Interpreter (3/3)

---

```
// result = (A<B)? 1 : 0; wrong
// current version
// if A and B have the same sign,
// then A<B works (slt == 1 if A-B<0)
// if A and B have different signs,
// then A<B if A is negative
// (slt == 1 if A<0)
    begin
        C = A - B;
        result = (A[31]^B[31])? A[31] :
                C[31];
    end
endcase // case(control)
zero = (result==0) ? 1'b1 : 1'b0;
end // always @ (A or B or control)
endmodule // ALU
```



# Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

- **Clock input (CLK)**

 - The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
  - Address valid  $\Rightarrow$  Data Out valid after “access time.”



# Verilog Memory for MIPS Interpreter (1/3)

```
// Behavioral model of Random Access Memory:  
// 32-bit wide, 256 words deep,  
// asynchronous read-port if RD=1,  
// synchronous write-port if WR=1,  
// initialize from hex file ("data.dat")  
// on positive edge of reset signal,  
// dump to binary file ("dump.dat")  
// on positive edge of dump signal.
```

```
module mem
```

```
(CLK, RST, DMP, WR, RD, address, writeD, readD);
```

```
input CLK, RST, DMP, WR, RD;
```

```
input [31:0] address, writeD;
```

```
output [31:0] readD;
```

```
reg [31:0] readD;
```

```
parameter memSize=256; // ~ Constant dec.
```

```
reg [31:0] memArray [0:memSize-1];
```

```
integer chann, i;
```

```
// Temp variables: for loops
```



## Verilog Memory for MIPS Interpreter (2/3)

---

```
integer      chann, i;
  always @ (posedge RST)
    $readmemh("data.dat", memArray);
  always @ (posedge CLK)
    if (WR) memArray[address[9:2]] =
                                                    written;
// write if WR & positive clock edge (synchronous)
  always @ (address or RD)
    if (RD)
      begin
        readD = memArray[address[9:2]];
        $display("Getting address %h
containing %h", address[9:2], readD);
      end
// read if RD, independent of clock (asynchronous)
```



# Verilog Memory for MIPS Interpreter (3/3)

---

```
end;
always @ (posedge DMP)
begin
    chann = $fopen("dump.dat");
    if (chann==0)
        begin
            $display("$fopen of
dump.dat failed.");
            $finish;
        end
        // Temp variables chan, i
    for (i=0; i<memSize; i=i+1)
        begin
            $fdisplay(chann, "%b",
                    memArray[i]);
        end
    end // always @ (posedge DMP)
endmodule // mem
```



# Peer Instruction

---

- A. We should use the main ALU to compute  $PC=PC+4$
- B. We're going to be able to read 2 registers and write a 3<sup>rd</sup> in 1 cycle
- C. Datapath is hard, Control is easy

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



# Summary: Single cycle datapath

## ◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

## ◦ Control is the hard part

## ◦ Next time!

