

inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**

## Lecture 27 – Single Cycle CPU Datapath, with Verilog II




**2004-11-01**

**Lecturer PSOE Dan Garcia**

**[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)**

**Another shutout for Cal! ⇒**

 **Unbelievable! The #4 Bears were dominant in beating ASU 27-0. JJ Arrington shatters Cal records w/his 7<sup>th</sup>-straight 100yd game, becoming the fastest Cal player ever to reach 1,000 yds. It's ASU's 1<sup>st</sup> shutout loss in 9 yrs & our first time in the top 5 in 52 years!!**



# Why is it “`memArray [address [9:2]]`”?

---

- **Our memory is always byte-addressed**
  - We can `1b` from `0x0`, `0x1`, `0x2`, `0x3`, ...
- **`1w` only reads word-aligned requests**
  - We only call `1w` with `0x0`, `0x4`, `0x8`, `0xC`, ...
  - I.e., the last two bits are always 0
- **`memArray` is a word wide and  $2^8$  deep**
  - `reg [31:0] memArray [0:256-1];`
  - Size = 4 Bytes/row \* 256 rows = 1024 B
  - If we're simulating `1w/sw`, we R/W words
  - What bits select the first 256 words? `[9:2]!`
  - 1<sup>st</sup> word = `0x0 = 0b000 = memArray[0];`  
2<sup>nd</sup> word = `0x4 = 0b100 = memArray[1], etc.`



# How to Design a Processor: step-by-step


- **1. Analyze instruction set architecture (ISA)**  
**=> datapath requirements**
  - meaning of each instruction is given by the *register transfers*
  - datapath must include storage element for ISA registers
  - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic (hard part!)**


 
# Storage Element: Register (Building Block)

---

- **Similar to D Flip Flop except**
  - N-bit input and output
  - Write Enable input
- **Write Enable:**
  - negated (or deasserted) (0):  
Data Out will not change
  - asserted (1):  
Data Out will become Data In



# Verilog 32-bit Register for MIPS Interpreter

---

```
// Behavioral model of 32-bit Register:  
// positive edge-triggered,  
// synchronous active-high reset.  
module reg32 (CLK,Q,D,wEnb) ;  
    input    CLK, wEnb;  
    input    [31:0] D;  
    output   [31:0] Q;  
    reg     [31:0] Q;  
  
    always @ (posedge CLK)  
        if (wEnb)  
            Q = D;  
endmodule // reg32
```




# Storage Element: Register File

- Register File consists of 32 registers:

- Two 32-bit output busses:

busA and busB

- One 32-bit input bus: busW

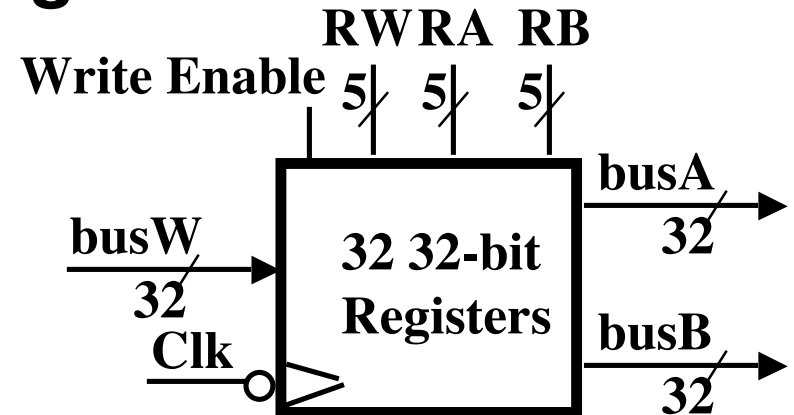

- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:

- RA or RB valid => busA or busB valid after “access time.”



# Verilog Register File for MIPS Interpreter (1/3)

---

```
// Behavioral model of register file:  
// 32-bit wide, 32 words deep,  
// two asynchronous read-ports,  
// one synchronous write-port.  
// Dump register file contents to  
// console on pos edge of dump signal.
```



## Verilog Register File for MIPS Interpreter (2/3)

```
module regFile (CLK, wEnb, DMP,  
    writeReg, writeD, readReg1, readD1,  
    readReg2, readD2);  
    input CLK, wEnb, DMP;  
    input [4:0] writeReg, readReg1,  
        readReg2;  
    input [31:0] writeD;  
    output [31:0] readD1, readD2;  
    reg [31:0] readD1, readD2;  
    reg [31:0] array [0:31];  
    reg dirty1, dirty2;  
    integer i;
```

- 3 5-bit fields to select registers: 1 write register, 2 read register





# Verilog Register File for MIPS Interpreter (3/3)

---

```
always @ (posedge CLK)
    if (wEnb)
        if (writeReg!=5'h0) // why?
            begin
                array[writeReg] = writeD;
                dirty1=1'b1;
                dirty2=1'b1;
            end
always @ (readReg1 or dirty1)
    begin
        readD1 = array[readReg1];
        dirty1=0;
    end
```



## Step 3: Assemble DataPath meeting requirements


---

- Register Transfer Requirements  
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation


 
## 3a: Overview of the Instruction Fetch Unit


- The common RTL operations
  - Fetch the Instruction:  $\text{mem}[\text{PC}]$
  - Update the program counter:
    - Sequential Code:  $\text{PC} = \text{PC} + 4$
    - Branch and Jump:  $\text{PC} = \text{“something else”}$



 
## 3b: Add & Subtract

•  $R[rd] = R[rs] \text{ op } R[rt]$  Ex.: `addU rd,rs,rt`

- Ra, Rb, and Rw come from instruction's **Rs**, **Rt**, and **Rd** fields




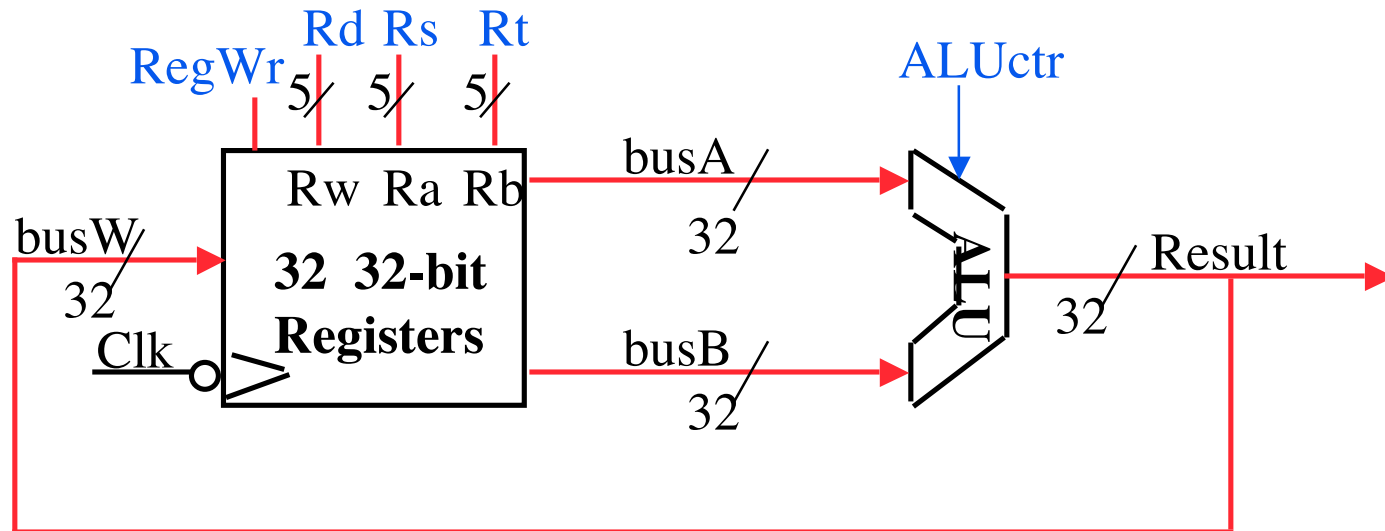- **ALUctr** and **RegWr**: control logic after decoding the instruction



• Already defined register file, ALU



# Clocking Methodology

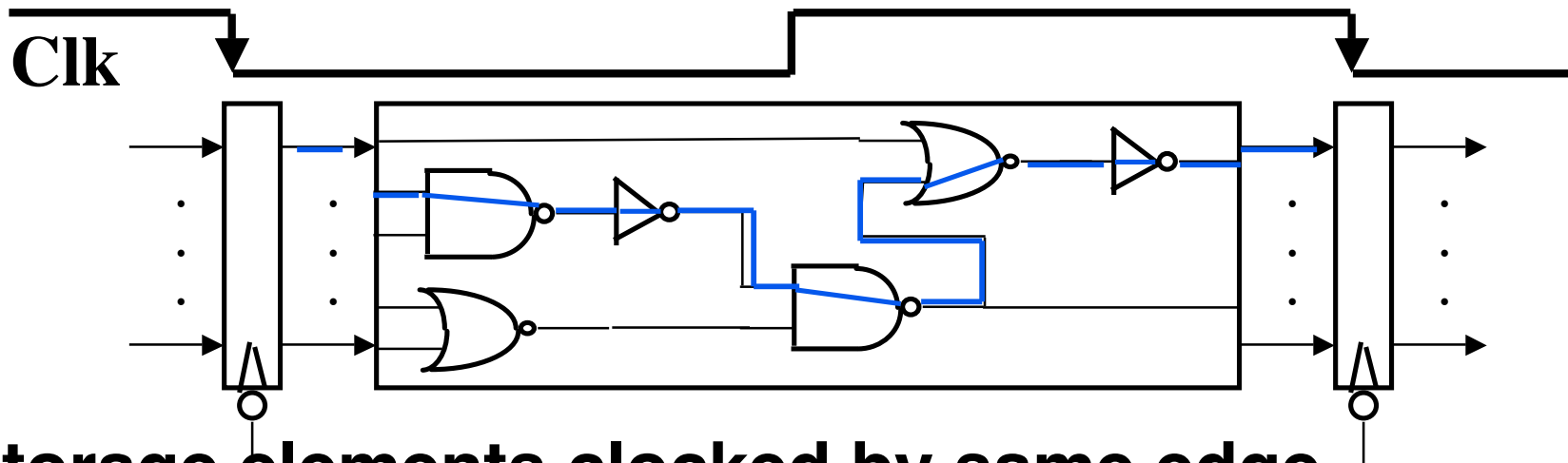

- **Storage elements clocked by same edge**
- **Being physical devices, flip-flops (FF) and combinational logic have some delays**
  - **Gates: delay from input change to output change**
  - **Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF, and we have the usual clock-to-Q delay**
- **“Critical path” (longest path through logic) determines length of clock period**




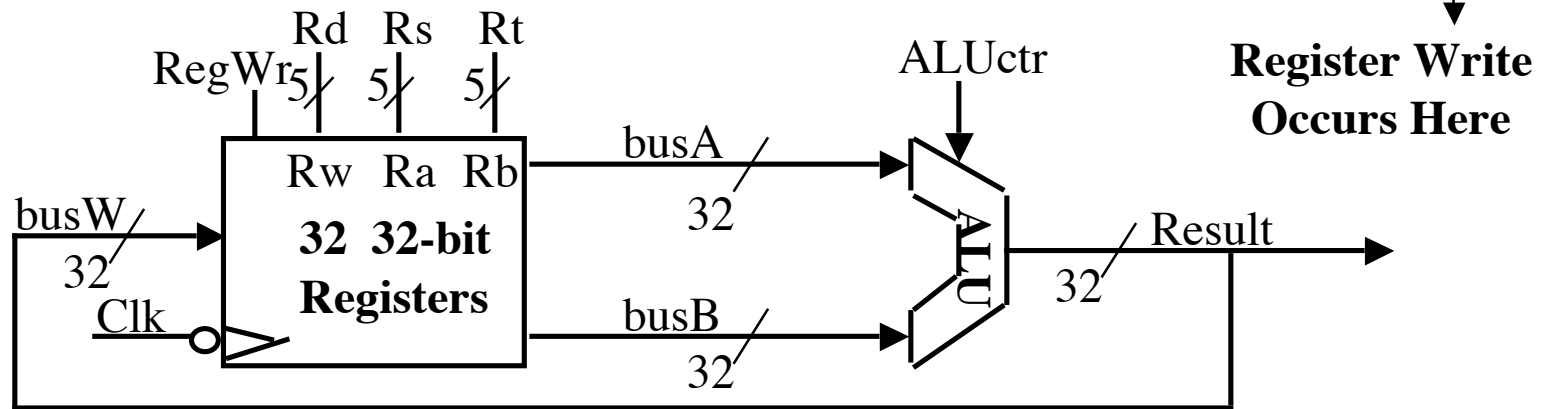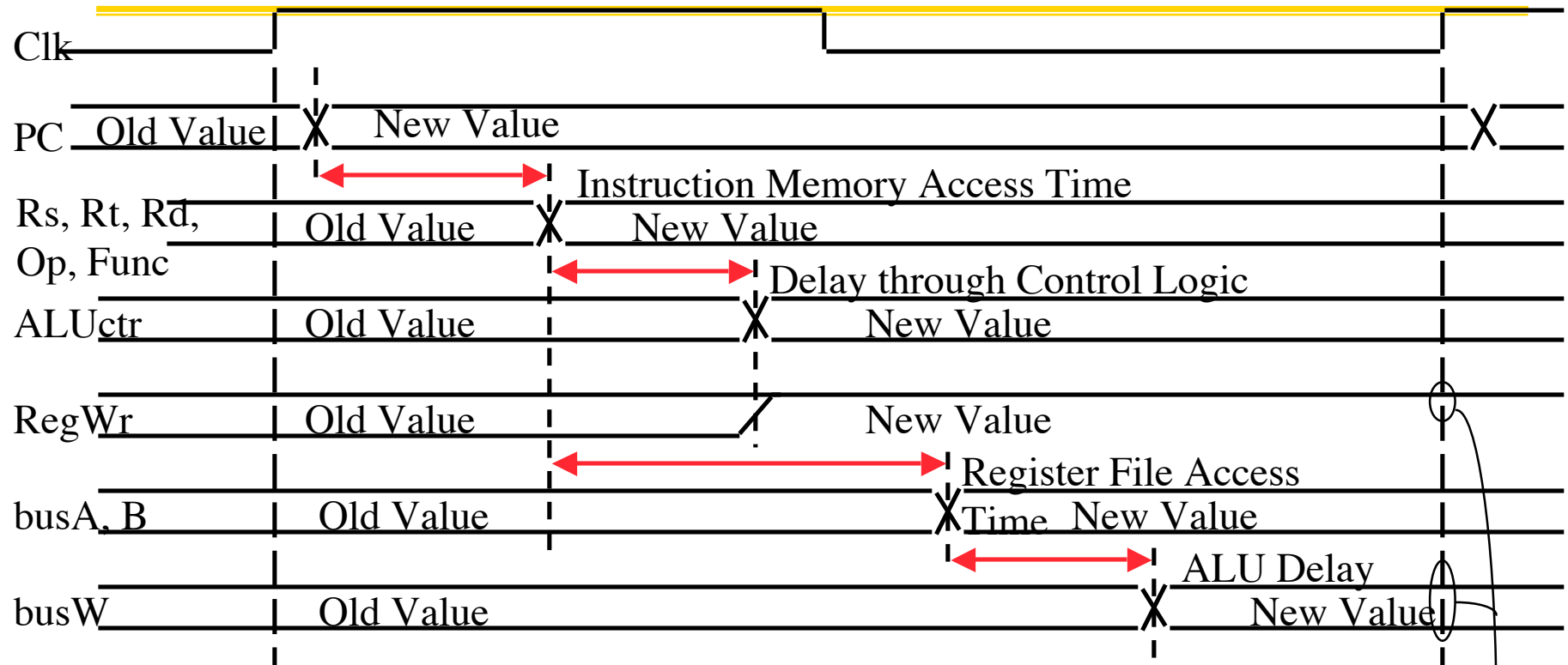
# Register-Register Timing: One complete cycle


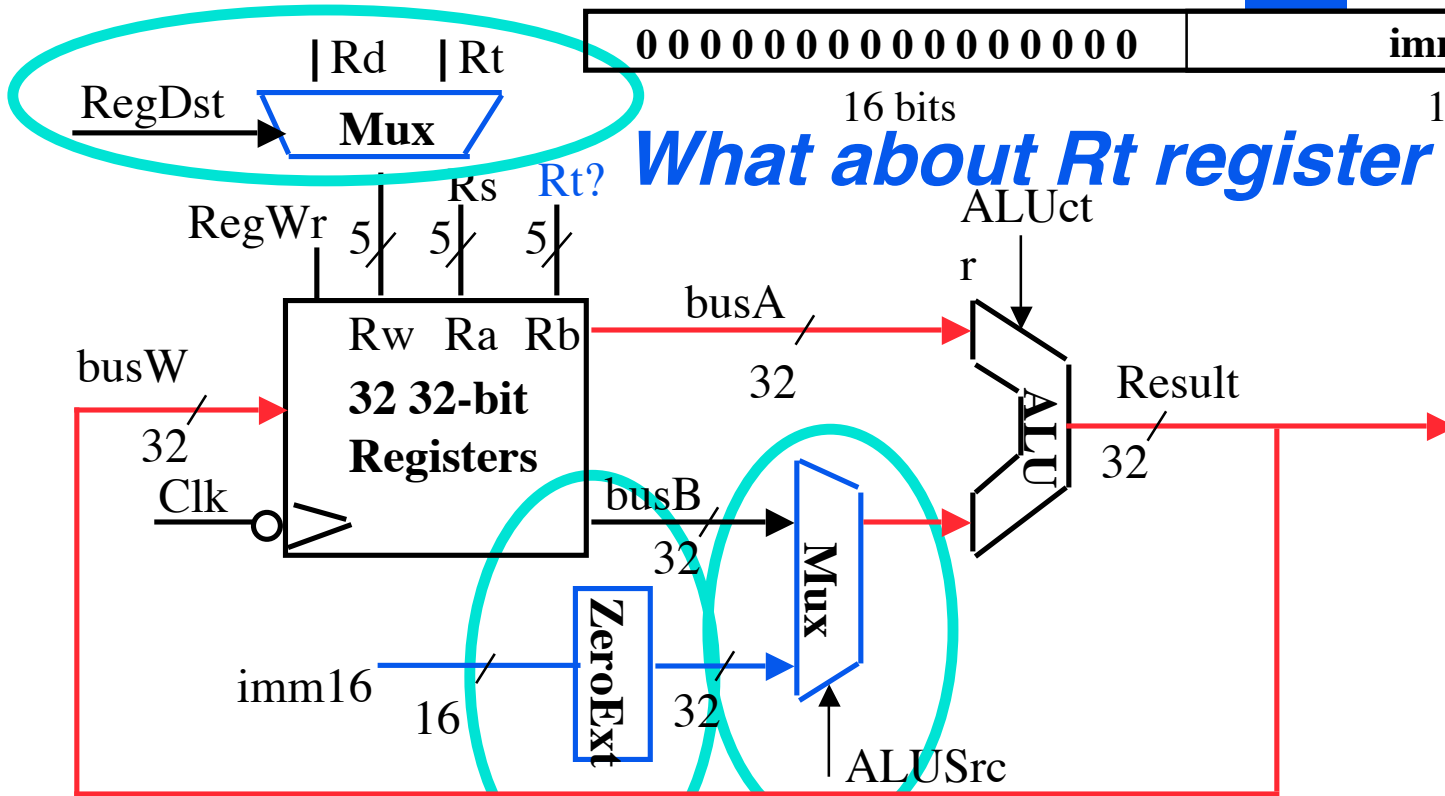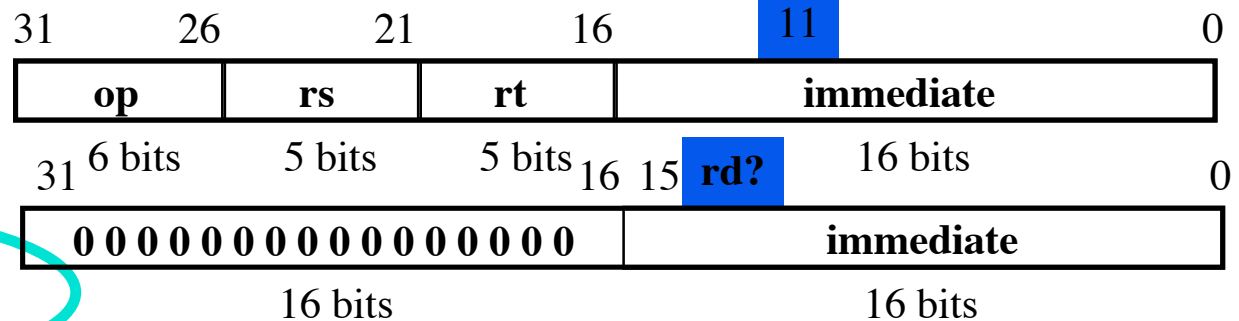
# 3c: Logical Operations with Immediate

- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$





*What about Rt register read??*



• Already defined 32-bit MUX; Zero Ext?
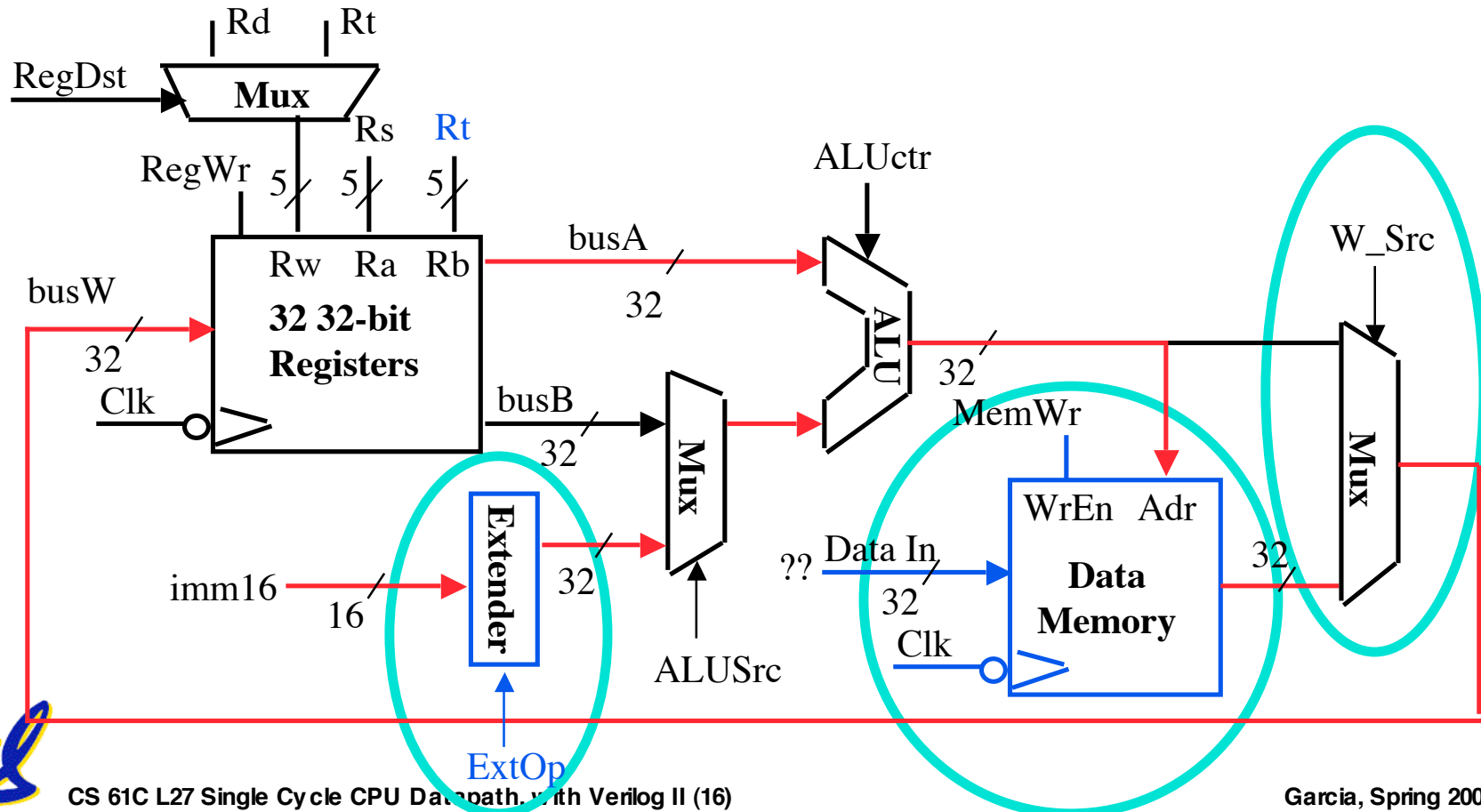 
# 3d: Load Operations


- $R[rt] = Mem[R[rs] + SignExt[imm16]]$   
**Example: `lw rt, rs, imm16`**





 
# 3e: Store Operations

- $\text{Mem}[ R[\text{rs}] + \text{SignExt}[\text{imm16}] ] = R[\text{rt}]$   
 Ex.: `sw rt, rs, imm16`



# 3f: The Branch Instruction

---

 



- **beq rs, rt, imm16**
  - **mem[PC] Fetch the instruction from memory**
  - **Equal = R[rs] == R[rt] Calculate branch condition**
  - **if (Equal) Calculate the next instruction's address**
    - **PC = PC + 4 + ( SignExt(imm16) x 4 )**
  - else**
    - **PC = PC + 4**



# Datapath for Branch Operations

- **beq rs, rt, imm16**


**Datapath generates condition (equal)**

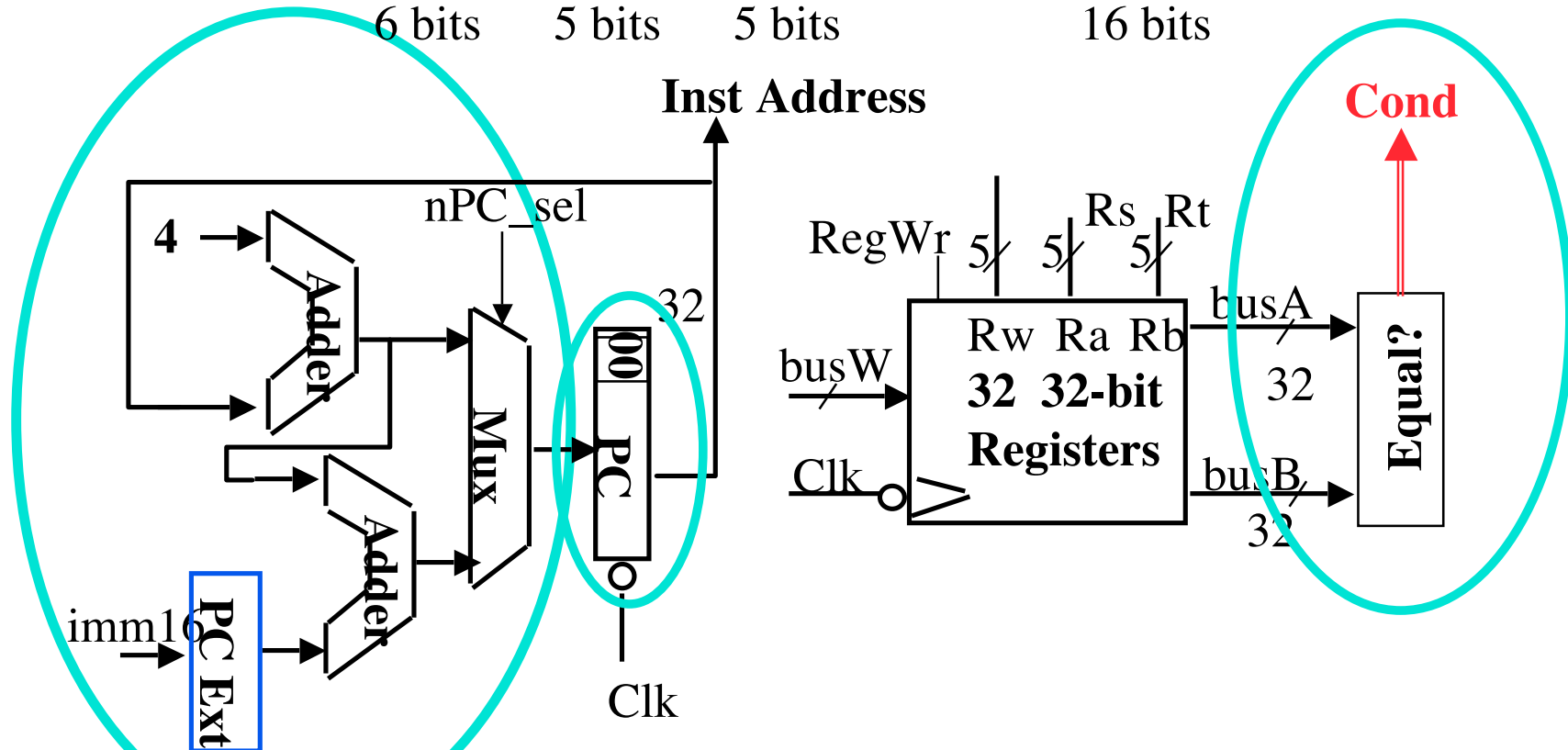 


• **Already MUX, adder, sign extend, zero**


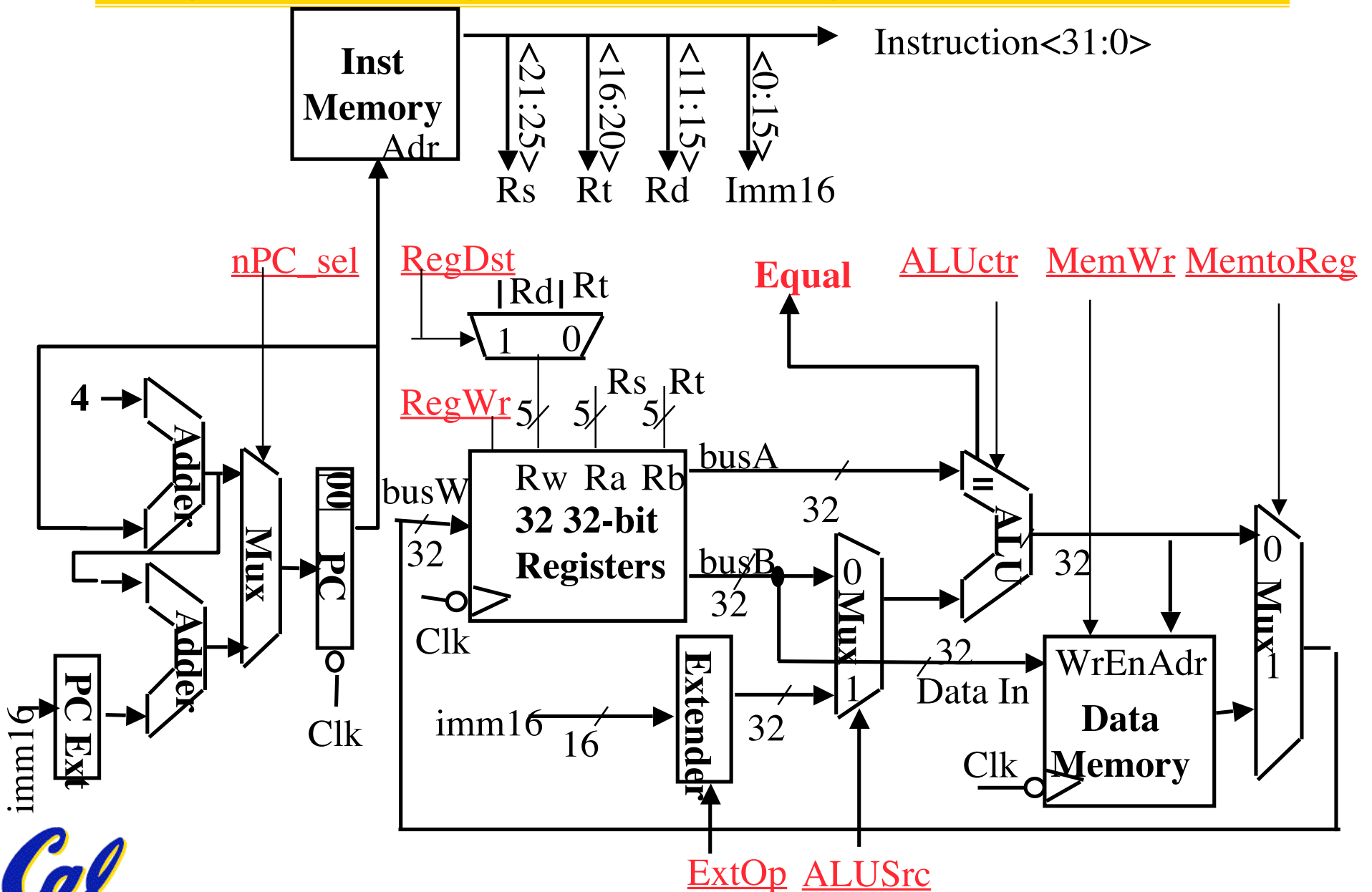
# Putting it All Together: A Single Cycle Datapath



# An Abstract View of the Implementation

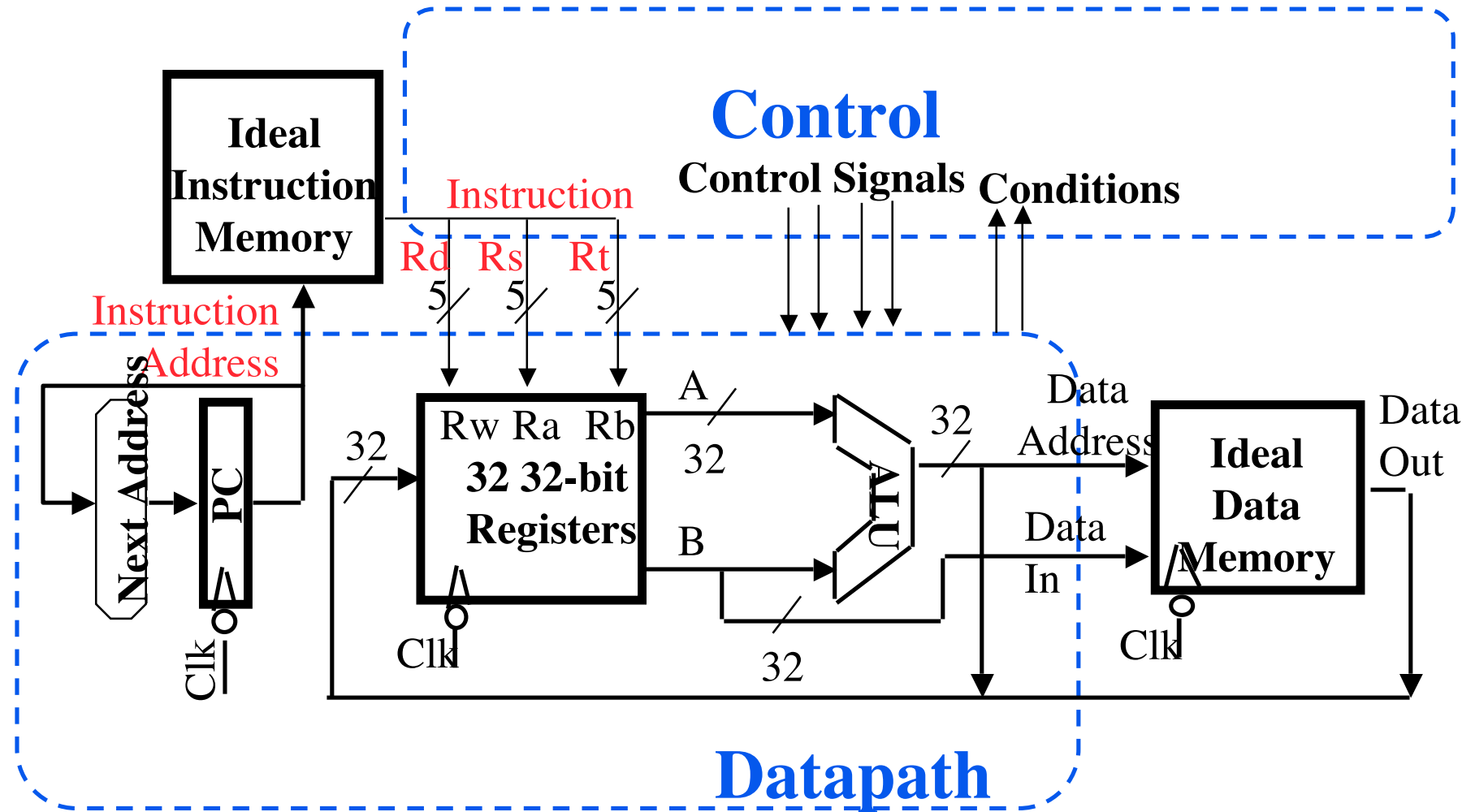

# Peer Instruction

---

Suppose we're writing a MIPS interpreter in Verilog. Which sequence below is best organization for the interpreter?

- A. repeat loop that fetches instructions
- B. while loop that fetches instructions
- C. Decodes instructions using case statement
- D. Decodes instr. using chained if statements
- E. Executes each instruction
- F. Increments PC by 4

- |    |      |
|----|------|
| 1: | ACEF |
| 2: | ADEF |
| 3: | AECF |
| 4: | AEDF |
| 5: | BCEF |
| 6: | BDEF |
| 7: | BECF |
| 8: | BEDF |
| 9: | EF   |
| 0: | FAE  |


# Summary: Single cycle datapath

## ◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

## ◦ Control is the hard part

## ◦ Next time!

 

# Dwarfing the importance of this lecture...

---

...is the importance that tomorrow you  
get out and

# VOTE!

