

2004-11-05

Andrew Schultz

inst.eecs.berkeley.edu/~cs61c-tb




13TB of Memory →  
 Soon after delivering a  
 10,240 processor supercomputer to  
 NASA, SGI delivers a 2,048 node  
 system to Japan with the worlds  
 largest memory capacity, 13TB



[http://www.sgi.com/company\\_info/newsroom/press\\_releases/2004/november/jaeri.html](http://www.sgi.com/company_info/newsroom/press_releases/2004/november/jaeri.html)  
CS 61C L29 Single Cycle CPU Control II (1) Garcia, Fall 2004 © UCB


 
**Review: Single cycle datapath**

- 5 steps to design a processor
  - 1. Analyze instruction set => datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. Assemble the control logic
- **Control is the hard part**
- MIPS makes that easier
  - Instructions same size
  - Source registers always in same place
  - Immediates same size, location
- Operations always on registers/immediates





CS 61C L29 Single Cycle CPU Control II (2) Garcia, Fall 2004 © UCB

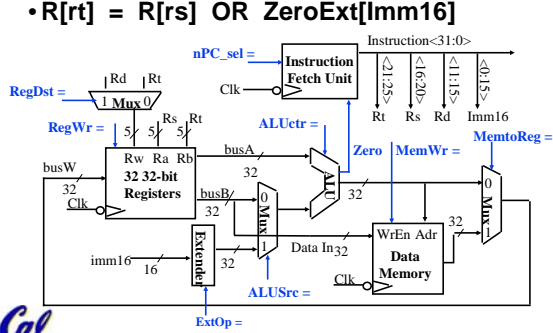 **Single Cycle Datapath during Or Immediate?**





CS 61C L29 Single Cycle CPU Control II (4) Garcia, Fall 2004 © UCB

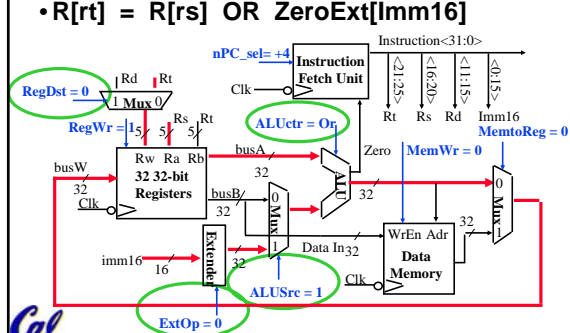 **Single Cycle Datapath during Or Immediate?**





CS 61C L29 Single Cycle CPU Control II (4) Garcia, Fall 2004 © UCB

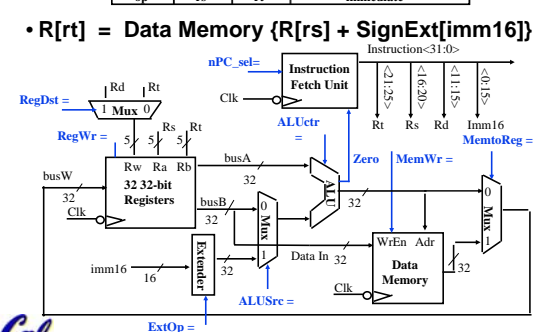 **The Single Cycle Datapath during Load?**









CS 61C L29 Single Cycle CPU Control II (6) Garcia, Fall 2004 © UCB

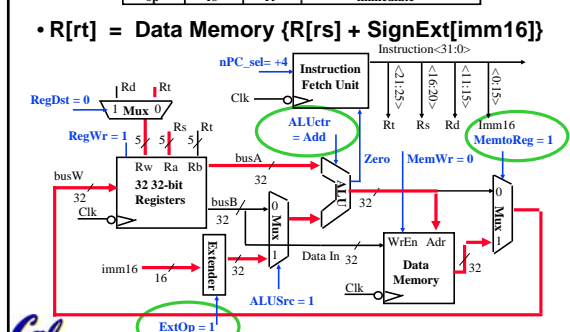 **The Single Cycle Datapath during Load**



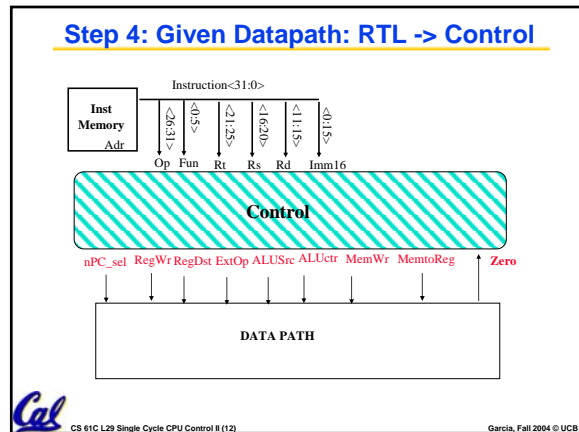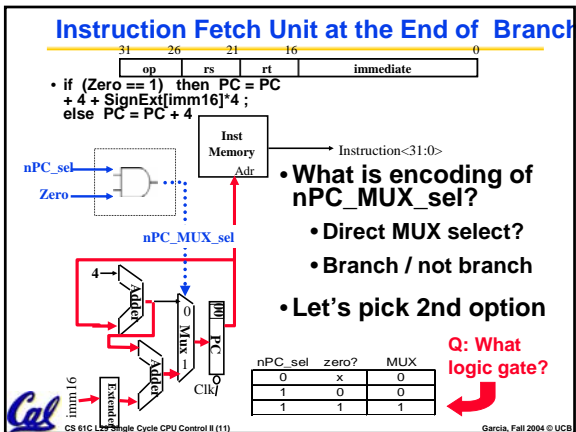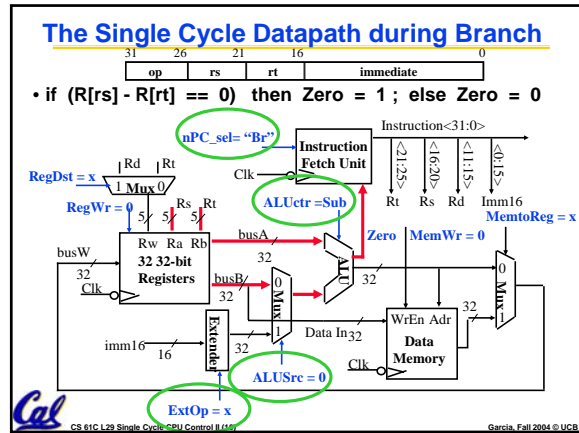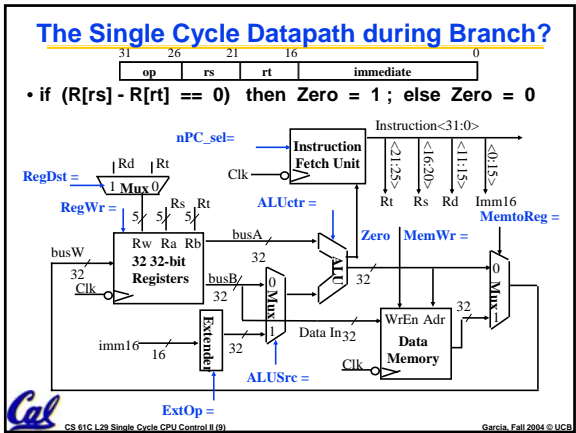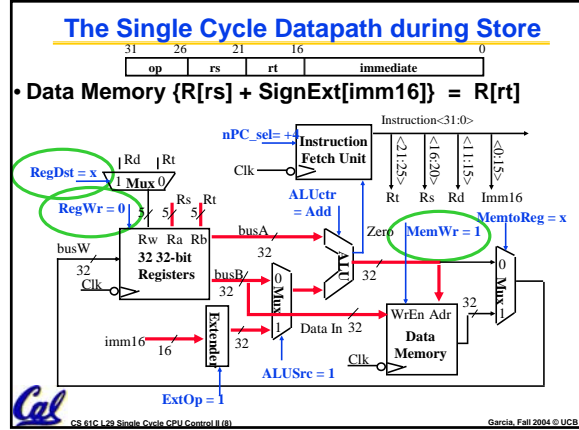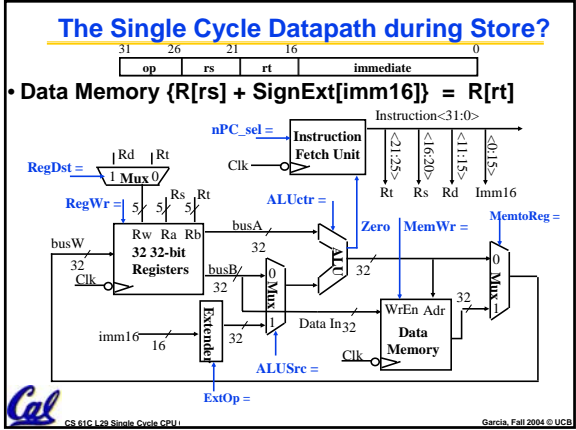CS 61C L29 Single Cycle CPU Control II (6) Garcia, Fall 2004 © UCB



## A Summary of the Control Signals (1/2)

inst	Register Transfer
ADD	$R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$ $ALUSrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC\_sel = "+4"$
SUB	$R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$ $ALUSrc = RegB, ALUctr = "sub", RegDst = rd, RegWr, nPC\_sel = "+4"$
ORI	$R[rt] \leftarrow R[rs] + zero\_ext(Imm16); \quad PC \leftarrow PC + 4$ $ALUSrc = Im, Extop = "Z", ALUctr = "or", RegDst = rt, RegWr, nPC\_sel = "+4"$
LOAD	$R[rt] \leftarrow MEM[R[rs] + sign\_ext(Imm16)]; \quad PC \leftarrow PC + 4$ $ALUSrc = Im, Extop = "Sn", ALUctr = "add",$ $MemtoReg, RegDst = rt, RegWr, \quad nPC\_sel = "+4"$
STORE	$MEM[R[rs] + sign\_ext(Imm16)] \leftarrow R[rs]; \quad PC \leftarrow PC + 4$ $ALUSrc = Im, Extop = "Sn", ALUctr = "add", MemWr, nPC\_sel = "+4"$
BEQ	$if (R[rs] == R[rt]) then PC \leftarrow PC + sign\_ext(Imm16)    00 else PC \leftarrow PC + 4$ $nPC\_sel = "Br", ALUctr = "sub"$




CS 61C L29 Single Cycle CPU Control II (13)

Garcia, Fall 2004 © UCB

## A Summary of the Control Signals (2/2)

See Appendix A

func	10 0000	10 0010	We Don't Care :-)				
op	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	0
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx

 

CS 61C L29 Single Cycle CPU Control II (14)

Garcia, Fall 2004 © UCB

## Administrivia

- Final exam time/location set  
Tuesday, December 14<sup>th</sup>, 12:30 – 3:30 pm  
At the Hearst Gym (lucky us!)




CS 61C L29 Single Cycle CPU Control II (15)

Garcia, Fall 2004 © UCB
 
## Review: Finite State Machine (FSM)

- States represent possible output values.
- Transitions represent changes between states based on inputs.
- Implement with CL and clocked register feedback.



CS 61C L29 Single Cycle CPU Control II (16)

Garcia, Fall 2004 © UCB

## Finite State Machines extremely useful!

- They define
  - How output signals respond to input signals and previous state.
  - How we change states depending on input signals and previous state
- The output signals could be our familiar control signals
  - Some control signals may only depend on CL, not on state at all...
- We could implement very detailed FSMs w/Programmable Logic Arrays



CS 61C L29 Single Cycle CPU Control II (17)

Garcia, Fall 2004 © UCB

## Taking advantage of sum-of-products

- Since sum-of-products is a convenient notation and way to think about design, offer hardware building blocks that match that notation
- One example is Programmable Logic Arrays (PLAs)
- Designed so that can select (program) ands, ors, complements after you get the chip
  - Late in design process, fix errors, figure out what to do later, ...



CS 61C L29 Single Cycle CPU Control II (18)

Garcia, Fall 2004 © UCB

### Programmable Logic Arrays

- Pre-fabricated building block of many AND/OR gates
- "Programmed" or "Personalized" by making or breaking connections among gates
- Programmable array block diagram for sum of products form

**Or Programming:**

- How to combine product terms?
- How many outputs?

**And Programming:**

- How many inputs?
- How to combine inputs?
- How many product terms?

CS 61C L29 Single Cycle CPU Control II (19) Garcia, Fall 2004 © UCB

### Enabling Concept

- Shared product terms among outputs

example:

$$F_0 = A + B'C'$$

$$F_1 = AC' + AB$$

$$F_2 = B'C' + AB$$

$$F_3 = B'C' + A$$

input side: 3 inputs  
 1 = uncomplemented in term  
 0 = complemented in term  
 - = does not participate

output side: 4 outputs  
 1 = term connected to output  
 0 = no connection to output

reuse of terms; 5 product terms

**personality matrix**

Product term	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

CS 61C L29 Single Cycle CPU Control II (20) Garcia, Fall 2004 © UCB

### Before Programming

- All possible connections available before "programming"

CS 61C L29 Single Cycle CPU Control II (21) Garcia, Fall 2004 © UCB

### After Programming

- Unwanted connections are "blown"
  - Fuse (normally connected, break unwanted ones)
  - Anti-fuse (normally disconnected, make wanted connections)

CS 61C L29 Single Cycle CPU Control II (22) Garcia, Fall 2004 © UCB

### Alternate Representation

- Short-hand notation--don't have to draw all the wires
- X Signifies a connection is present and perpendicular signal is an input to gate

notation for implementing

$$F_0 = AB + A'B'$$

$$F_1 = CD' + C'D$$

CS 61C L29 Single Cycle CPU Control II (23) Garcia, Fall 2004 © UCB

### Other Programmable Logic Arrays

- There are other types of PLAs which can be reprogrammed on the fly
- The most common is called a **Field Programmable Gate Array (FPGA)**
- FPGAs are made up of configurable logic blocks (CLBs) and flip-flops which can be programmed by software
- Berkeley has on-going research into reconfigurable computing with FPGAs
  - Check out Brass and BEE2 projects

CS 61C L29 Single Cycle CPU Control II (24) Garcia, Fall 2004 © UCB

### Peer Instruction

**ABC**

1: **SRF**  
 2: **SRT**  
 3: **SEF**  
 4: **SET**  
 5: **BRF**  
 6: **BRT**  
 7: **BEF**  
 8: **BET**

A. MemToReg='x' & ALUctr='sub'. **SUB** or **BEQ**?

B. ALUctr='add'. Which 1 signal is different for all 3 of: ADD, LW, & SW? **RegDst** or **ExtOp**?

C. "Don't Care" signals are useful because we can simplify our PLA personality matrix. **F / T**?

CS 61C L23 Single Cycle CPU Control II (29) Garcia, Fall 2004 © UCB

### And in Conclusion... Single cycle control

- 5 steps to design a processor
  - 1. Analyze instruction set => datapath requirements
  - 2. **Select** set of datapath components & establish clock methodology
  - 3. **Assemble** datapath meeting the requirements
  - 4. **Analyze** implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. **Assemble** the control logic

**Control is the hard part**

- MIPS makes that easier
  - Instructions same size
  - Source registers always in same place
  - Immediates same size, location
  - Operations always on registers/immediates

CS 61C L23 Single Cycle CPU Control II (26) Garcia, Fall 2004 © UCB