

`inst.eecs.berkeley.edu/~cs61c`
CS61C : Machine Structures

**Lecture 29 –
Single Cycle CPU Control II**



2004-11-05

Andrew Schultz

`inst.eecs.berkeley.edu/~cs61c-tb`

**13TB of Memory ⇒
Soon after delivering a
10,240 processor supercomputer to
NASA, SGI delivers a 2,048 node
system to Japan with the worlds
largest memory capacity, 13TB**



Review: Single cycle datapath


◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

◦ **Control** is the hard part


◦ MIPS makes that easier

 - Instructions same size
- Source registers always in same place
- Immediates same size, location




Operations always on registers/immediates

 
Single Cycle Datapath during Or Immediate?



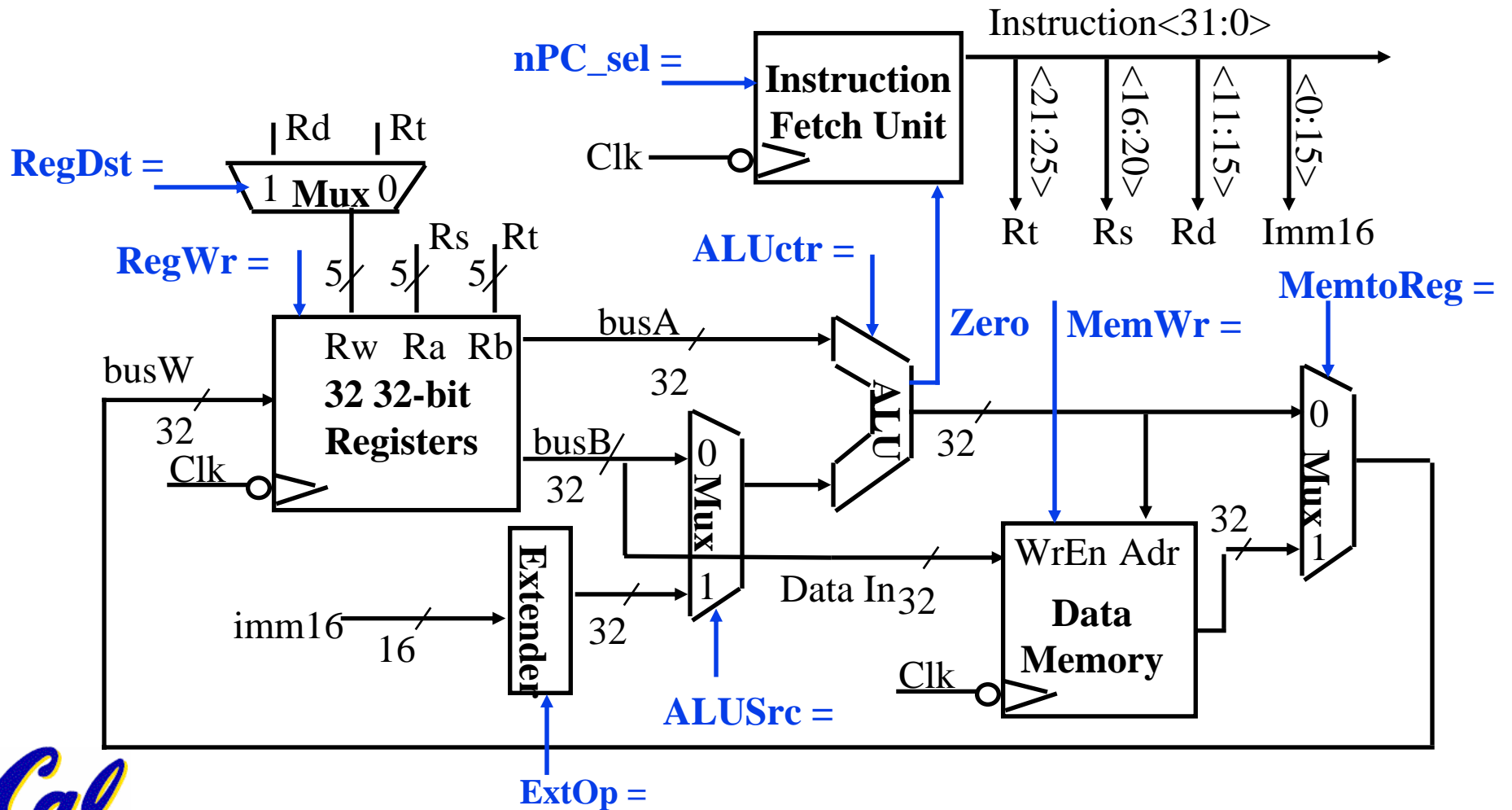
• $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$



 
Single Cycle Datapath during Or Immediate?



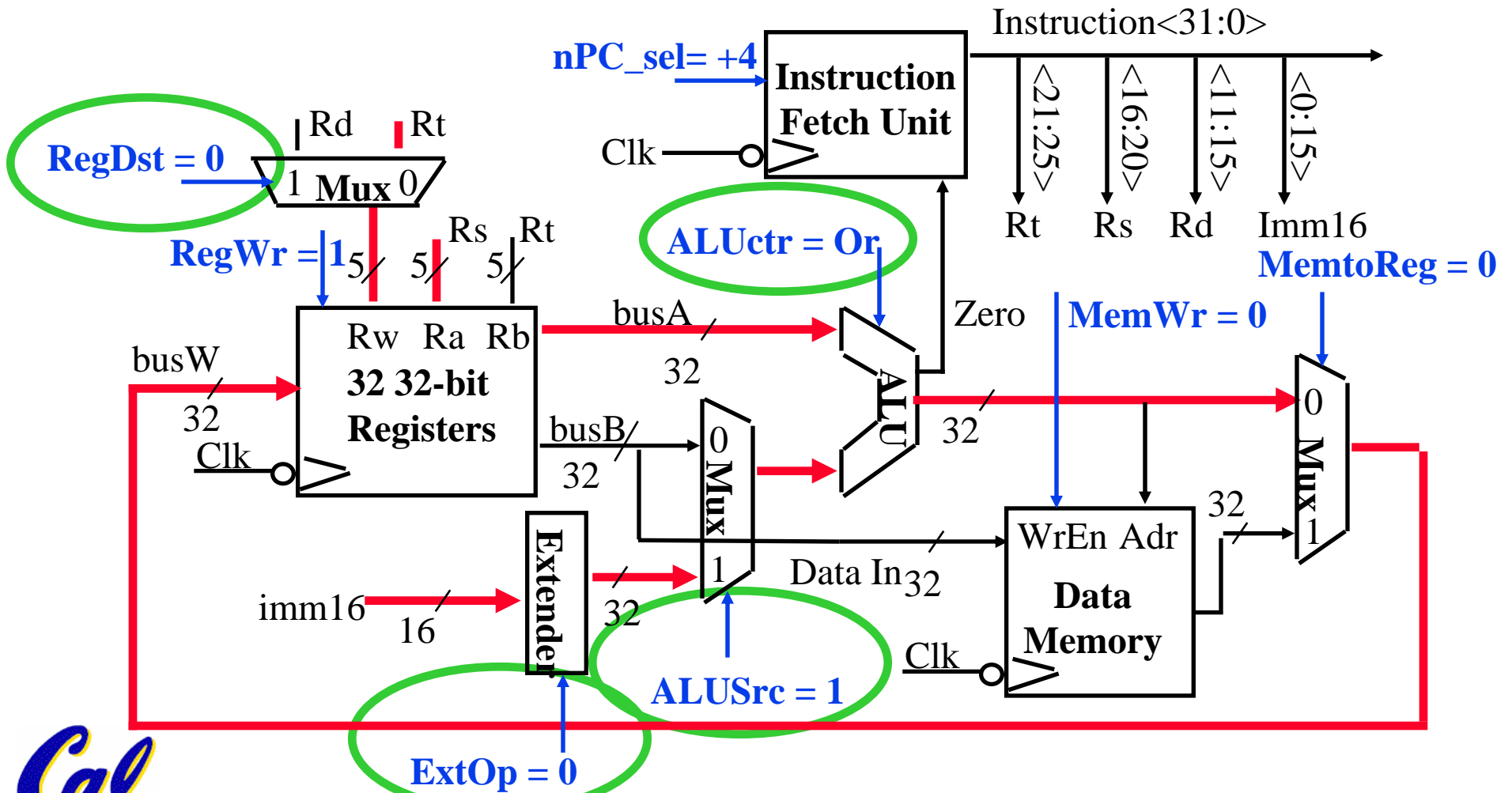
• $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




The Single Cycle Datapath during Load?

 

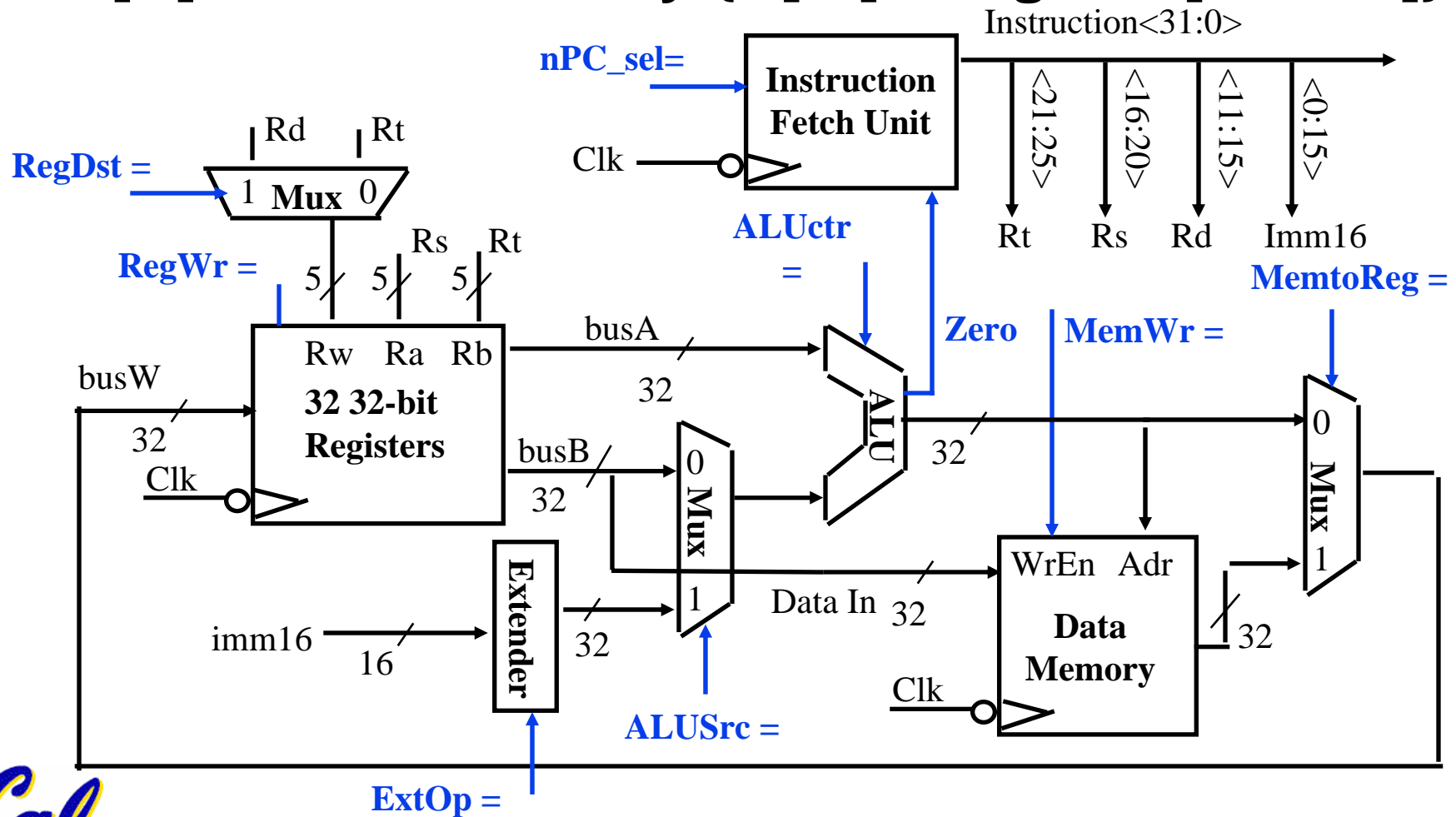
- $R[rt] = \text{Data Memory } \{R[rs] + \text{SignExt}[imm16]\}$




The Single Cycle Datapath during Load

 

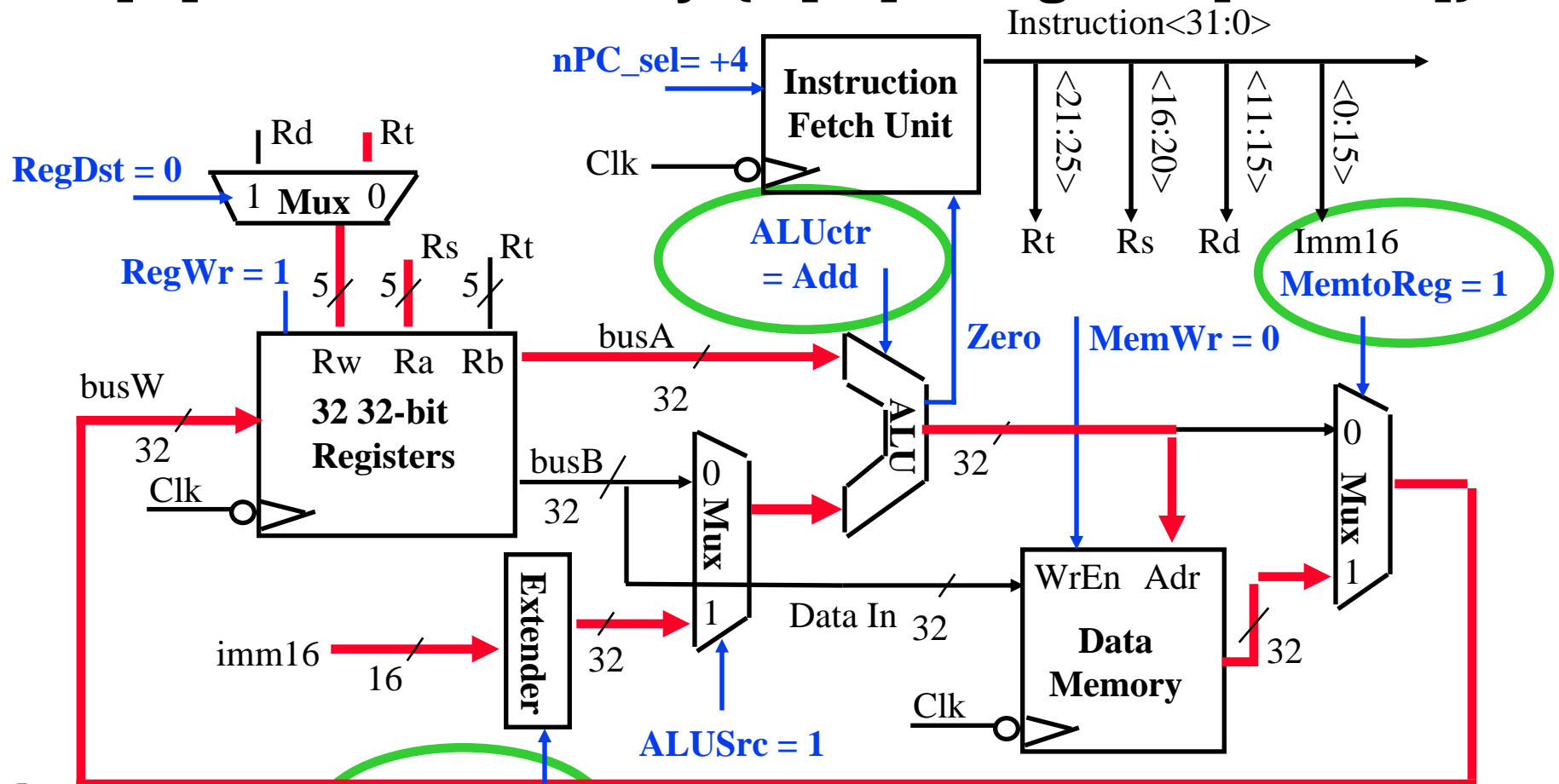
- $R[rt] = \text{Data Memory } \{R[rs] + \text{SignExt}[imm16]\}$




The Single Cycle Datapath during Store?

 

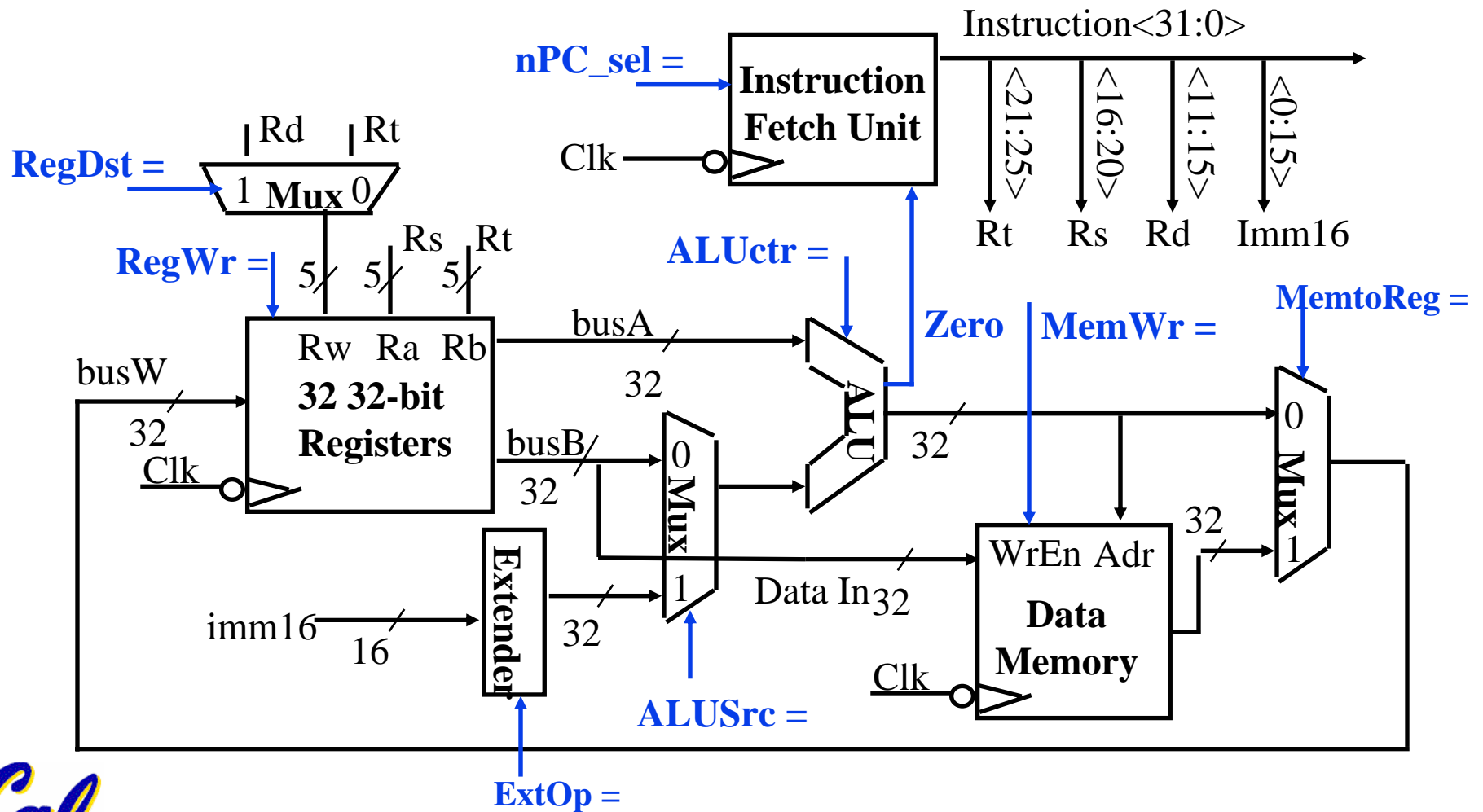
- Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




The Single Cycle Datapath during Store

 

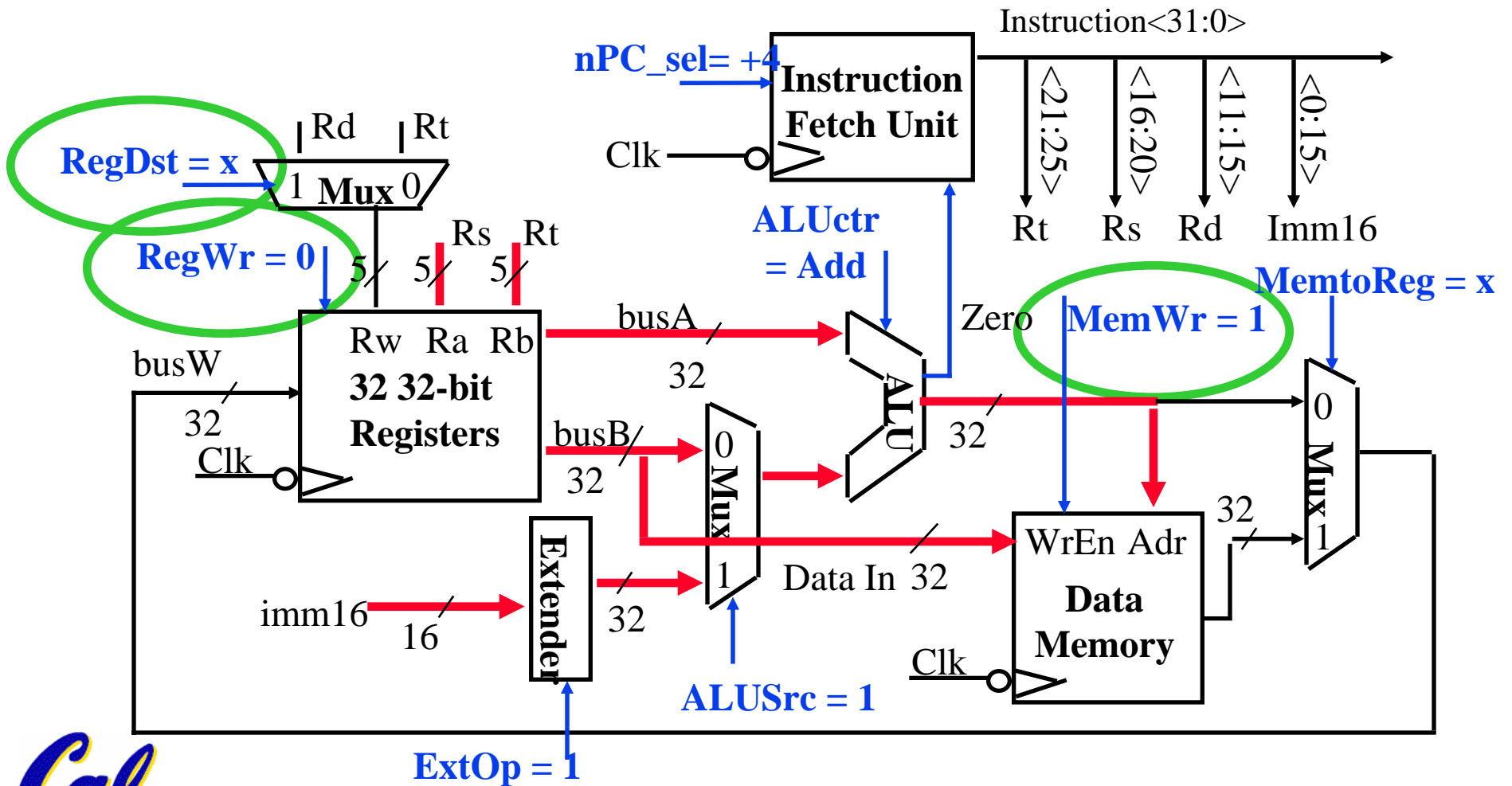
- Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




The Single Cycle Datapath during Branch?

 

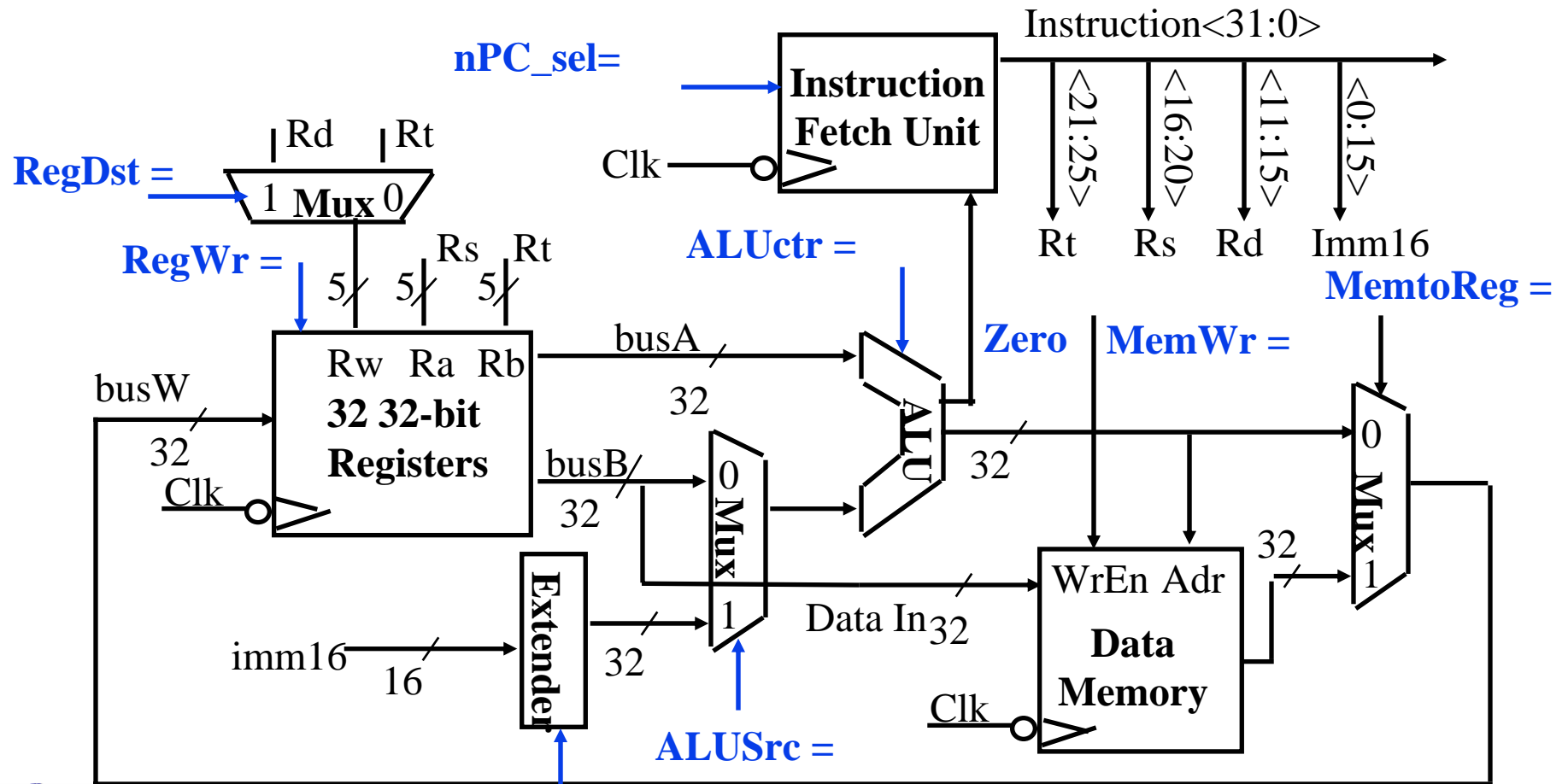
- if $(R[rs] - R[rt] == 0)$ then Zero = 1 ; else Zero = 0




The Single Cycle Datapath during Branch

 

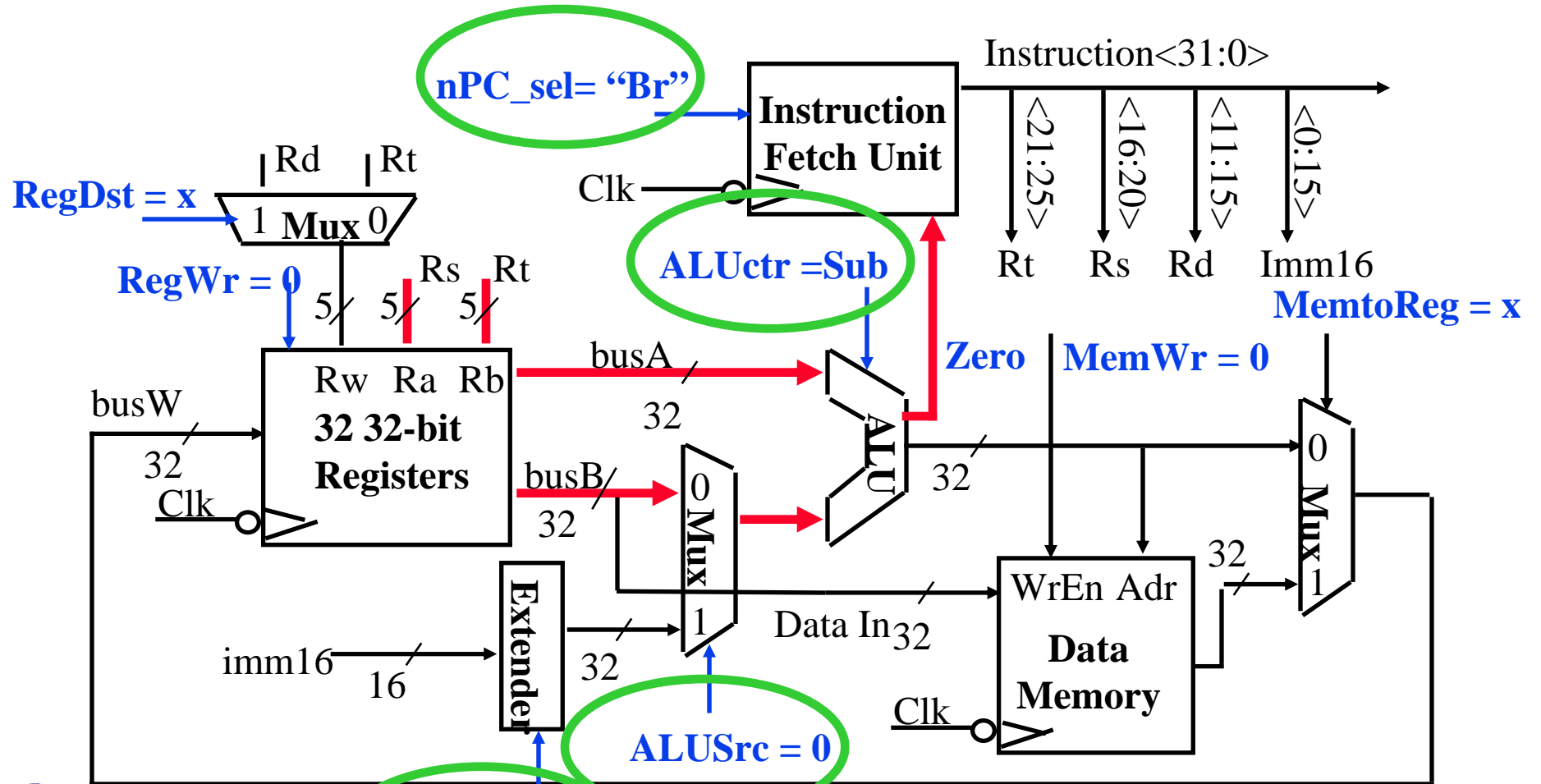
- if $(R[rs] - R[rt]) == 0$ then Zero = 1 ; else Zero = 0



 Instruction Fetch Unit at the End of Branch



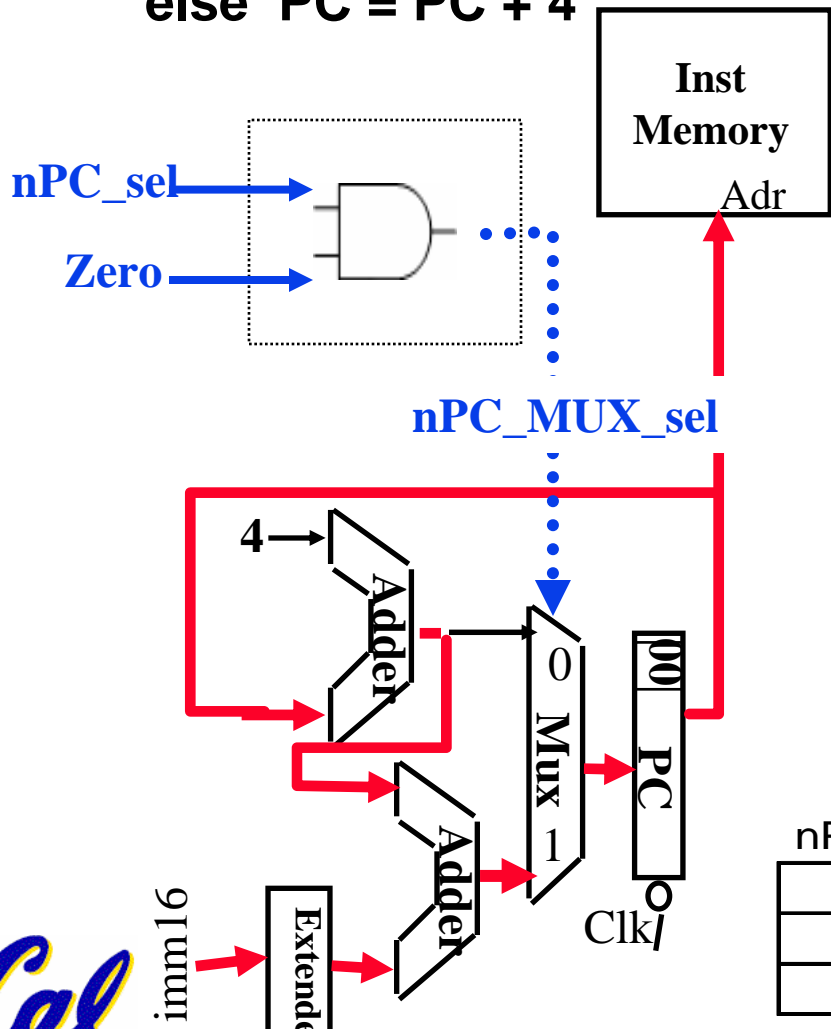- if (Zero == 1) then PC = PC + 4 + SignExt[imm16]*4 ;
 else PC = PC + 4



- What is encoding of nPC_MUX_sel?
 - Direct MUX select?
 - Branch / not branch
- Let's pick 2nd option


Q: What logic gate?



nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1



Step 4: Given Datapath: RTL -> Control

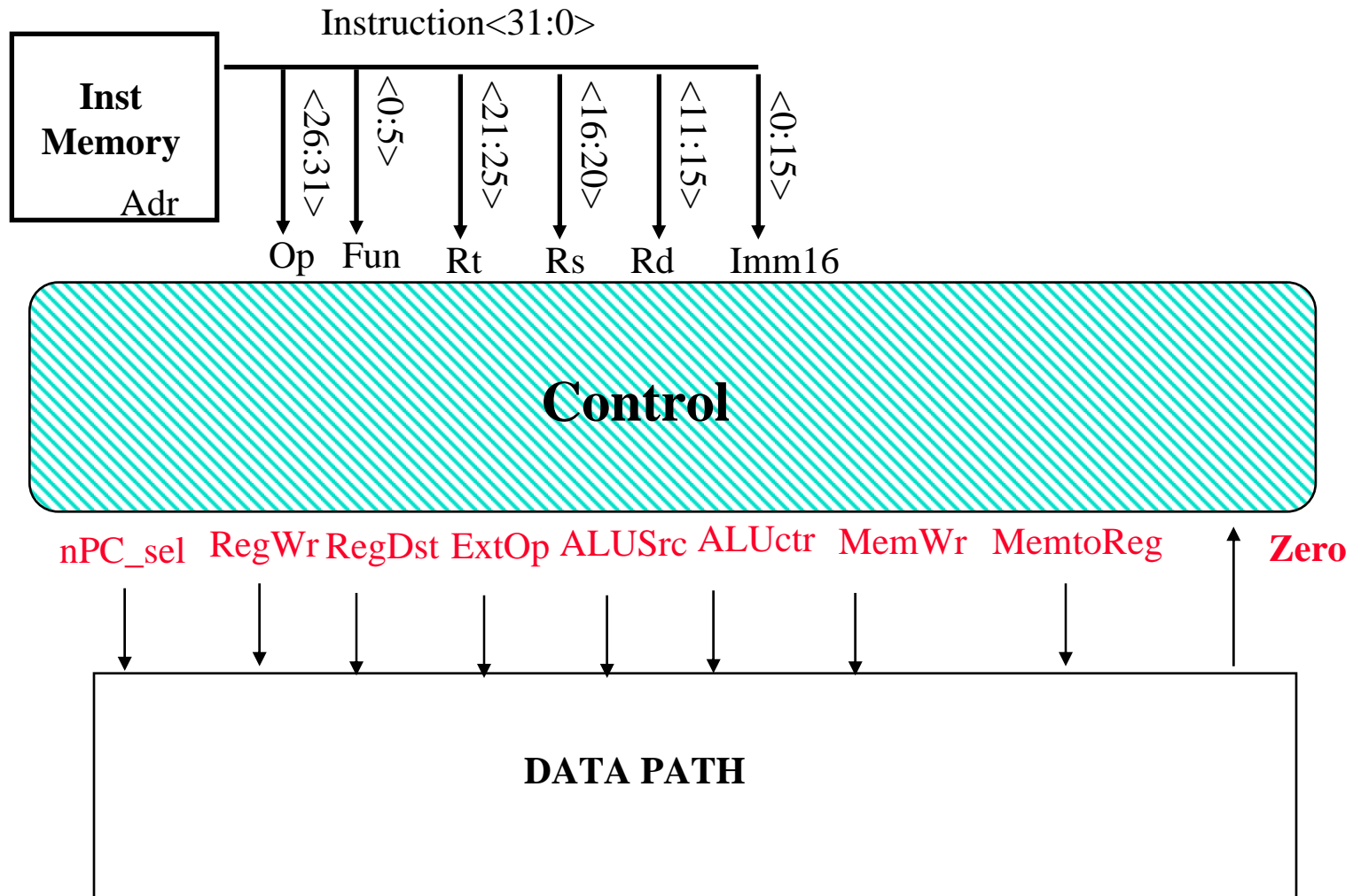

A Summary of the Control Signals (1/2)

inst Register Transfer

ADD $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"

SUB $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = "sub", RegDst = rd, RegWr, nPC_sel = "+4"

ORi $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16});$ $PC \leftarrow PC + 4$

ALUsrc = Im, Extop = "Z", ALUctr = "or", RegDst = rt, RegWr, nPC_sel = "+4"

LOAD $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = "Sn", ALUctr = "add",
MementoReg, RegDst = rt, RegWr, nPC_sel = "+4"**

STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$ $PC \leftarrow PC + 4$

ALUsrc = Im, Extop = "Sn", ALUctr = "add", MemWr, nPC_sel = "+4"

BEQ $\text{if } (R[rs] == R[rt]) \text{ then } PC \leftarrow PC + \text{sign_ext}(\text{Imm16}) \parallel 00 \text{ else } PC \leftarrow PC + 4$


nPC_sel = "Br", ALUctr = "sub"



A Summary of the Control Signals (2/2)

See Appendix A → **func**
 → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	0
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx

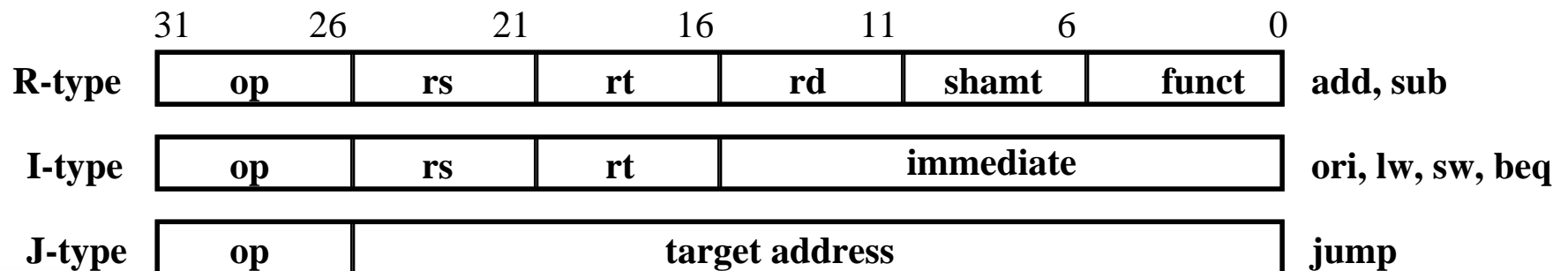


Administrivia

- **Final exam time/location set**
Tuesday, December 14th, 12:30 – 3:30 pm
At the Hearst Gym (lucky us!)



Review: Finite State Machine (FSM)

 - **States** represent possible output values.
- **Transitions** represent changes between states based on inputs.
- **Implement** with CL and clocked register feedback.



Finite State Machines extremely useful!

- They define
 - How **output signals** respond to input signals and previous state.
 - How we **change states** depending on input signals and previous state
- The output signals could be our familiar **control signals**
 - Some control signals **may only depend on CL, not on state at all...**
- We could implement very detailed FSMs w/**Programmable Logic Arrays**




Taking advantage of sum-of-products

- Since sum-of-products is a convenient notation and way to think about design, offer hardware building blocks that match that notation
- One example is **Programmable Logic Arrays (PLAs)**
- Designed so that can select (program) ands, ors, complements after you get the chip
 - Late in design process, fix errors, figure out what to do later, ...



Programmable Logic Arrays

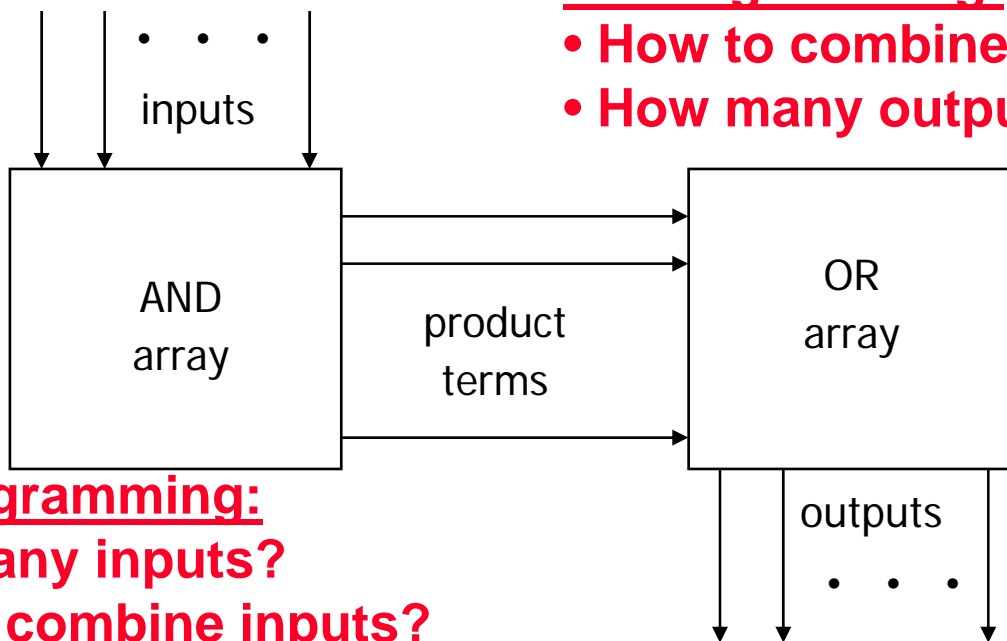- Pre-fabricated building block of many AND/OR gates
 - “Programmed” or “Personalized” by making or breaking connections among gates
- Programmable array block diagram for sum of products form



Or Programming:

- How to combine product terms?
- How many outputs?

And Programming:

- How many inputs?
- How to combine inputs?
- How many product terms?



Enabling Concept

• Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

input side: 3 inputs

1 = uncomplemented in term
 0 = complemented in term
 - = does not participate

personality matrix

Product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

output side: 4 outputs


1 = term connected to output
 0 = no connection to output

reuse of terms;
 5 product terms




Before Programming

 - All possible connections available before "programming"



After Programming

 - Unwanted connections are "blown"
 - Fuse (normally connected, break unwanted ones)
 - Anti-fuse (normally disconnected, make wanted connections)





Alternate Representation

- Short-hand notation--don't have to draw all the wires
- X Signifies a connection is present and perpendicular signal is an input to gate

notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

  


Other Programmable Logic Arrays

- There are other types of PLAs which can be reprogrammed on the fly
- The most common is called a **Field Programmable Gate Array (FPGA)**
- FPGAs are made up of configurable logic blocks (CLBs) and flip-flops which can be programmed by software
- Berkeley has on-going research into reconfigurable computing with FPGAs
 - Check out Brass and BEE2 projects



Peer Instruction

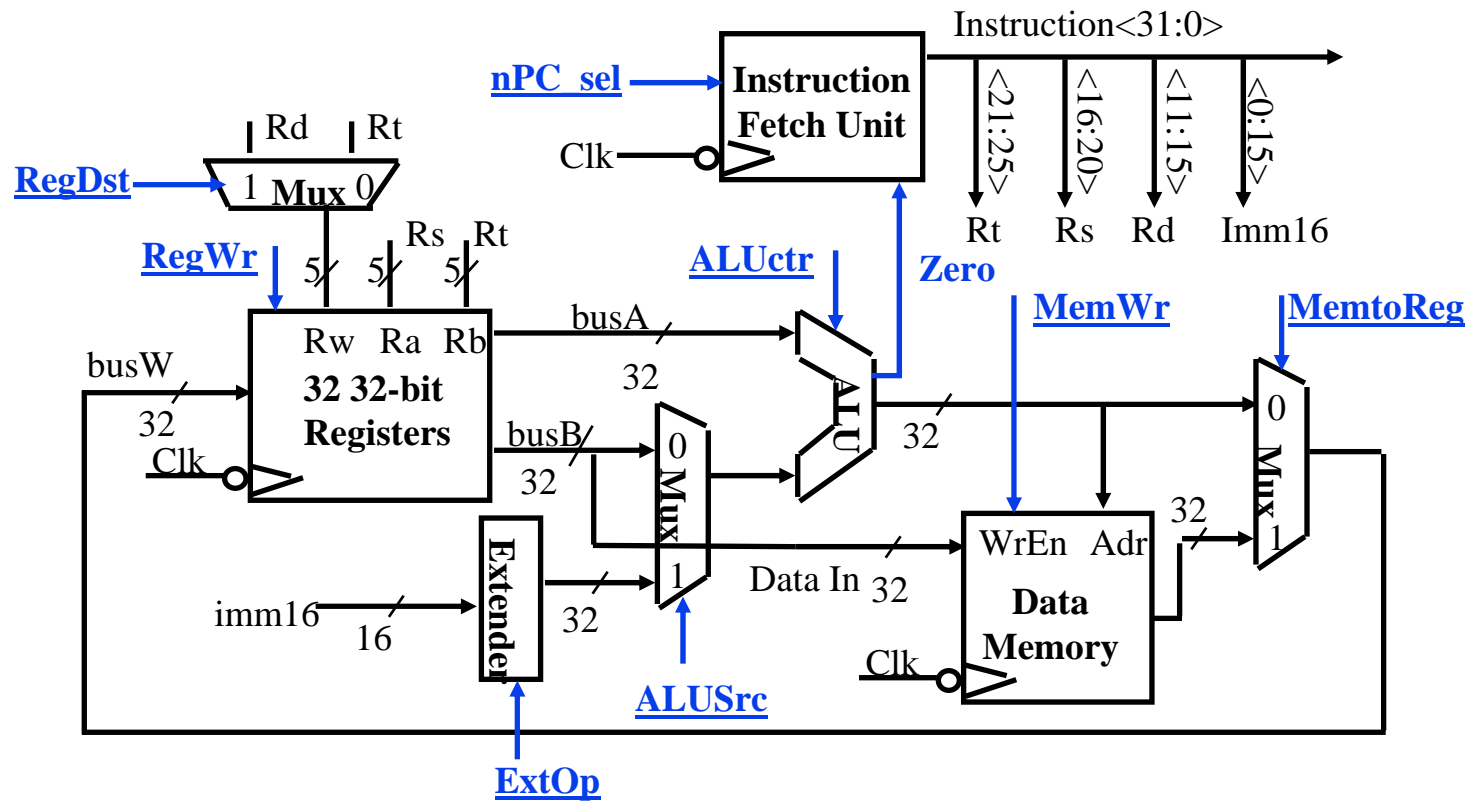

- A. MemToReg='x' & ALUctr='sub'. SUB or BEQ?
- B. ALUctr='add'. Which 1 signal is different for all 3 of: ADD, LW, & SW? RegDst or ExtOp?
- C. "Don't Care" signals are useful because we can simplify our PLA personality matrix. F / T?

	ABC
1:	S <u>R</u> F
2:	S <u>R</u> T
3:	S <u>E</u> F
4:	S <u>E</u> T
5:	<u>B</u> R <u>F</u>
6:	<u>B</u> R <u>T</u>
7:	<u>B</u> E <u>F</u>
8:	<u>B</u> E <u>T</u>



And in Conclusion... Single cycle control


◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

◦ **Control** is the hard part

◦ MIPS makes that easier

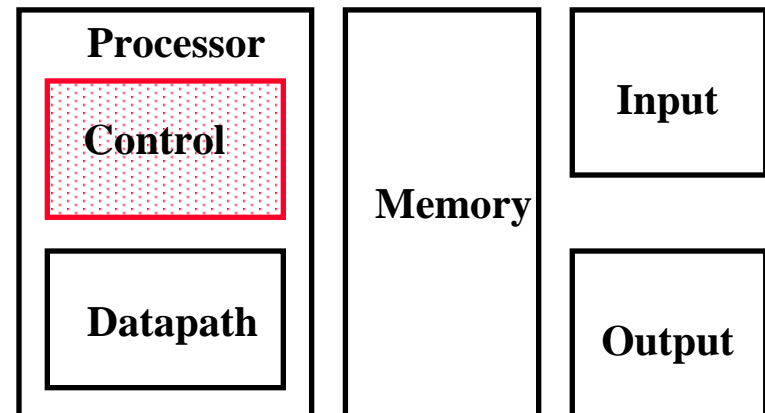- Instructions same size
- Source registers always in same place
- Immediates same size, location



Operations always on registers/immediates