

CS 61C: Great Ideas in Computer Architecture Single Cycle MIPS CPU—Part I

Instructors:
Krste Asanovic, Randy H. Katz
<http://inst.eecs.Berkeley.edu/~cs61c/fa12>

10/26/12 Fall 2012 – Lecture #25 1

You are Here!

Software

- Parallel Requests
Assigned to computer
e.g., Search "Katz"
- Parallel Threads
Assigned to core
e.g., Lookup, Ads
- Parallel Instructions
>1 instruction @ one time
e.g., 5 pipelined instructions
- Parallel Data
>1 data item @ one time
e.g., Add of 4 pairs of words
- Hardware descriptions
All gates @ one time
- Programming Languages

Hardware

Warehouse Scale Computer

Smart Phone

Harness Parallelism & Achieve High Performance

Computer

Core ... Core

Memory (Cache)

Input/Output

Core

Instruction Unit(s)

Functional Unit(s)

Cache Memory

Logic Gates

10/26/12 Fall 2012 – Lecture #25 2

Levels of Representation/ Interpretation

High Level Language Program (e.g., C)

↓ Compiler

Assembly Language Program (e.g., MIPS)

↓ Assembler

Machine Language Program (MIPS)

```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;

lw $t0, 0($2)
lw $t1, 4($2)
sw $t1, 0($2)
sw $t0, 4($2)
```

Anything can be represented as a number, i.e., data or instructions

```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```

Machine Interpretation

Hardware Architecture Description (e.g., block diagrams)

Architecture Implementation

Logic Circuit Description (Circuit Schematic Diagrams)

10/26/12 Fall 2012 – Lecture #25 3

Review

- Hardware systems made from *Stateless* Combinational Logic and *Stateful* "Memory" Logic (Registers)
- Clocks tell us when D-flip-flops change
 - Setup and Hold times important
- We pipeline long-delay CL for faster clock cycle
 - Split up the *critical path*
- Finite State Machines extremely useful
- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Can implement muxes hierarchically
- Can implement FSM with register + logic

10/26/12 Fall 2012 – Lecture #18 4

Agenda

- MIPS-lite Datapath
- Administrivia
- CPU Timing
- MIPS-lite Control

10/26/12 Fall 2012 – Lecture #25 5

Agenda

- MIPS-lite Datapath
- Administrivia
- CPU Timing
- MIPS-lite Control

10/26/12 Fall 2012 – Lecture #25 6

Processor Design Process

- Five steps to design a processor:
 - Analyze instruction set → datapath requirements
 - Select set of datapath components & establish clock methodology
 - Assemble datapath meeting the requirements
 - Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

10/26/12 Fall 2012 – Lecture #25 7

The MIPS-lite Subset

- ADDU and SUBU

31	26	21	16	11	6	0
op	rs	rt	rd	shamt	funct	
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	
- OR Immediate:

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	
- LOAD and STORE Word

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	
- BRANCH:

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	

10/26/12 Fall 2012 – Lecture #25 8

Register Transfer Language (RTL)

- RTL gives the meaning of the instructions


```
{op, rs, rt, rd, shamt, funct} ← MEM[ PC ]
{op, rs, rt, Imm16} ← MEM[ PC ]
```
- All start by fetching the instruction

Inst Register Transfers

```
ADDU R[rd] ← R[rs] + R[rt]; PC ← PC + 4
SUBU R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ORI R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
LOAD R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
STORE MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
BEQ if ( R[rs] == R[rt] )
    then PC ← PC + 4 + (sign_ext(Imm16) || 00)
    else PC ← PC + 4
```

10/26/12 Fall 2012 – Lecture #25 9

Step 1: Requirements of the Instruction Set

- Memory (MEM)
 - Instructions & data (will use one for each: really caches)
- Registers (R: 32 x 32)
 - Read *rs*
 - Read *rt*
 - Write *rt* or *rd*
- PC
- Extender (sign/zero extend)
- Add/Sub/OR unit for operation on register(s) or extended immediate
- Add 4 (+ maybe extended immediate) to PC
- Compare if registers equal?

10/26/12 Fall 2012 – Lecture #25 10

Generic Steps of Datapath

- Instruction Fetch
- Decode/ Register Read
- Execute
- Memory
- Register Write

10/26/12 Fall 2012 – Lecture #25 11

Step 2: Components of the Datapath

- Combinational Elements
- State Elements + Clocking Methodology
- Building Blocks

10/26/12 Fall 2012 – Lecture #25 12

ALU Needs for MIPS-lite + Rest of MIPS


- Addition, subtraction, logical OR, ==:


```

            ADDU R[rd] = R[rs] + R[rt]; ...
            SUBU R[rd] = R[rs] - R[rt]; ...
            ORI R[rt] = R[rs] | zero_ext(Imm16) ...
            BEQ if ( R[rs] == R[rt] ) ...
            
```
- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if A < B, 0 otherwise)
- ALU from Appendix C, section C.5

10/26/12 Fall 2012 - Lecture #25 13


Storage Element: Idealized Memory

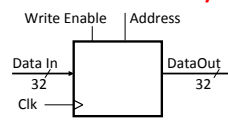

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is found by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block: Address valid ⇒ Data Out valid after “access time”

10/26/12 Fall 2012 - Lecture #25 14

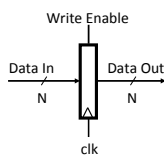
Storage Element: Register (Building Block)



- Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - Negated (or deasserted) (0): Data Out will not change
 - Asserted (1): Data Out will become Data In on rising edge of clock

10/26/12 Fall 2012 - Lecture #25 15

Storage Element: Register File

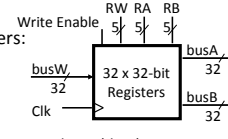


- Register File consists of 32 registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
 - Clk input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid ⇒ busA or busB valid after “access time.”

10/26/12 Fall 2012 - Lecture #25 16

Step 3: Assemble DataPath Meeting Requirements

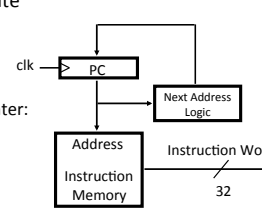
- Register Transfer Requirements ⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
 - Fetch the Instruction: mem[PC]
 - Update the program counter:
 - Sequential Code: PC ← PC + 4
 - Branch and Jump: PC ← “something else”



10/26/12 Fall 2012 - Lecture #25 17

Step 3: Add & Subtract

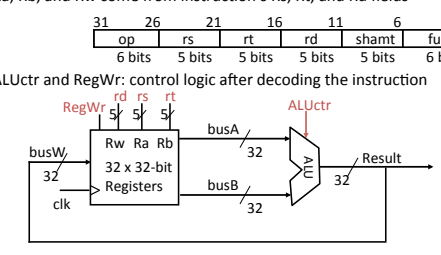- $R[rd] = R[rs] \text{ op } R[rt]$ (addu rd, rs, rt)
 - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields



10/26/12 Fall 2012 - Lecture #25 18

Agenda

- MIPS-lite Datapath
- Administrivia
- CPU Timing
- MIPS-lite Control

10/26/12

Fall 2012 -- Lecture #25

19

Who is in CS61c? Surprisingly Diverse Set of Majors

• Applied Math	6	• Film	1
• Architecture	1	• IEOR	2
• Bioengineering	6	• Japanese	2
• Business Admin	9	• Legal Studies	1
• Chemical Eng	1	• Linguistics	1
• Chemistry	2	• Mathematics	4
• Civil Eng	1	• Mechanical Eng	4
• Cognitive Sci	11	• OR & Mgt Sci	1
• Computer Science	3	• Physics	2
• Double	11	• Political Econ	1
• Economics	6	• Political Sci	2
• ECS & Mat Sci	2	• Statistics	3
• Elec Engr Comp Sci	227	• Triple	1
• Elec Engr Physics	1	• Undecl Eng	5
• Engr-Mat Sci	1	• Undecl	149

Fall 2012 enrollment > 2 x Fall 2011 enrollment!

10/26/12

Fall 2012 -- Lecture #25

20

Agenda


- MIPS-lite Datapath
- Administrivia
- CPU Timing
- MIPS-lite Control

10/26/12

Fall 2012 -- Lecture #25

21

Clocking Methodology

 


- Storage elements clocked by same edge
- "Critical path" (longest path through logic) determines length of clock period
- Have to allow for Clock-to-Q and Setup Times too
- This lecture (and P&H sections) 4.3-4.4 do whole instruction in 1 clock cycle for pedagogic reasons
 - Project 4 will do it in 2 clock cycles via simple pipelining
 - Soon explain pipelining and use 5 clock cycles per instruction

10/26/12

Fall 2012 -- Lecture #25

22

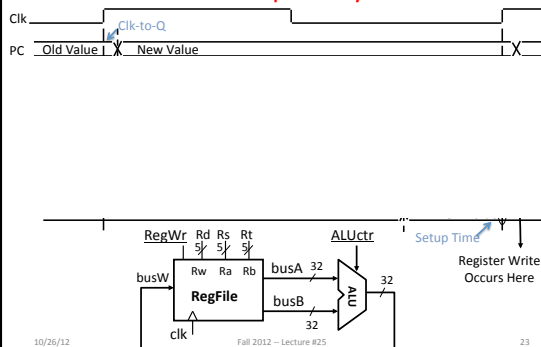Register-Register Timing: One Complete Cycle




10/26/12

Fall 2012 -- Lecture #25

23

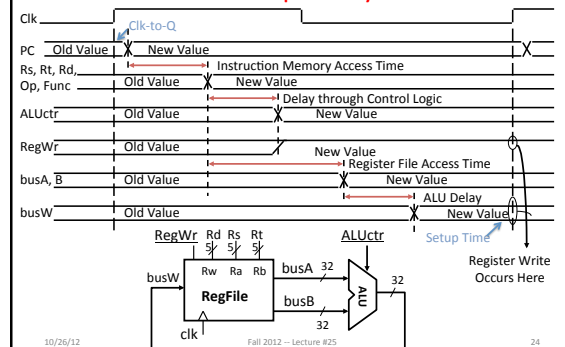Register-Register Timing: One Complete Cycle



10/26/12

Fall 2012 -- Lecture #25

24

Agenda

- MIPS-lite Datapath
- Administrivia
- CPU Timing
- MIPS-lite Control


10/26/12

Fall 2012 -- Lecture #25


25

Logical Operations with Immediate

 - $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



 But we're writing to Rt register??
And immediate ALU input??




10/26/12

Fall 2012 -- Lecture #25

26

Logical Operations with Immediate

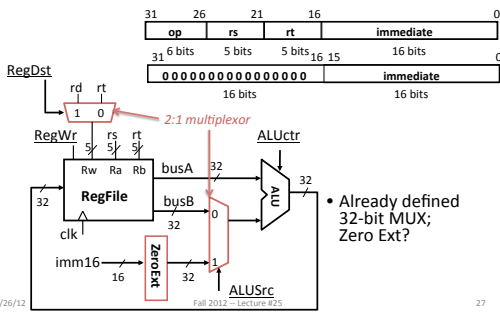- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$




10/26/12

Fall 2012 -- Lecture #25


27

Load Operations

 - $R[rt] = \text{Mem}[R[rs] + \text{SignExt}[imm16]]$
- Example: `lw rt, rs, imm16`



What sign extending??
And where is Mem??

 


10/26/12

Fall 2012 -- Lecture #25

28

Load Operations

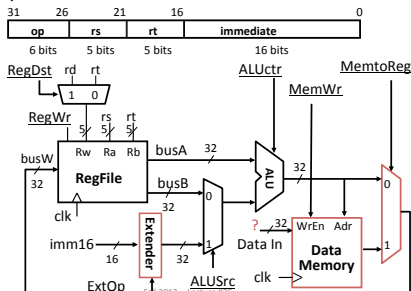- $R[rt] = \text{Mem}[R[rs] + \text{SignExt}[imm16]]$
- Example: `lw rt, rs, imm16`



10/26/12


Fall 2011 -- Lecture #25

29

And in Conclusion, ... Single-Cycle Processor

- Five steps to design a processor:

 1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - Formulate Logic Equations
 - Design Circuits
5. Assemble the control logic



10/26/12

Fall 2011 -- Lecture #25

30