

## CS 61C: Great Ideas in Computer Architecture *Single Cycle MIPS CPU—Part II*

Instructors:  
Krste Asanovic, Randy H. Katz  
<http://inst.eecs.Berkeley.edu/~cs61c/fa12>

10/25/12 Fall 2012 – Lecture #26 1

## You are Here!

**Software**

- Parallel Requests  
Assigned to computer  
e.g., Search "Katz"
- Parallel Threads  
Assigned to core  
e.g., Lookup, Ads
- Parallel Instructions  
>1 instruction @ one time  
e.g., 5 pipelined instructions
- Parallel Data  
>1 data item @ one time  
e.g., Add of 4 pairs of words
- Hardware descriptions  
All gates @ one time
- Programming Languages

**Hardware**

Warehouse Scale Computer

Smart Phone

Harness Parallelism & Achieve High Performance

Computer

Core ... Core

Memory (Cache)

Input/Output

Core

Instruction Unit(s)

Functional Unit(s)

Cache Memory

Logic Gates

10/25/12 Fall 2012 – Lecture #26 2

## Levels of Representation/ Interpretation

High Level Language Program (e.g., C)

Compiler

Assembly Language Program (e.g., MIPS)

Assembler

Machine Language Program (MIPS)

Machine Interpretation

Hardware Architecture Description (e.g., block diagrams)

Architecture Implementation

Logic Circuit Description (Circuit Schematic Diagrams)

```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;

lw  $t0, 0($2)
lw  $t1, 4($2)
sw  $t1, 0($2)
sw  $t0, 4($2)
```

Anything can be represented as a number, i.e., data or instructions

```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```

10/25/12 Fall 2012 – Lecture #26 3

## Processor Design Process

- Five steps to design a processor:
  - Analyze instruction set → datapath requirements
  - Select set of datapath components & establish clock methodology
  - Assemble datapath meeting the requirements
  - Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - Assemble the control logic
    - Formulate Logic Equations
    - Design Circuits

10/25/12 Fall 2012 – Lecture #26 4

## Agenda

- Datapath Control
- Administrivia
- Control Implementation

10/25/12 Fall 2012 – Lecture #26 5

## Agenda

- Datapath Control
- Administrivia
- Control Implementation

10/25/12 Fall 2012 – Lecture #26 6

### The MIPS-lite Subset

- ADDU and SUBU
 

31	26	21	16	11	6	0
op	rs	rt	rd	shamt	funct	
6 bits		5 bits		5 bits		6 bits

 - addu rd,rs,rt  
 - subu rd,rs,rt
- OR Immediate:
 

31	26	21	16	0
op	rs	rt	immediate	
6 bits		5 bits		16 bits

 - ori rt,rs,imm16
- LOAD and STORE Word
 

31	26	21	16	0
op	rs	rt	immediate	
6 bits		5 bits		16 bits

 - lw rt,rs,imm16  
 - sw rt,rs,imm16
- BRANCH:
 

31	26	21	16	0
op	rs	rt	immediate	
6 bits		5 bits		16 bits

 - beq rs,rt,imm16


### Register Transfer Language (RTL)

- RTL gives the meaning of the instructions
 

```
{op, rs, rt, rd, shamt, funct} ← MEM[ PC ]
{op, rs, rt, Imm16} ← MEM[ PC ]
```
- All start by fetching the instruction
 Inst Register Transfers


```
ADDU R[rd] ← R[rs] + R[rt]; PC ← PC + 4
SUBU R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ORI R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
LOAD R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
STORE MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
BEQ if ( R[rs] == R[rt] )
    then PC ← PC + 4 + (sign_ext(Imm16) || 00)
    else PC ← PC + 4
```

### RTL: The Add Instruction

 


- add rd, rs, rt
- MEM[PC] Fetch the instruction from memory
  - R[rd] = R[rs] + R[rt] The actual operation
  - PC = PC + 4 Calculate the next instruction's address

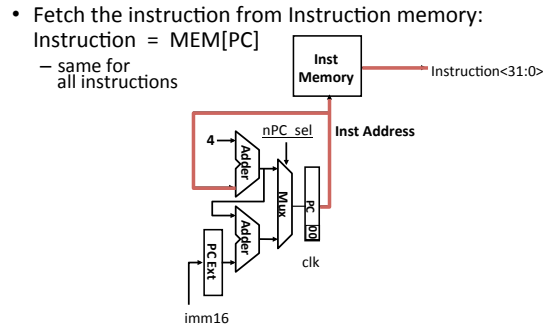
### Instruction Fetch Unit at the Beginning of Add













### Single Cycle Datapath during Add

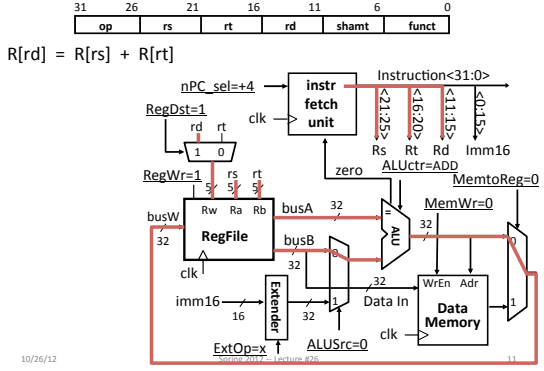

### Instruction Fetch Unit at End of Add

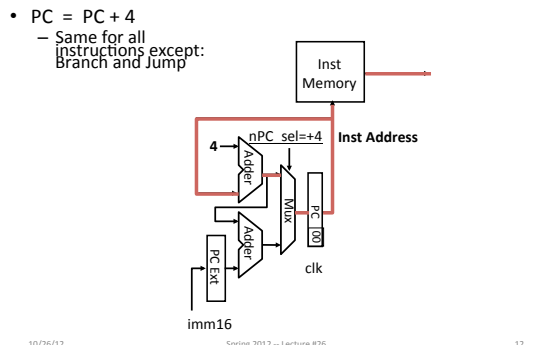

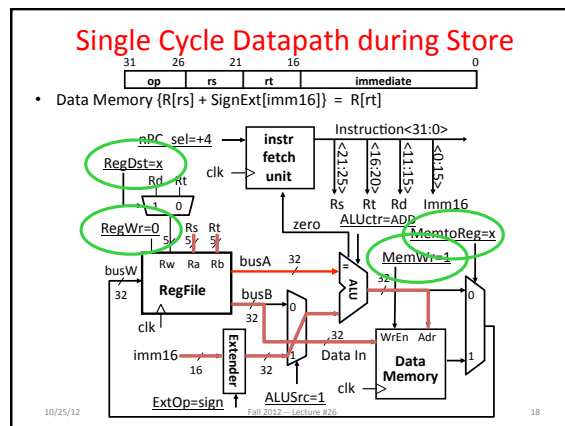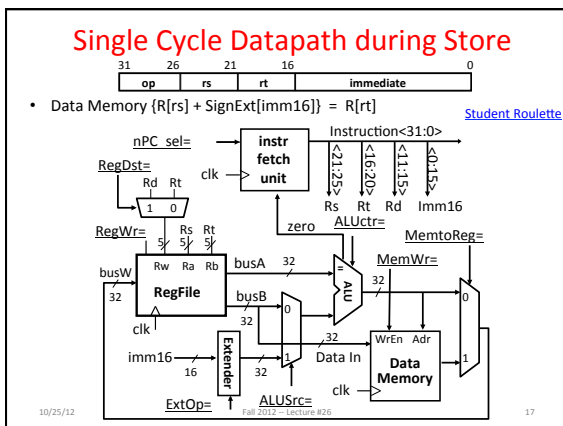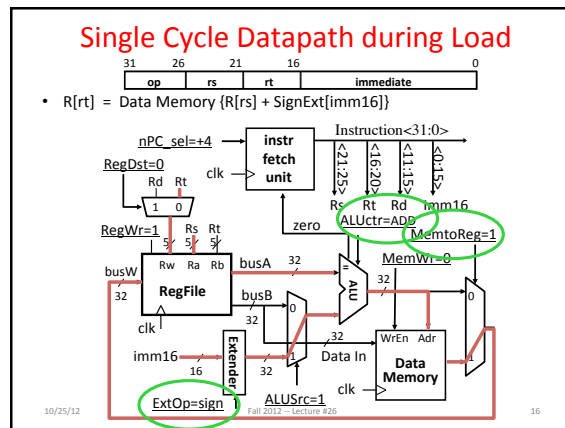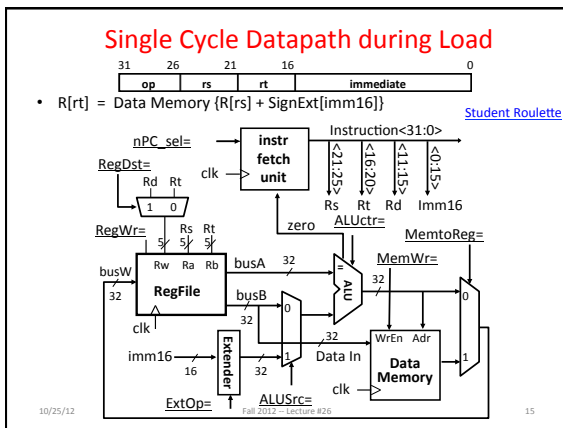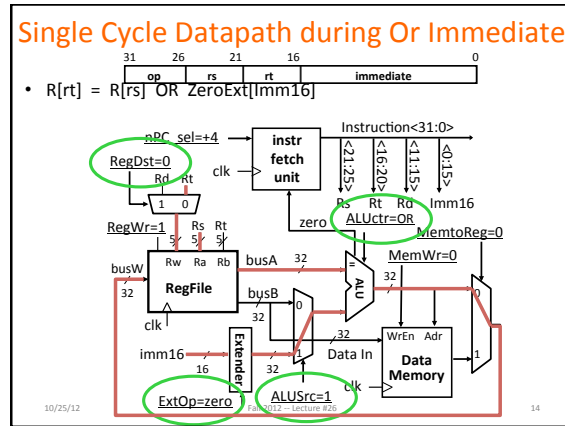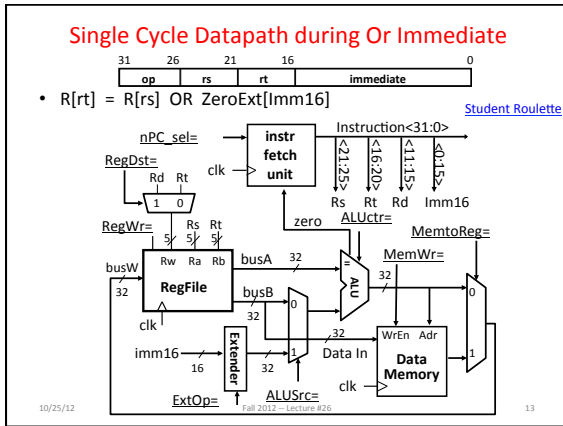

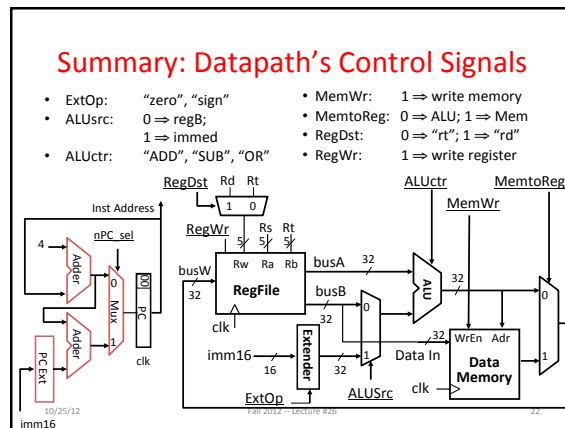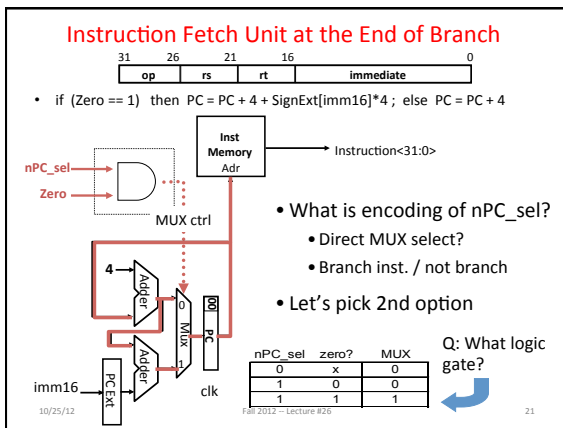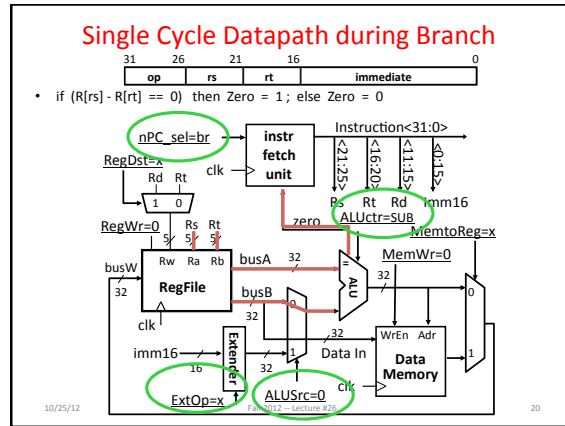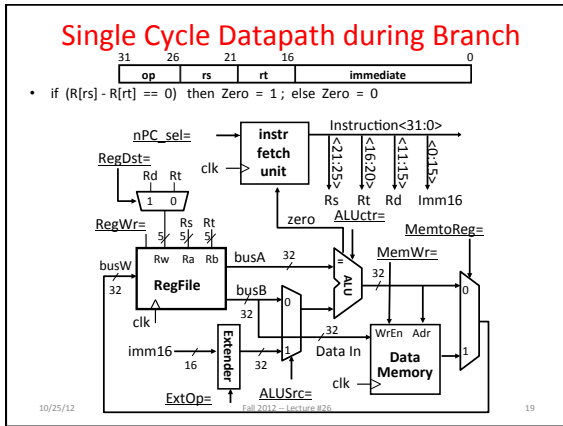

- ### Agenda
- Datapath Control
  - Administrivia
  - Control Implementation
- 10/25/12 Fall 2012 - Lecture #26 23

### Sleek Tablet, but Clumsy Software

OCTOBER 24, 2012, 7:04 AM | 3 Comments

## Move to the Cloud in the Least Expensive iPad Mini

### The iPad Mini and Its Competition

The iPad Mini was announced Tuesday, with a retail price starting at \$329. How it compares with other small tablet models currently available:

Related Article >

IPAD MINI	KINDLE FIRE HD	GALAXY TAB 2 (7.0)	NEXUS 7	NOOK HD
MAKER: Apple	Amazon	Samsung	Google	Barnes & Noble
RETAIL PRICE: \$329 to \$559	\$199 to \$249	\$200	\$199 to \$249	\$199 to \$229
DIMENSIONS: 7.9" x 5.3" x 0.3"	7.6" x 5.4" x 0.4"	7.6" x 4.8" x 0.4"	7.6" x 4.7" x 0.4"	7.7" x 5.0" x 0.4"
RESOLUTION: 1024 x 768	1280 x 800	1024 x 800	1280 x 800	1440 x 900
WEIGHT: 11 ounces	14 ounces	12 ounces	12 ounces	11 ounces
MEMORY: 16, 32 or 64 GB	16 or 32 GB	8 GB	8 or 16 GB	8 or 16 GB

10/26/12 Illustration by The New York Times

OCTOBER 22, 2012, 3:56 PM | 24 Comments

## Amazon Cloud Service Goes Down and Takes Popular Sites With It

By NICOLE PERLROTH

**7:11 p.m. | Updated Updated throughout.**

Some services at Amazon.com's data centers went down Monday afternoon, taking with them a number of popular Web sites and services, including Flipboard and Foursquare.

Amazon **reported problems** at data centers in Northern Virginia that appeared to have had a ripple effect across the Internet, as many companies depend on the company's cloud service to run their businesses. Several frustrated customers took to Twitter to complain.

In June, an electrical storm caused problems at the same Northern Virginia data centers and **took down sites including Netflix, Pinterest and Instagram for a weekend.**

The companies that were affected by the latest shutdown scrambled to respond.

"Like many other services, we've been taken down by the outage," said Erin Gleason, a spokeswoman for Foursquare, the mobile check-in service. "Both the site and the app are inaccessible right now."


Ms. Gleason said the company was still awaiting information from Amazon about when its service might be restored.

10/26 25

## Agenda

- Datapath Control
- Administrivia
- Control Implementation

10/25/12 Fall 2012 -- Lecture #26 26

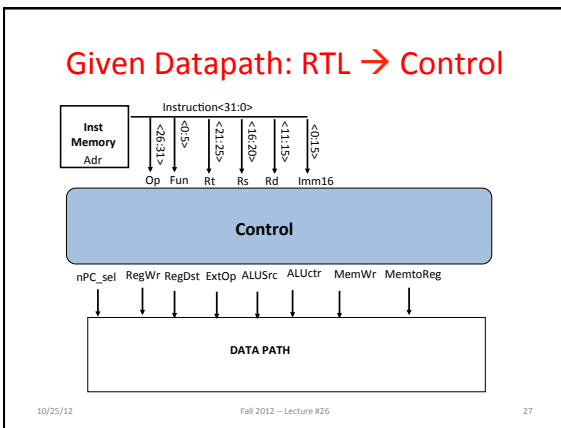

### Summary of the Control Signals (1/2)

```

inst Register Transfer
add R[rd] ← R[rs] + R[rt]; PC ← PC + 4
   ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"
sub R[rd] ← R[rs] - R[rt]; PC ← PC + 4
   ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"
ori R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4
   ALUSrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"
lw  R[rt] ← MEM[ R[rs] + sign_ext(Imm16)]; PC ← PC + 4
   ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
   nPC_sel = "+4"
sw  MEM[ R[rs] + sign_ext(Imm16)] ← R[rs]; PC ← PC + 4
   ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"
beq if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) || 00
   else PC ← PC + 4
   nPC_sel = "br", ALUctr = "SUB"
    
```

10/25/12 Fall 2012 -- Lecture #26 28

### Summary of the Control Signals (2/2)

See Appendix A → func

	10 0000	10 0010	We Don't Care :-)			
op	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100
	add	sub	ori	lw	sw	beq
RegDst	1	1	0	0	x	x
ALUSrc	0	0	1	1	1	0
MemtoReg	0	0	0	1	x	x
RegWrite	1	1	1	1	0	0
MemWrite	0	0	0	0	1	0
nPCsel	0	0	0	0	0	1
Jump	0	0	0	0	0	0
ExtOp	x	x	0	1	1	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract

R-type: 31 26 21 16 11 6 0  
 op rs rt rd shamt funct add, sub

I-type: 31 26 21 16 11 6 0  
 op rs rt immediate ori, lw, sw, beq

10/25/12 Fall 2012 -- Lecture #26 29

### Boolean Expressions for Controller

```

RegDst = add + sub
ALUSrc = ori + lw + sw
MemtoReg = lw
RegWrite = add + sub + ori + lw
MemWrite = sw
nPCsel = beq
Jump = jump
ExtOp = lw + sw
ALUctr[0] = sub + beq (assume ALUctr is 00 ADD, 01: SUB, 10: OR)
ALUctr[1] = or
    
```

Where:

```




rtype = ~op3 * ~op4 * ~op5 * ~op6 * ~op7 * ~op8
ori = ~op3 * ~op4 * op5 * op6 * ~op7 * op8
lw = op3 * ~op4 * ~op5 * ~op6 * op7 * op8
sw = op3 * ~op4 * op5 * ~op6 * op7 * op8
beq = ~op3 * ~op4 * ~op5 * op6 * ~op7 * ~op8
jump = ~op3 * ~op4 * ~op5 * ~op6 * op7 * ~op8
    
```

How do we implement this in gates?

```

add = rtype * func5 * ~func4 * ~func3 * ~func2 * ~func1 * ~func0
sub = rtype * func5 * ~func4 * ~func3 * ~func2 * func1 * ~func0
    
```

10/25/12 Fall 2012 -- Lecture #26 30

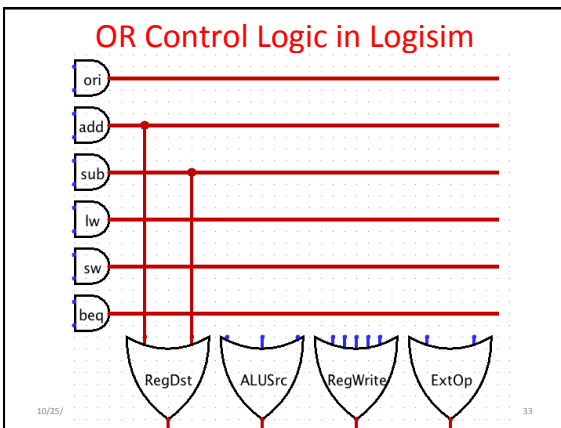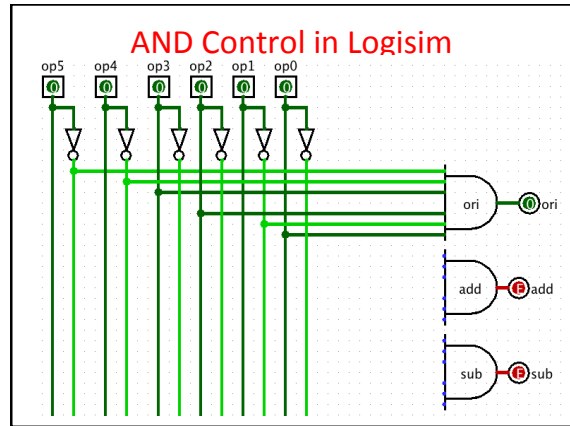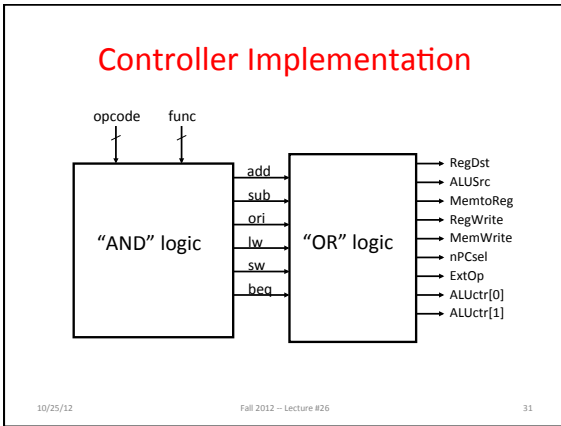

### Single Cycle Performance

- Assume time for actions are
  - 100ps for register read or write; 200ps for other events
- Clock rate is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- What can we do to improve clock rate?
- Will this improve performance as well?  
Want increased clock rate to mean faster programs

10/25/12 Fall 2012 -- Lecture #26 Student Roulette? 34

### And in Conclusion, ... Single-Cycle Processor

- Five steps to design a processor:
  - Analyze instruction set → datapath requirements
  - Select set of datapath components & establish clock methodology
  - Assemble datapath meeting the requirements
  - Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - Assemble the control logic
    - Formulate Logic Equations
    - Design Circuits

10/25/12 Fall 2012 -- Lecture #26 35