

inst.eecs.berkeley.edu/~cs61c
CS61C : Machine Structures

Lecture 20 – Introduction to Synchronous Digital Systems



Lecturer PSOE Dan Garcia


www.cs.berkeley.edu/~ddgarcia

NY Public Library ⇒

They've digitized their collection and put 275,000 images online! Manuscripts, historical maps, vintage posters, rare prints & photos, illustrated books & more!



What are “Machine Structures”?

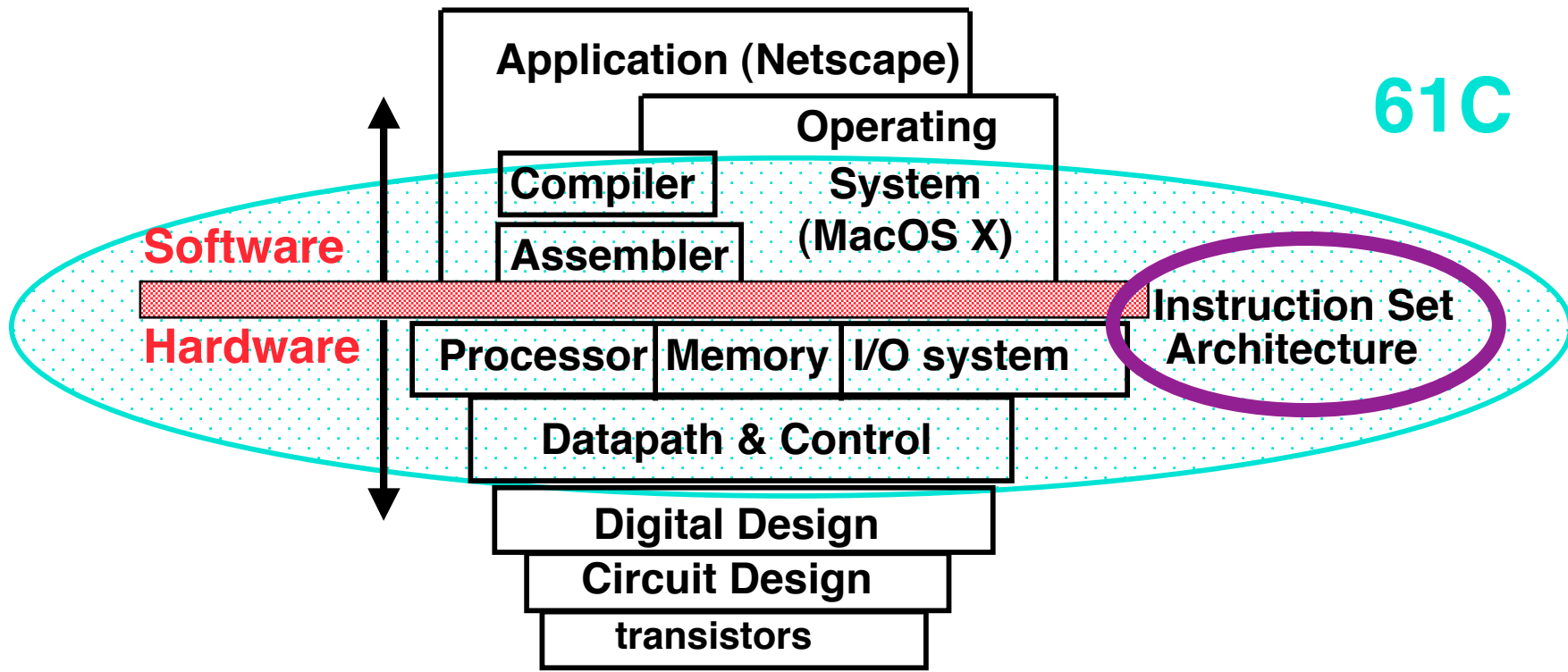

Coordination of many *levels of abstraction*


We'll investigate lower abstraction layers!
(contract between HW & SW)



Below the Program


- High-level language program (in C)
 
```
swap int v[], int k){
    int temp;
    temp = v[k];
    v[k] = v[k+1];
    v[k+1] = temp;
}
```




- Assembly language program (for MIPS)
 
```
swap: sll    $2, $5, 2
      add    $2, $4, $2
      lw     $15, 0($2)
      lw     $16, 4($2)
      sw     $16, 0($2)
      sw     $15, 4($2)
      jr     $31
```



- Machine (object) code (for MIPS)
 
```
000000 00000 00101 00010000010000000
000000 00100 00010 00010000000100000 . . .
```



Logic Design

- **Next 2 weeks: we'll study how a modern processor is built starting with basic logic elements as building blocks.**
- **Why study logic design?**
 - **Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)**
 - **Background for more detailed hardware courses (CS 150, CS 152)**




Logic Gates

- **Basic building blocks are logic *gates*.**
 - In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
 - Can build gates with transistors and resistors
- **Then found theoretical basis for design**
 - Can represent and reason about gates with truth tables and Boolean algebra
 - Assume know truth tables and Boolean algebra from a math or circuits course.
 - Section B.2 in the textbook has a review




Physical Hardware

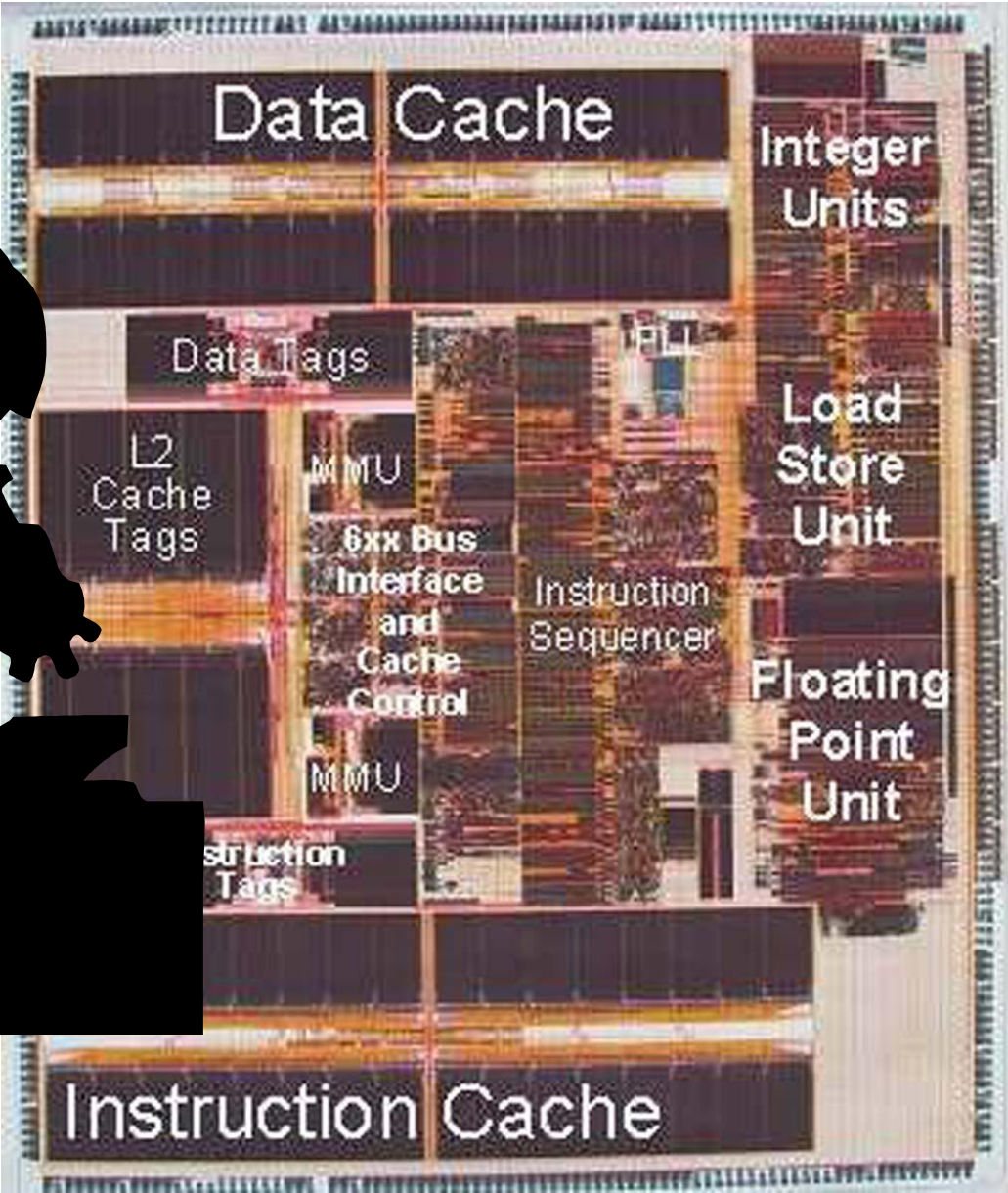


Let's look closer...



Gate-level view vs. Block diagram

 


≡


 


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Signals and Waveforms: Clocks

 


Signals and Waveforms: Adders

  

Signals and Waveforms: Grouping

x_3 x_2 x_1 x_0
↓ ↓ ↓ ↓


 


Signals and Waveforms: Circuit Delay



$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

  


Combinational Logic

- **Complex logic blocks are built from basic AND, OR, NOT building blocks we'll see shortly.**
- **A *combinational* logic block is one in which the output is a function only of its current input.**
- **Combinational logic **cannot have memory** (e.g., a register is not a combinational unit).**



Circuits with STATE (e.g., register)

 

Administrivia

- **Midterm tonight @ 7pm in 1 Le Conte.
Heard this enough yet?**



Peer Instruction

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



And in conclusion...

- **ISA is very important abstraction layer**
 - **Contract between HW and SW**
- **Basic building blocks are logic *gates***
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types**
 - **Stateless Combinational Logic (&,!,~)**
 - **State circuits (e.g., registers)**

