

**Lecture 21 –
 State Elements: Circuits That Remember**



Lecturer PSOE Dan Garcia
www.cs.berkeley.edu/~ddgarcia

CPU, GPU, now PPU! ⇒
 Ageia's "PhysX" chip will
 accelerate physics common to video
 games: rigid, soft body & fluid
 dynamics, collision detection, finite
 element analysis, hair & clothing sim!
www.ageia.com/technology.html



**The First 30 Years of Berkeley CS
 3/10 Thursday, 6-7pm 306 Soda**



Prof Richard Karp
 Turing Award Winner, Distinguished Teacher

**A personal perspective on the
 history of the Computer Science
 Division, including the personalities
 and politics behind its formation, its
 greatest achievements, and its
 prospects for the future.**




Review...

- ISA is very important abstraction layer
 - Contract between HW and SW
- Basic building blocks are logic *gates*
- Clocks control pulse of our circuits
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types
 - Stateless Combinational Logic (&,!,~), in which **output is function of input only**
 - State circuits (e.g., registers)




Accumulator Example

 

Want: `S=0;`
`for (i=0; i<n; i++)`
`S = S + Xi`




First try...Does this work?

 


Nope!
Reason #1... What is there to control the next iteration of the 'for' loop?
Reason #2... How do we say: 's=0'?




Second try...How about this? Yep!

 

Rough timing...

 

Register Details... What's in it anyway?

 


- n instances of a "Flip-Flop", called that because the output flips and flops betw. 0,1
- D is "data"
- Q is "output"
- Also called "d-q Flip-Flop", "d-type Flip-Flop"



CS61C L21 State Elements: Circuits That Remember (7)

Garcia © UCB

What's the timing of a Flip-flop? (1/2)

 


- Edge-triggered d-type flip-flop
 - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."



CS61C L21 State Elements: Circuits That Remember (8)

Garcia © UCB

What's the timing of a Flip-flop? (2/2)

 

- Edge-triggered d-type flip-flop
 - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."




CS61C L21 State Elements: Circuits That Remember (9)

Garcia © UCB

Administrivia - Midterm

- Your TAs and readers stayed up until 6:30am to get your exams back to you!
- \bar{x} : 47, Median: 48, σ : 14.4


 
UCB CS61C 2005Sp Midterm
mean=47, median=48, stdev=14



CS61C L

Garcia © UCB

 
 
Accumulator Revisited (proper timing 1/2)



CS61C L21 State Elements: Circuits That Remember (11)

Garcia © UCB

  
Accumulator Revisited (proper timing 2/2)




CS61C L21 State Elements: Circuits That Remember (12)

Garcia © UCB


Pipelining to improve performance (1/2)

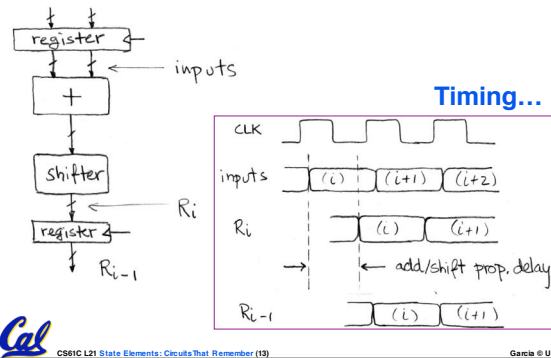


Pipelining to improve performance (2/2)

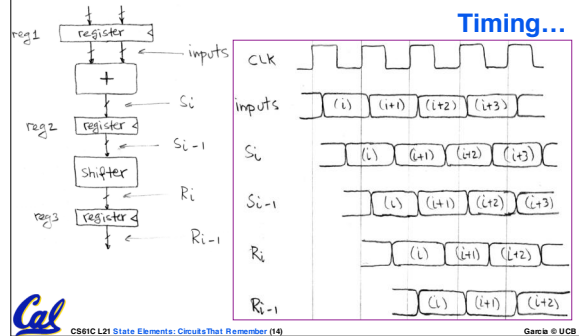

Finite State Machines Introduction

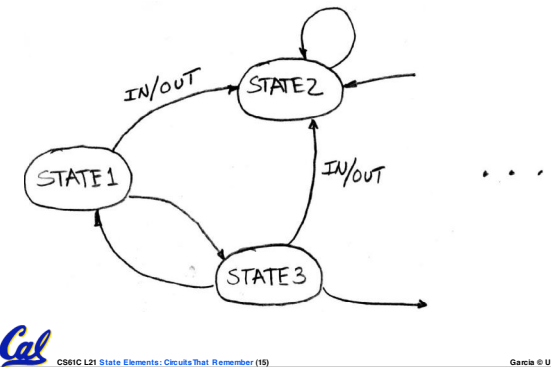

Finite State Machine Example: 3 ones...

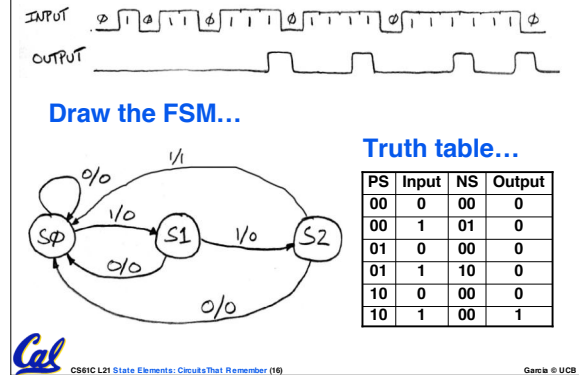


Draw the FSM...


Truth table...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

Hardware Implementation of FSM

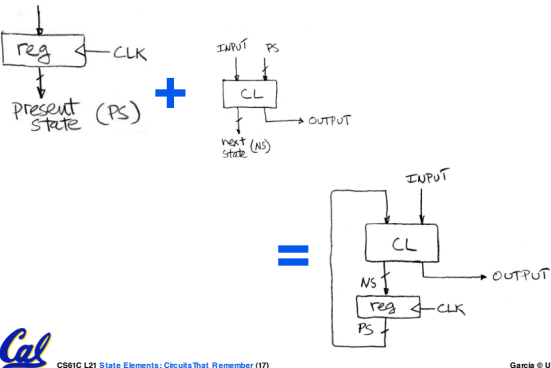

General Model for Synchronous Systems

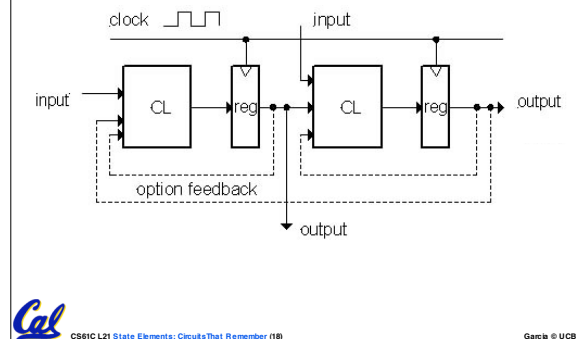

Peer Instruction

- A. HW feedback akin to SW recursion
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	FTT
8:	TTT

CS61C L21 State Elements: Circuits That Remember (19)

Garcia © UCB

"And In conclusion..."

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
 - Setup and Hold times important
- We pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
 - You'll see them in HW classes (150,152) & 164



CS61C L21 State Elements: Circuits That Remember (21)

Garcia © UCB