

inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**

**Lecture 21 –  
State Elements: Circuits That Remember**



**Lecturer PSOE Dan Garcia**

[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)

**CPU, GPU, now PPU! ⇒**  
**Ageia's "PhysX" chip will**  
**accelerate physics common to video**  
**games: rigid, soft body & fluid**  
**dynamics, collision detection, finite**  
**element analysis, hair & clothing sim!**



[www.ageia.com/technology.html](http://www.ageia.com/technology.html)



upe.cs.berkeley.edu

## UPE Undergraduate Lecture Series

**The First 30 Years of Berkeley CS**  
**3/10 Thursday, 6-7pm 306 Soda**



**Prof Richard Karp**

Turing Award Winner, Distinguished Teacher

**A personal perspective on the history of the Computer Science Division, including the personalities and politics behind its formation, its greatest achievements, and its prospects for the future.**



# Review...


---

- **ISA is very important abstraction layer**
  - **Contract between HW and SW**
- **Basic building blocks are logic *gates***
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types**
  - **Stateless Combinational Logic (&,!,~), in which *output is function of input only***
  - **State circuits (e.g., registers)**



# Accumulator Example


---

 

**Want:**     `S=0;`  
          `for (i=0;i<n;i++)`  
              `S = S + Xi`

# First try...Does this work?

---

 


**Nope!**

**Reason #1... What is there to control the next iteration of the 'for' loop?**


**Reason #2... How do we say: 's=0'?**




# Second try...How about this? Yep!

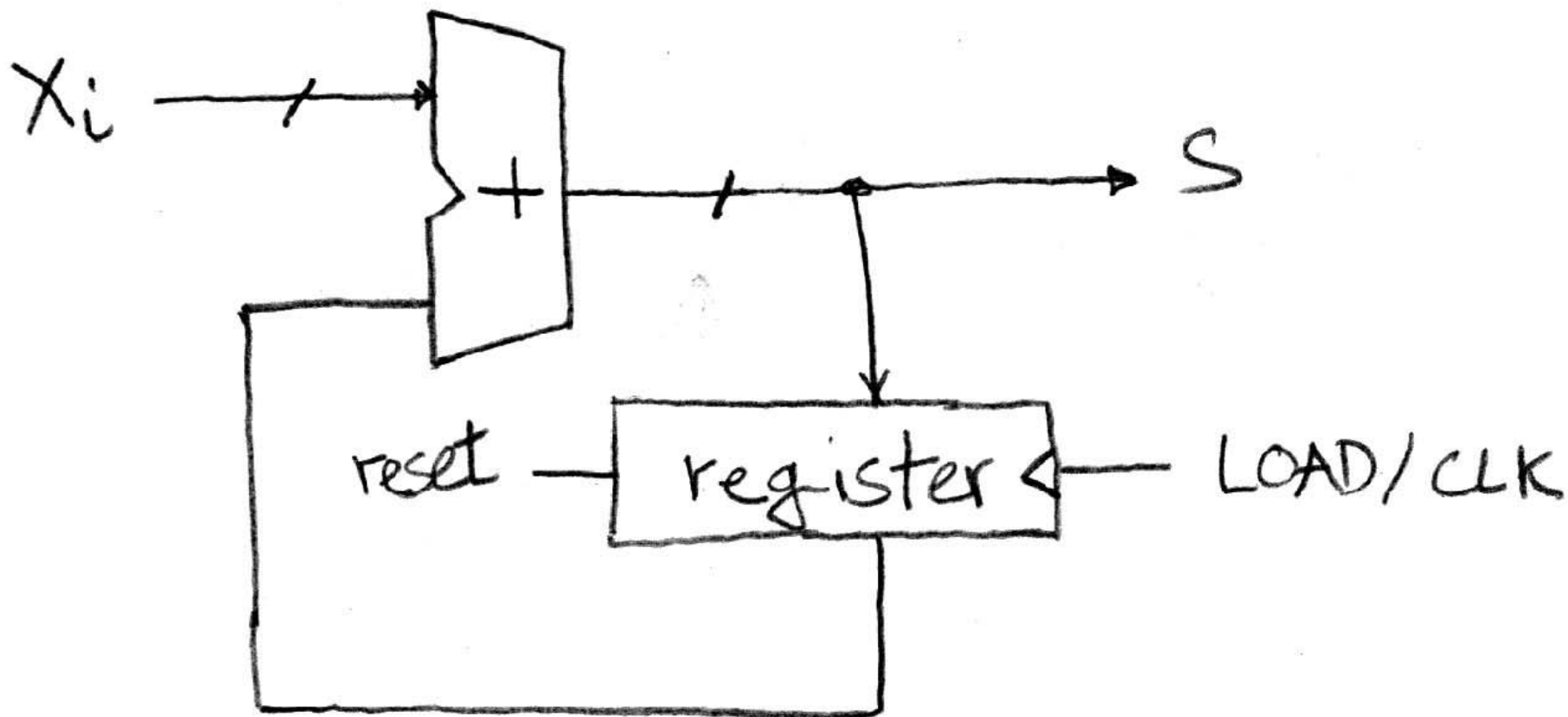

Rough timing...

 

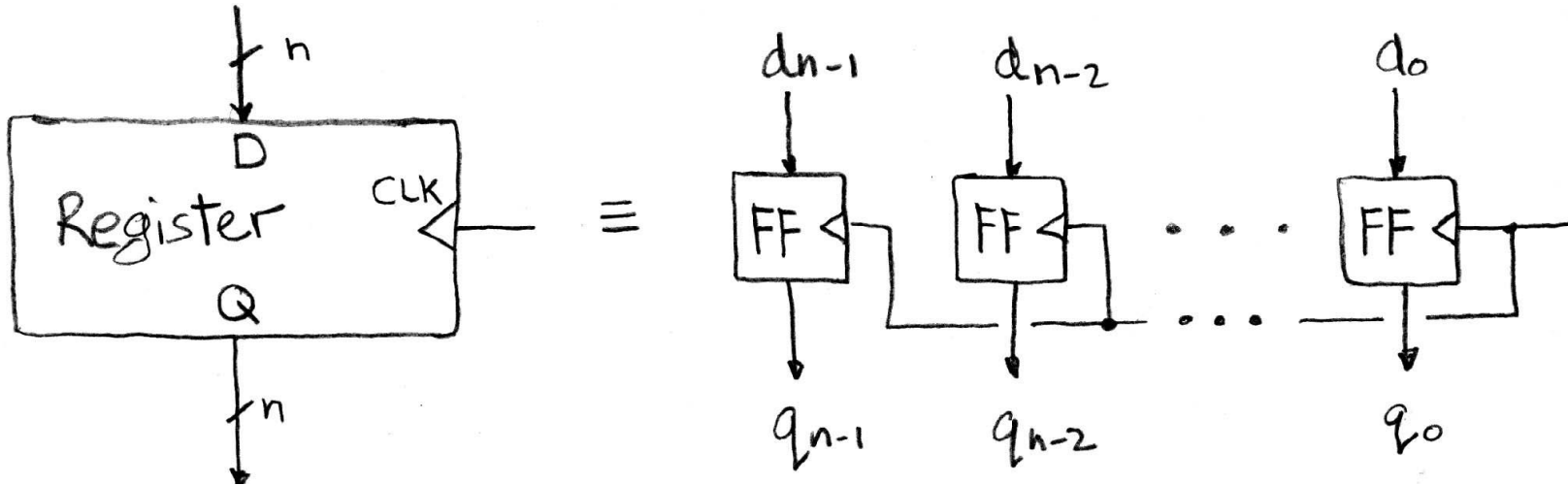
# Register Details...What's in it anyway?



- $n$  instances of a “Flip-Flop”, called that because the output flips and flops betw. 0,1
- $D$  is “data”
- $Q$  is “output”
- Also called “d-q Flip-Flop”, “d-type Flip-Flop”



 
# What's the timing of a Flip-flop? (1/2)



- **Edge-triggered d-type flip-flop**

- This one is “positive edge-triggered”

 


- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”





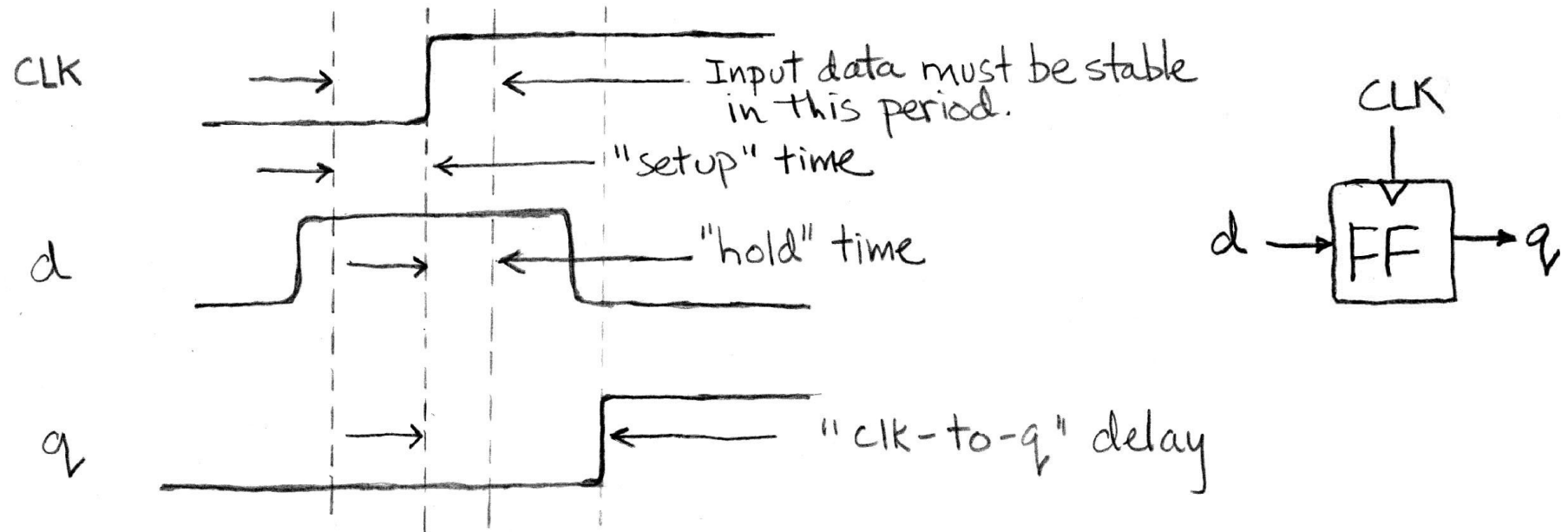
# What's the timing of a Flip-flop? (2/2)



- **Edge-triggered d-type flip-flop**

- This one is "positive edge-triggered"

 


- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."


 
# Administrivia - Midterm

- Your TAs and readers stayed up until 6:30am to get your exams back to you!
- $\bar{x}$ : 47, Median: 48,  $\sigma$ : 14.4



UCB CS61C 2005Sp Midterm  
mean=47, median=48, stdev=14



  
# Accumulator Revisited (proper timing 1/2)



  
# Accumulator Revisited (proper timing 2/2)



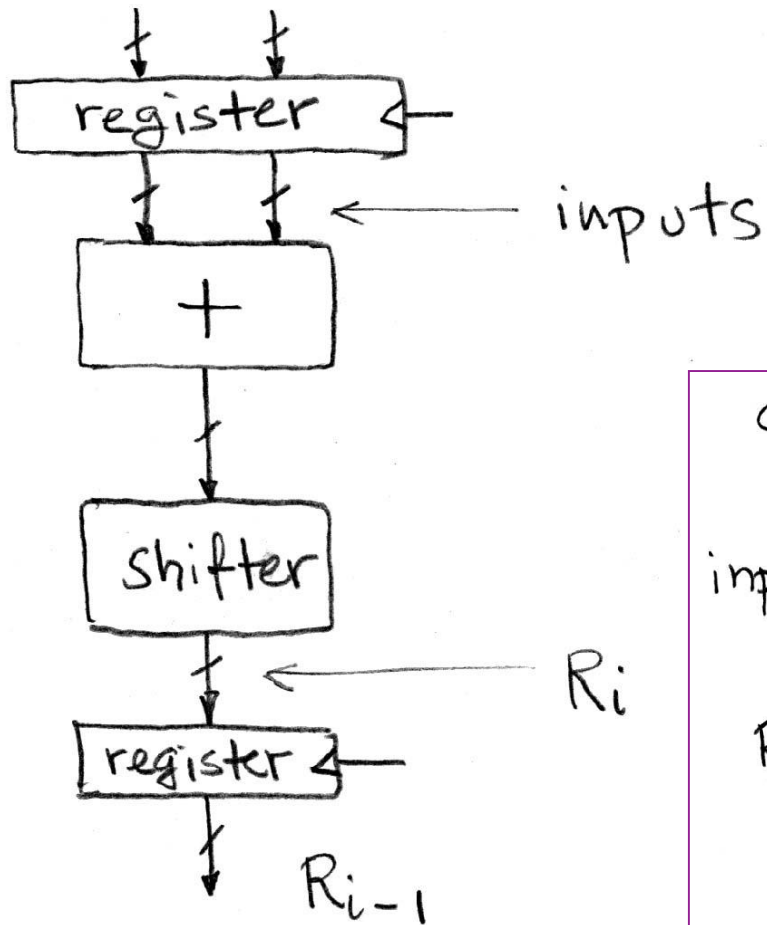
# Pipelining to improve performance (1/2)




## Timing...

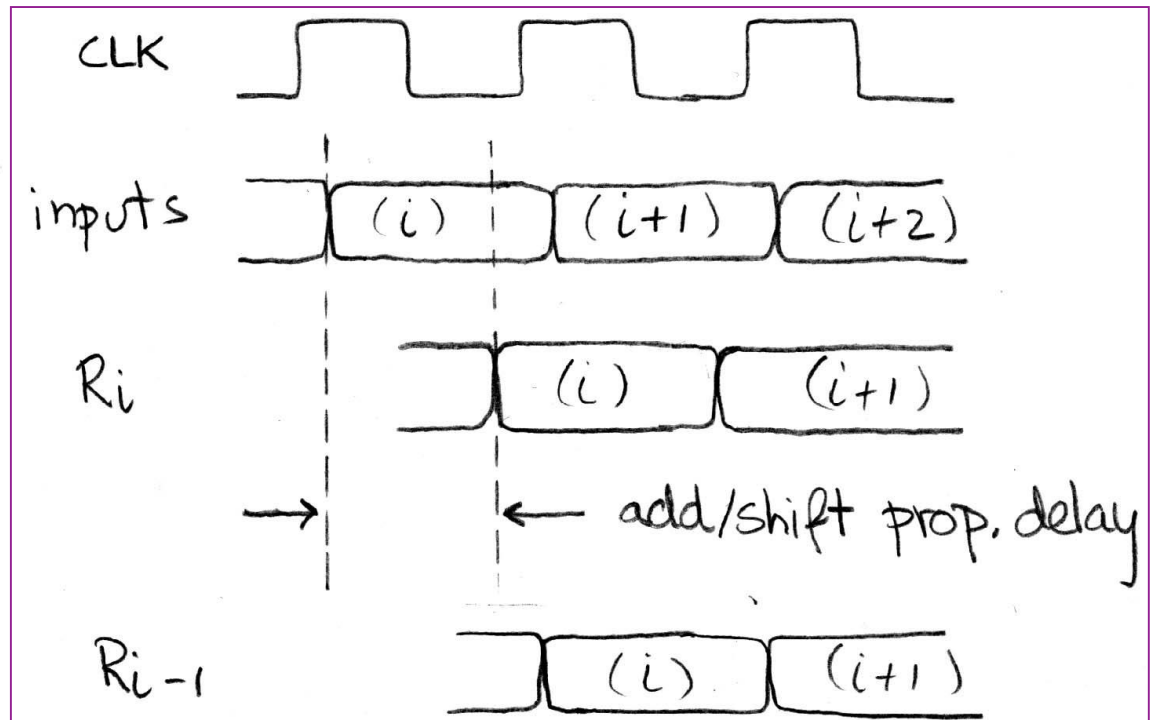
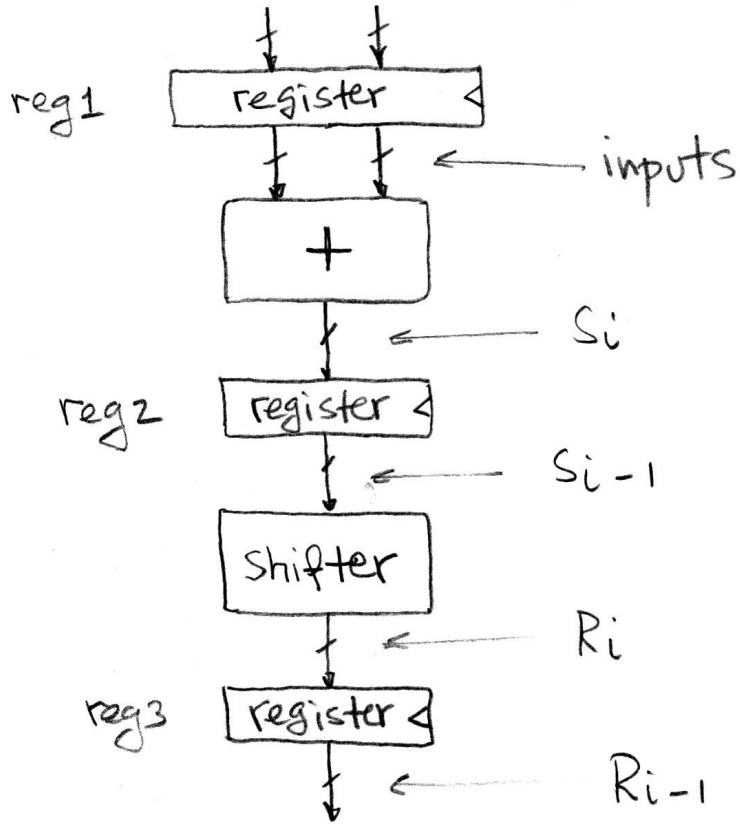
# Pipelining to improve performance (2/2)




## Timing...

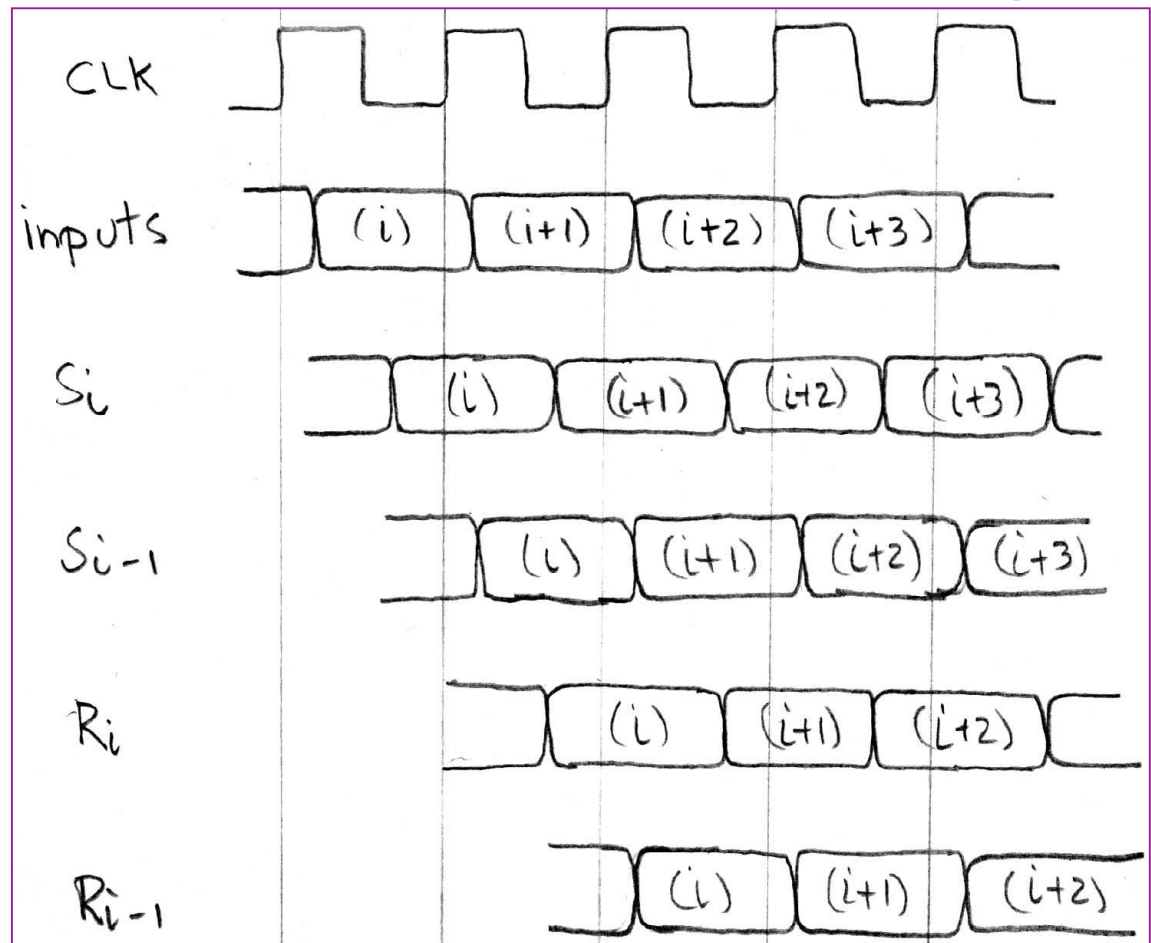


# Finite State Machines Introduction


---

 
 
# Finite State Machine Example: 3 ones...



Draw the FSM...

 


Truth table...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1






# Hardware Implementation of FSM

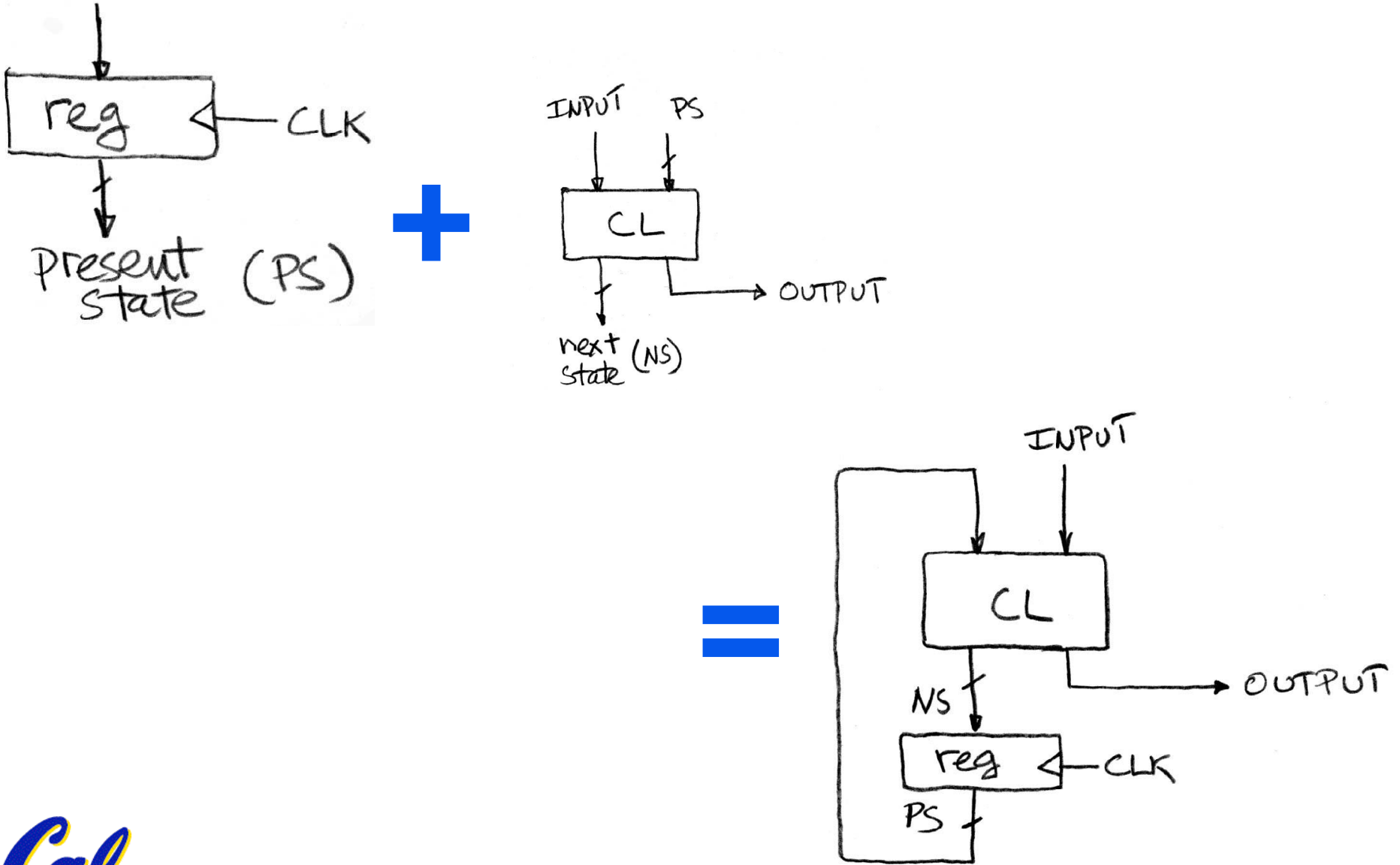

# General Model for Synchronous Systems

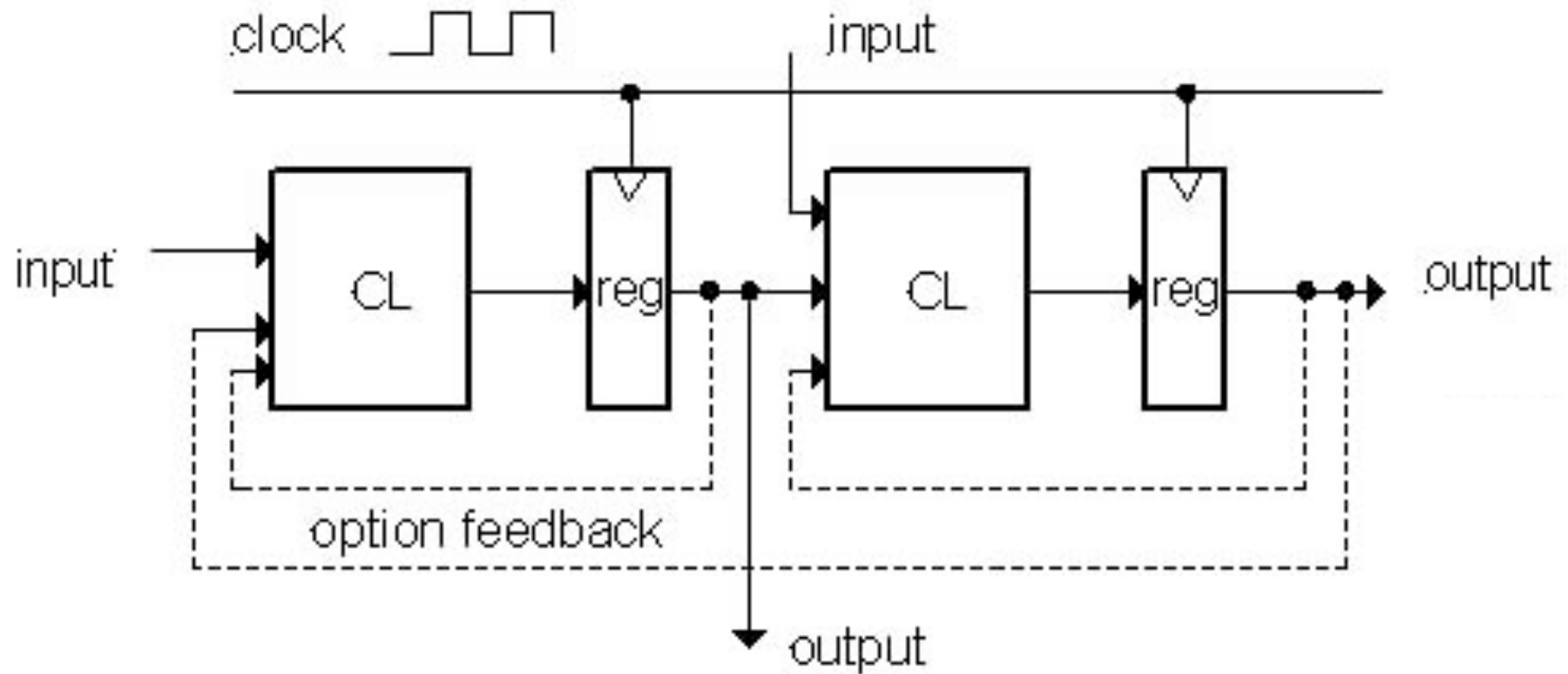

# Peer Instruction

---

- A. HW feedback akin to SW recursion**
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

	ABC
1:	<b>FFF</b>
2:	<b>FFT</b>
3:	<b>FTF</b>
4:	<b>FTT</b>
5:	<b>TFF</b>
6:	<b>TFT</b>
7:	<b>TF</b>
8:	<b>TTT</b>

## “And In conclusion...”

---

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
  - Setup and Hold times important
- We pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
  - You’ll see them in HW classes (150,152) & 164

