

inst.eecs.berkeley.edu/~cs61c
CS61C : Machine Structures

**Lecture 24 –
Latches**



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia


SETI@Home? Yak! ⇒

The Honeynet project uses “honeypot” PCs & monitors how long it takes (sec-min) for them to be hacked and what happens. **1 Mebi “botnets”** are used for spam, viruses, DDoS, Google AdSense, hacking gambling, id theft!



news.bbc.co.uk/2/hi/technology/4354109.stm

Last time: Extremely Clever Subtractor

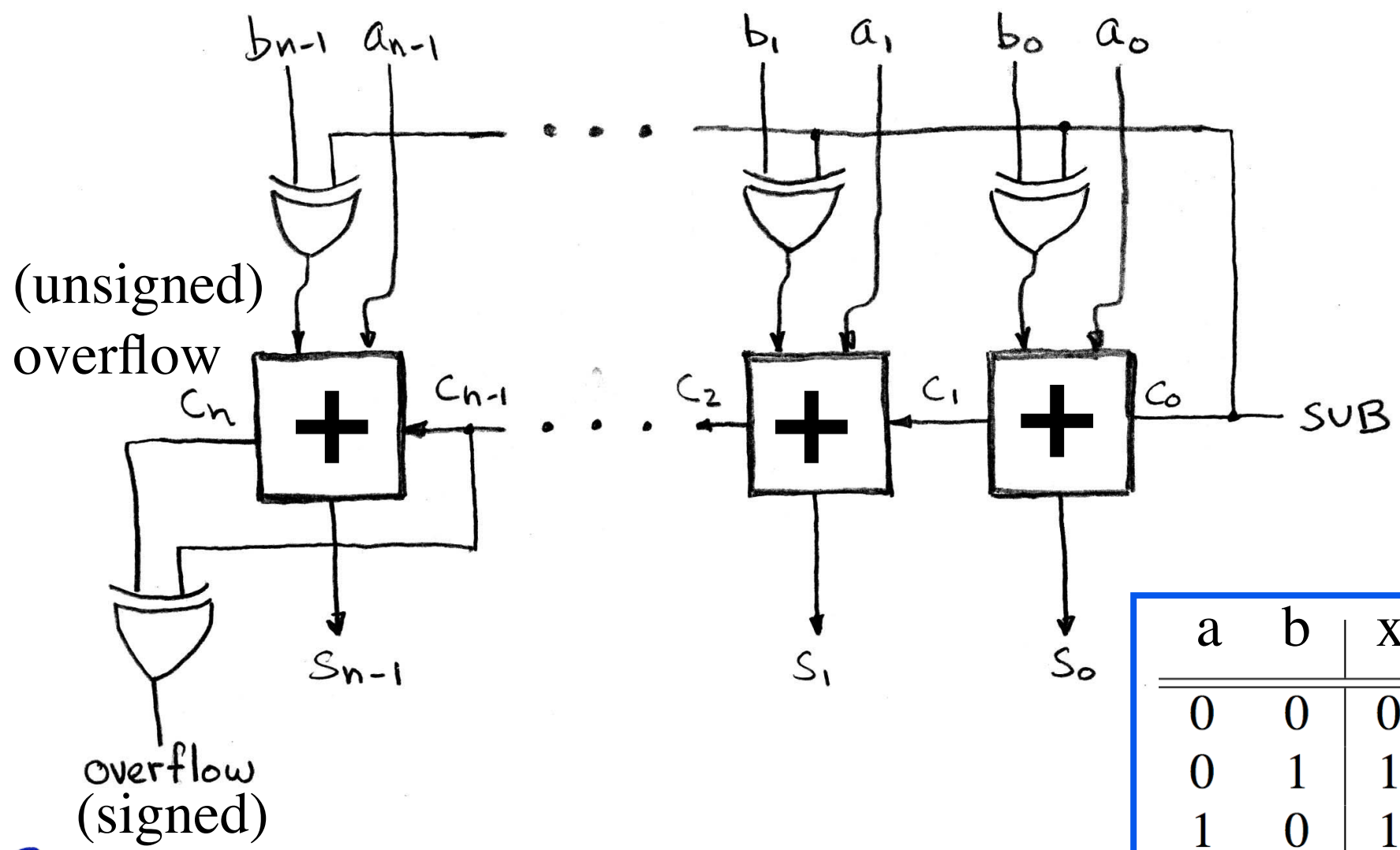


a	b	xor
0	0	0
0	1	1
1	0	1
1	1	0

Garcia © UCB



2-Input Multiplexor (MUX) Review

Symbol

 

Definition

D	C
0	A
1	B


Review...

- **Use muxes to select among input**
 - **S input bits selects 2^S inputs**
 - **Each input can be n-bits wide, indep of S**
- **Implement muxes hierarchically**
- **ALU can be implemented using a mux**
 - **Coupled with basic block elements**
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - **XOR serves as conditional inverter**



Combinational Logic from 10 miles up

 - CL circuits simply compute a binary function (e.g., from truth table)
- Once the inputs go away, the outputs go away, nothing is saved, **no STATE**
 - Similar to a function in Scheme with no `set!` or `define` to save anything




```
(define (xor x y)
  (or (and (not x) y)
      (and x (not y))))
```

- How does the computer **remember** data? [e.g., for registers]



State Circuits Overview


- State circuits have **feedback**, e.g.

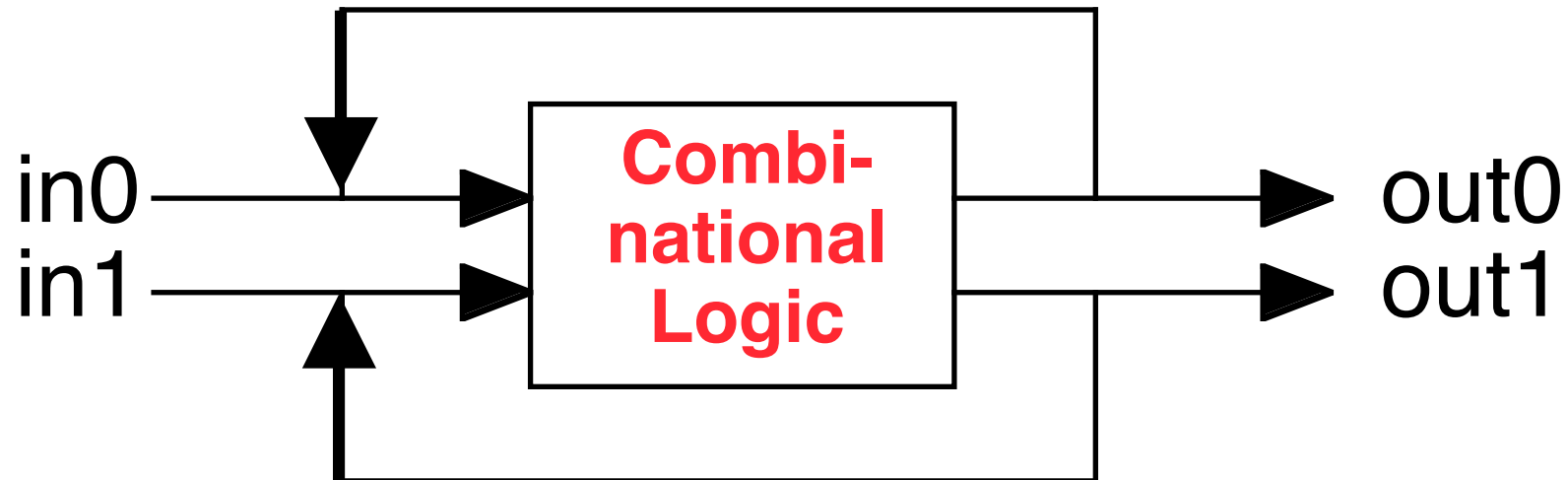


- Output is function of inputs + fed-back signals.
- Feedback signals are the circuit's **state**.
- What aspects of this circuit might cause complications?



A simpler state circuit: two inverters

 

 - When started up, it's **internally stable**.
- Provide an **or** gate for coordination:




What's the result? **How do we set to 0?**


An R-S latch (cross-coupled NOR gates)

- S means “set” (to 1),
R means “reset” (to 0).

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 


- Adding Q' gives standard RS-latch:

 

Truth table

S	R	Q
0	0	hold (keep value)
0	1	0
1	0	1
1	1	unstable

An R-S latch (in detail)

 


A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Truth table

S	R	Q	\bar{Q}	Q(t+ Δt)
0	0	0	1	0 hold
0	0	1	0	1 hold
0	1	0	1	0 reset
0	1	1	0	0 reset
1	0	0	1	1 set
1	0	1	0	1 set
1	1	0	x	x unstable
1	1	1	x	x unstable



R-S latch in scheme

 

**It's really just...
recursion!
(demo)**


A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

```
(define (rs-latch r s)
  (define (rsl-h q qbar)
    (rsl-h (nor r qbar)
           (nor q s)))
  (rsl-h #t #f))
```



State diagram

 - **States represent possible output values.**
- **Transitions represent changes between states based on inputs.**



What does it mean to “clobber” midterm?

- You **STILL** have to take the final even if you aced the midterm!
- The final will contain midterm-material Qs and new, post-midterm Qs
- They will be graded separately
- If you do “**better**” on the midterm-material, we will **clobber your midterm with the “new” score!** **If you do worse, midterm unchanged.**
- What does “better” mean?
 - Better w.r.t. Standard Deviations around mean
- What does “new” mean?
 - Score based on remapping St. Dev. score on final midterm-material to midterm score St. Dev.



“Clobber the midterm” example

- **Midterm**

- Mean: 47
- Standard Deviation: 14
- **You got a 33, one σ below**



- **Final Midterm-Material Questions**


- Mean: 40
- Standard Deviation: 20
- **You got a 60, one σ above**
- **Your new midterm score is now mean + σ
= 47 + 14 = 61 (~ double your old score)!**



Controlling R-S latch with a clock

- Can't change R and S while clock is active.

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 


- Clocked latches are called *flip-flops*.

D flip-flop are what we really use



- Inputs **C** (clock) and **D**.
- **When C is 1, latch open, output = D** (even if it changes, “transparent latch”)
- **When C is 0, latch closed, output = stored value.**

C	D	AND
0	0	0
0	1	0
1	0	0
1	1	1

 

D flip-flop details

  - We don't like transparent latches
- We can build them so that the latch is only open for an instant, on the **rising edge of a clock** (as it goes from 0⇒1)




Timing Diagram

But do you really understand NORs?

- If one input is 1, what is a NOR?
- If one input is 0, what is a NOR?

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 


A	NOR
0	B'
1	0

But do you really understand NANDs?

- If one input is 1, what is a NAND?
- If one input is 0, what is a NAND?


A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

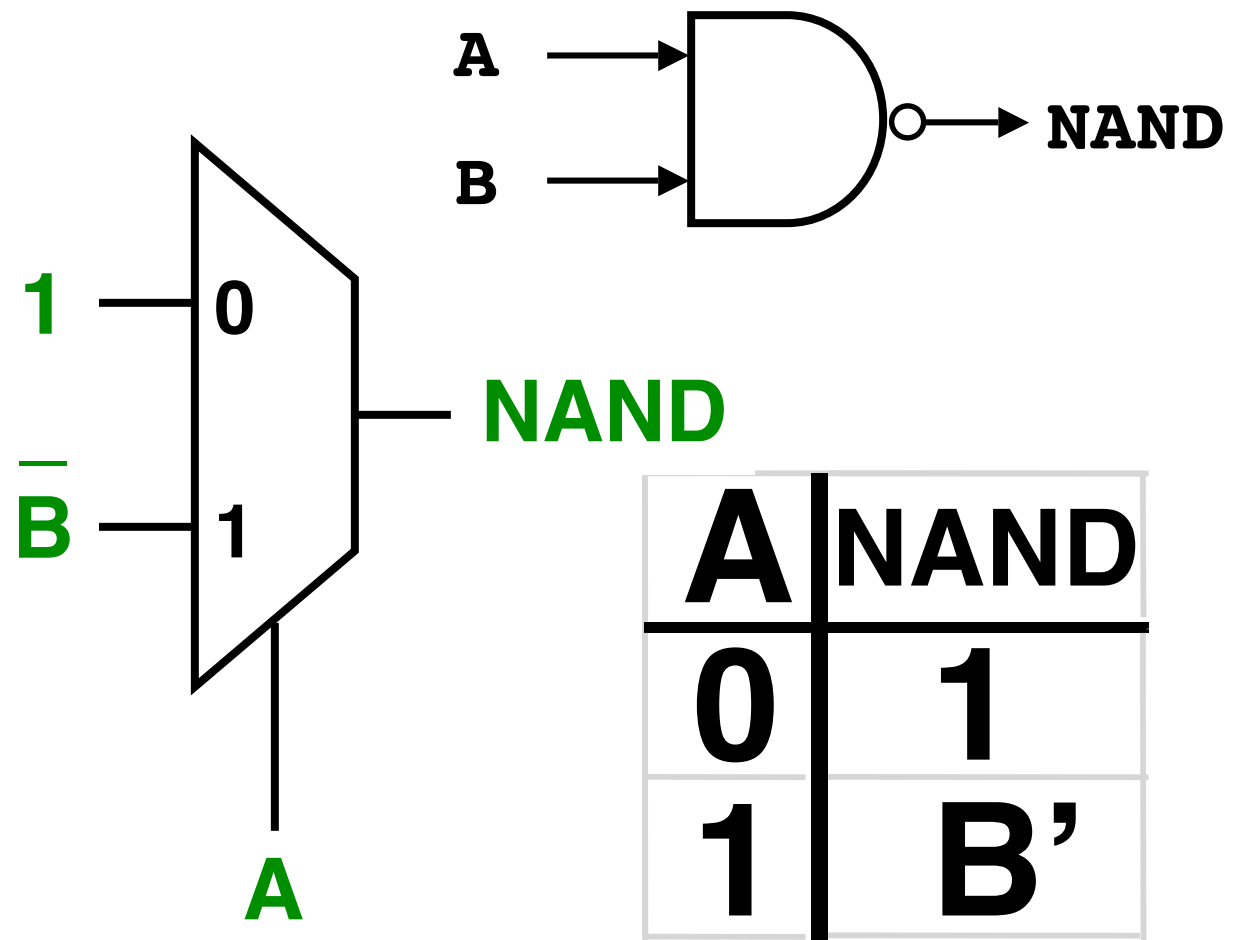

Peer instruction

Pick the truth table that results from substituting NAND gates for the NOR gates in the R-S latch:

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Q
0	0	hold
0	1	0
1	0	1
1	1	undef

A	B	Q
0	0	hold
0	1	1
1	0	0
1	1	undef

A	B	Q
0	0	undef
0	1	0
1	0	1
1	1	hold

A	B	Q
0	0	undef
0	1	1
1	0	0
1	1	hold

1

2

3

4



Peer Instruction

- A. $(a+b) \cdot (\bar{a}+b) = b$
- B. N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND
- C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. Truth table for mux with 4-bits of signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T

	ABC
1 :	FFF
2 :	FFT
3 :	FTF
4 :	FTT
5 :	TFF
6 :	TFT
7 :	TFF
8 :	TTT

“And In conclusion...”

- We use feedback to maintain **state**
- RS-Latch the simplest memory element
 - We're not allowed to assert both R and S
- Clocks tell us when latches change
- D-FlipFlops used to build Register files

