

**Lecture 25 –
 Single Cycle CPU Datapath**



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Paid to write a Mac virus?! =>

A Symantec employee claimed "Macs aren't more secure, there are just fewer virus writers!". DVForge, believing that Macs WERE more secure, initially offered \$25K to anyone (\$50K if from Symantec) who could infect a honeypot mac. They later retracted the offer.




CS61C L26 Single Cycle CPU Datapath (1)

www.dvforge.com/virus.shtml Garcia © UCB

Anatomy: 5 components of any Computer



This week and next

 

CS61C L26 Single Cycle CPU Datapath (2)

Garcia © UCB

Outline of Today's Lecture

- Design a processor: step-by-step
- Requirements of the Instruction Set
- Hardware components that match the instruction set requirements



CS61C L26 Single Cycle CPU Datapath (3)

Garcia © UCB

How to Design a Processor: step-by-step

1. Analyze instruction set architecture (ISA) => datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.




CS61C L26 Single Cycle CPU Datapath (4)

Garcia © UCB


Review: The MIPS Instruction Formats

• All MIPS instructions are 32 bits long. 3 formats:


• R-type

 

• I-type

 

• J-type

 

• The different fields are:

- **op**: operation ("opcode") of the instruction
- **rs, rt, rd**: the source and destination register specifiers
- **shamt**: shift amount
- **funct**: selects the variant of the operation in the "op" field
- **address / immediate**: address offset or immediate value
- **target address**: target address of jump instruction




CS61C L26 Single Cycle CPU Datapath (5)


Garcia © UCB

Step 1a: The MIPS-lite Subset for today


• ADDU and SUBU

 


• OR Immediate:

 

• LOAD and STORE Word

 

• BRANCH:

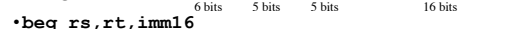

CS61C L26 Single Cycle CPU Datapath (6)

Garcia © UCB

Register Transfer Language

- RTL gives the **meaning** of the instructions

$\{op, rs, rt, rd, shamt, funct\} = MEM[PC]$

$\{op, rs, rt, Imm16\} = MEM[PC]$

- All start by fetching the instruction

inst Register Transfers

ADDU $R[rd] = R[rs] + R[rt]; PC = PC + 4$

SUBU $R[rd] = R[rs] - R[rt]; PC = PC + 4$

ORI $R[rt] = R[rs] \mid zero_ext(Imm16); PC = PC + 4$

LOAD $R[rt] = MEM[R[rs] + sign_ext(Imm16)]; PC = PC + 4$

STORE $MEM[R[rs] + sign_ext(Imm16)] = R[rt]; PC = PC + 4$

BEQ if ($R[rs] == R[rt]$) then
 $PC = PC + 4 + (sign_ext(Imm16) \parallel 00)$
 else $PC = PC + 4$



CS61C L26 Single Cycle CPU Datapath (7)

Garcia © UCB

Step 1: Requirements of the Instruction Set

- Memory (MEM)
 - instructions & data
- Registers (R: 32 x 32)
 - read RS
 - read RT
 - Write RT or RD
- PC
- Extender (sign extend)
- Add and Sub register or extended immediate
- Add 4 or extended immediate to PC



CS61C L26 Single Cycle CPU Datapath (8)

Garcia © UCB

Step 2: Components of the Datapath

- Combinational Elements
- Storage Elements
 - Clocking methodology




CS61C L26 Single Cycle CPU Datapath (9)


Garcia © UCB

Combinational Logic Elements (Building Blocks)


- Adder

 

- MUX

 

- ALU

 

CS61C L26 Single Cycle CPU Datapath (10)

Garcia © UCB

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

ADDU $R[rd] = R[rs] + R[rt]; \dots$

SUBU $R[rd] = R[rs] - R[rt]; \dots$

ORI $R[rt] = R[rs] \mid$
 $zero_ext(Imm16) \dots$

BEQ if ($R[rs] == R[rt]$)...

- Test to see if output == 0 for any ALU operation gives == test. How?

- P&H also adds AND, Set Less Than (1 if $A < B$, 0 otherwise)



ALU follows chap 5

CS61C L26 Single Cycle CPU Datapath (11)

Garcia © UCB

Administrivia

- Final Exam location TBA (exam grp 5)

• Sat, 2005-05-14, 12:30–3:30pm

• ALL students are required to complete ALL of the exam (even if you aced the midterm)

• Same format as the midterm

- 3 Hours
- Closed book, **except for 2 study sheets + green**
- Leave your backpacks, books at home

- Homework 6 out today, due in a week (mon)




CS61C L26 Single Cycle CPU Datapath (12)

Garcia © UCB

Storage Element: Idealized Memory

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is selected by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => Data Out valid after "access time."

 


CS61C L26 Single Cycle CPU Datapath (13)

Garcia © UCB

Storage Element: Register (Building Block)

 - Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - negated (or deasserted) (0): Data Out will not change
 - asserted (1): Data Out will become Data In




CS61C L26 Single Cycle CPU Datapath (14)

Garcia © UCB

Storage Element: Register File

- Register File consists of 32 registers:
 - Two 32-bit output buses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid => busA or busB valid after "access time."

 

CS61C L26 Single Cycle CPU Datapath (15)

Garcia © UCB

Step 3: Assemble DataPath meeting requirements

- Register Transfer Requirements => Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation




CS61C L26 Single Cycle CPU Datapath (16)

Garcia © UCB

3a: Overview of the Instruction Fetch Unit

 - The common RTL operations
 - Fetch the Instruction: mem[PC]
 - Update the program counter:
 - Sequential Code: PC = PC + 4
 - Branch and Jump: PC = "something else"




CS61C L26 Single Cycle CPU Datapath (17)

Garcia © UCB

3b: Add & Subtract

- $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: `addu rd, rs, rt`
 - Ra, Rb, and Rr come from instruction's Rs, Rt, and Rd fields
- | | | | | | | |
|--------|--------|--------|--------|--------|--------|---|
| 31 | 26 | 21 | 16 | 11 | 6 | 0 |
| op | rs | rt | rd | shamt | funct | |
| 6 bits | 5 bits | 5 bits | 5 bits | 5 bits | 6 bits | |
- ALUctr and RegWr: control logic after decoding the instruction

 

CS61C L26 Single Cycle CPU Datapath (18)

Garcia © UCB

- Already defined register file, ALU

Peer Instruction

- A. We should use the main ALU to compute $PC=PC+4$
- B. We're going to be able to read 2 registers and write a 3rd in 1 cycle
- C. Datapath is hard, Control is easy



CS61C L26 Single Cycle CPU Datapath (19)

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT

Garcia © UCB

How to Design a Processor: step-by-step

- 1. Analyze instruction set architecture (ISA)
=> datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)



CS61C L26 Single Cycle CPU Datapath (20)

Garcia © UCB