

Lecture 25 – Single Cycle CPU Datapath



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Paid to write a Mac virus?! ⇒


A Symantec employee claimed
“Macs aren’t more secure, there are just fewer
virus writers!”. DVForge, believing that Macs
WERE more secure, initially offered \$25K to
anyone (\$50K if from Symantec) who could infect
a honeypot mac. They later retracted the offer.




www.dvforge.com/virus.shtml



Anatomy: 5 components of any Computer

 

This week
and next

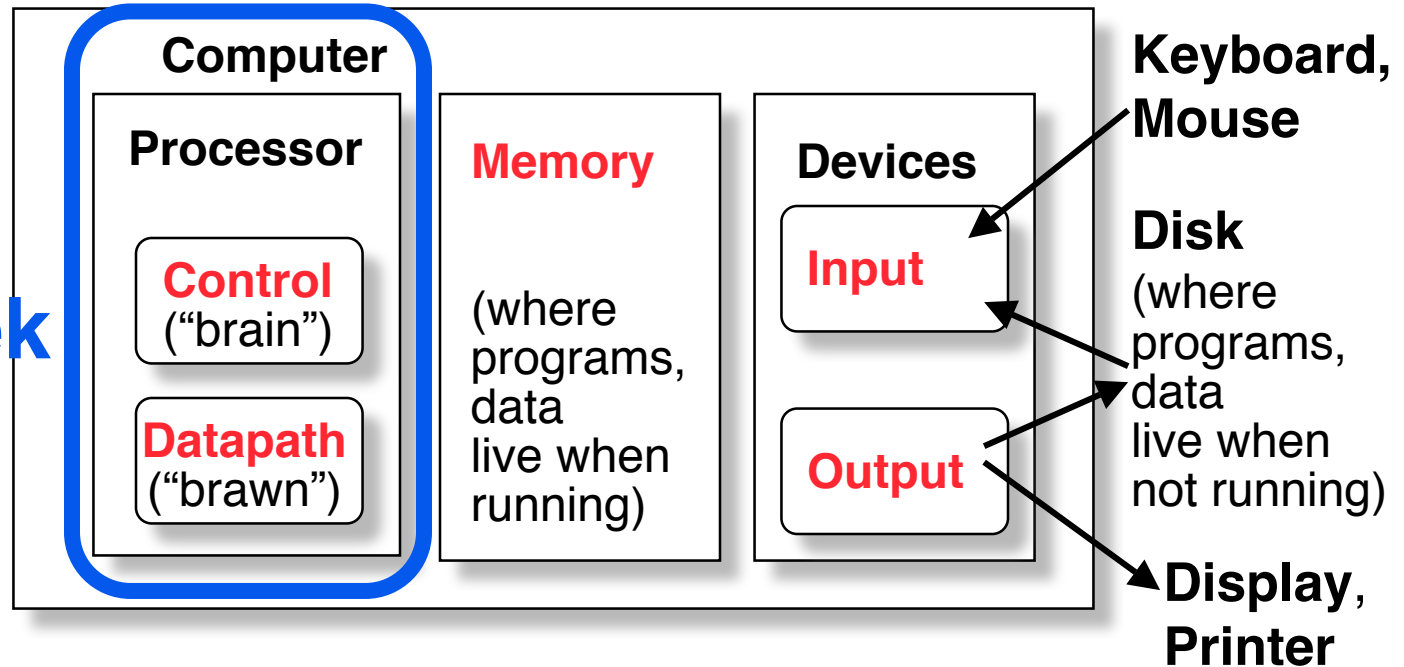

Outline of Today's Lecture

- **Design a processor: step-by-step**
- **Requirements of the Instruction Set**
- **Hardware components that match the instruction set requirements**



How to Design a Processor: step-by-step


- **1. Analyze instruction set architecture (ISA)**
=> datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic**




Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:

- R-type

 

- I-type

 

- J-type




- The different fields are:

- **op**: operation (“opcode”) of the instruction
- **rs, rt, rd**: the source and destination register specifiers
- **shamt**: shift amount
- **funct**: selects the variant of the operation in the “op” field
- **address / immediate**: address offset or immediate value
- **target address**: target address of jump instruction




Step 1a: The MIPS-lite Subset for today


• ADDU and SUBU

 


• OR Immediate:

 

• LOAD and STORE Word

 

• BRANCH:

 

Register Transfer Language

- **RTL gives the meaning of the instructions**

$$\{op, rs, rt, rd, shamt, funct\} = \text{MEM}[PC]$$
$$\{op, rs, rt, \text{Imm16}\} = \text{MEM}[PC]$$

- **All start by fetching the instruction**

inst Register Transfers

ADDU $R[rd] = R[rs] + R[rt];$ **PC = PC + 4**

SUBU $R[rd] = R[rs] - R[rt];$ **PC = PC + 4**

ORI $R[rt] = R[rs] \mid \text{zero_ext}(\text{Imm16});$ **PC = PC + 4**

LOAD $R[rt] = \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ **PC = PC + 4**

STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] = R[rt];$ **PC = PC + 4**

BEQ **if (R[rs] == R[rt]) then**

PC = PC + 4 + (sign_ext(Imm16) || 00)

else PC = PC + 4



Step 1: Requirements of the Instruction Set

- **Memory (MEM)**
 - instructions & data
- **Registers (R: 32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender (sign extend)**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**




Step 2: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology





Combinational Logic Elements (Building Blocks)

• Adder

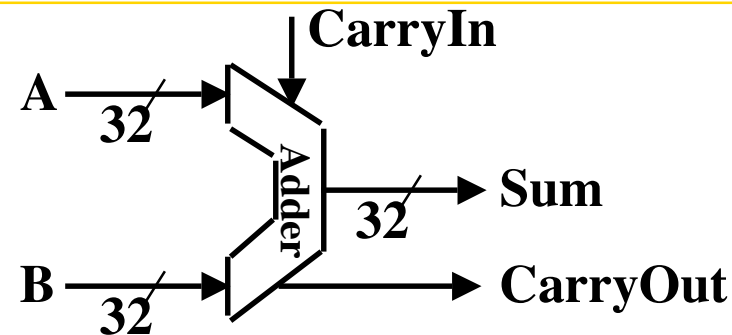

• MUX

  

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

```
ADDU R[rd] = R[rs] + R[rt]; ...
```

```
SUBU R[rd] = R[rs] - R[rt]; ...
```

```
ORI R[rt] = R[rs] |  
zero_ext(Imm16) ...
```

```
BEQ if ( R[rs] == R[rt] ) ...
```

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND,
Set Less Than (1 if $A < B$, 0 otherwise)

Administrivia

- **Final Exam location TBA (exam grp 5)**
 - **Sat**, 2005-05-14, 12:30–3:30pm
 - **ALL students are required to complete ALL of the exam (even if you aced the midterm)**
 - **Same format as the midterm**
 - 3 Hours
 - Closed book, **except for 2 study sheets + green**
 - Leave your backpacks, books at home
- **Homework 6 out today, due in a week (mon)**



Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus


- **Clock input (CLK)**

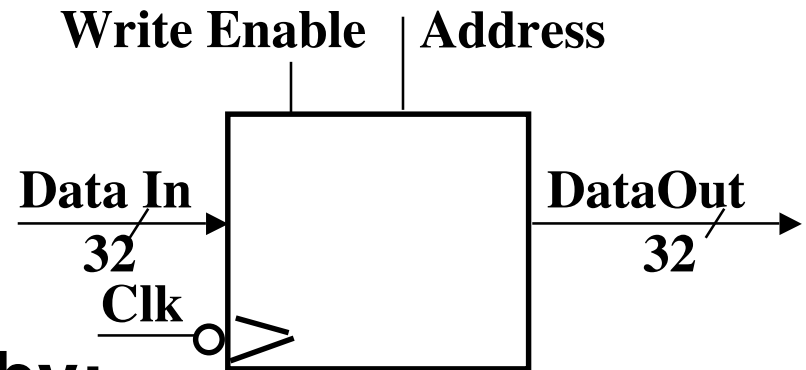- The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid \Rightarrow Data Out valid after “access time.”



Storage Element: Register (Building Block)

 - **Similar to D Flip Flop except**
 - N-bit input and output
 - Write Enable input
- **Write Enable:**
 - negated (or deasserted) (0):
Data Out will not change
 - asserted (1):
Data Out will become Data In




Storage Element: Register File

- Register File consists of 32 registers:

- Two 32-bit output busses:

busA and busB

- One 32-bit input bus: busW

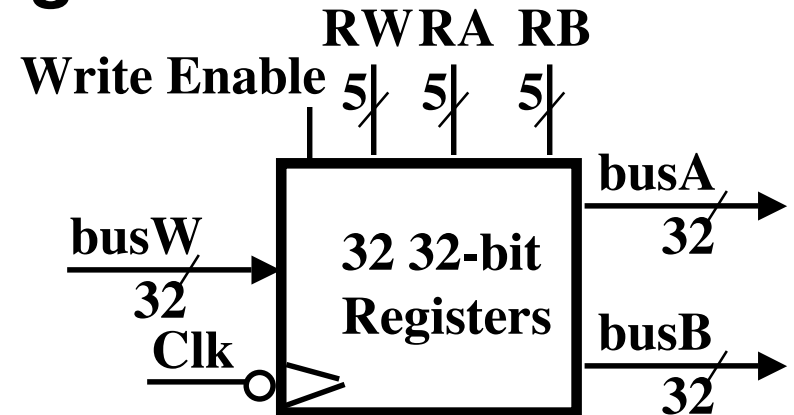

- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:

- RA or RB valid => busA or busB valid after “access time.”




Step 3: Assemble DataPath meeting requirements

- Register Transfer Requirements
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation



3a: Overview of the Instruction Fetch Unit

 
- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} = \text{PC} + 4$
 - Branch and Jump: $\text{PC} = \text{“something else”}$




3b: Add & Subtract

• $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: `addU rd,rs,rt`

 - Ra, Rb, and Rw come from instruction's **Rs**, **Rt**, and **Rd** fields



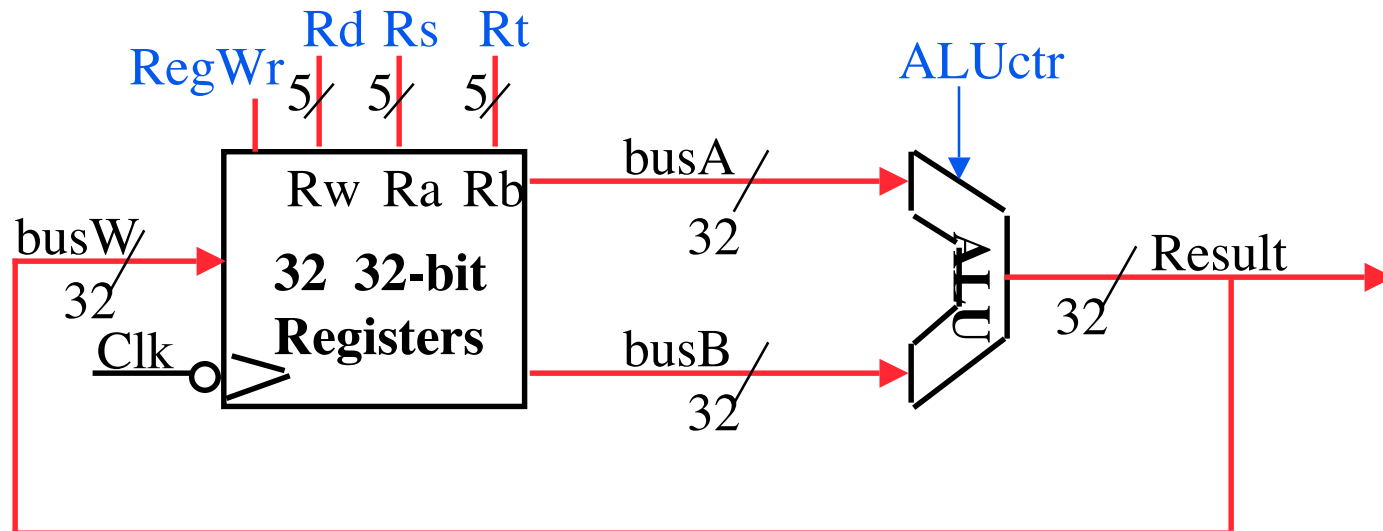- **ALUctr** and **RegWr**: control logic after decoding the instruction



• Already defined register file, ALU

Peer Instruction

- A. We should use the main ALU to compute $PC=PC+4$
- B. We're going to be able to read 2 registers and write a 3rd in 1 cycle
- C. Datapath is hard, Control is easy

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



How to Design a Processor: step-by-step

- **1. Analyze instruction set architecture (ISA)**
⇒ datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic (hard part!)**

