

`inst.eecs.berkeley.edu/~cs61c`
CS61C : Machine Structures

**Lecture 26 –
Single Cycle CPU Datapath II**



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

98,389 UC Identity thefts?! ⇒

A laptop was stolen from Grad division with names, SS #, birth dates of almost 10^6 former grad students at UC Berkeley. The thief may not know what they have! Sensitive data allowed on portables? Good idea...NOT!



newscenter.berkeley.edu/security/grad/

How to Design a Processor: step-by-step

- **1. Analyze instruction set architecture (ISA)**
=> datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic (hard part!)**




Step 3: Assemble DataPath meeting requirements

- Register Transfer Requirements
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation



3a: Overview of the Instruction Fetch Unit

 
- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} = \text{PC} + 4$
 - Branch and Jump: $\text{PC} = \text{“something else”}$




3b: Add & Subtract

• $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: `addU rd,rs,rt`

 • Ra, Rb, and Rw come from instruction's **Rs**, **Rt**, and **Rd** fields




 • **ALUctr** and **RegWr**: control logic after decoding the instruction



• We've already defined register file, ALU



Clocking Methodology

 

- **Storage elements clocked by same edge**
- **Being physical devices, flip-flops (FF) and combinational logic have some delays**
 - **Gates: delay from input change to output change**
 - **Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF, and we have the usual clock-to-Q delay**
- **“Critical path” (longest path through logic) determines length of clock period**




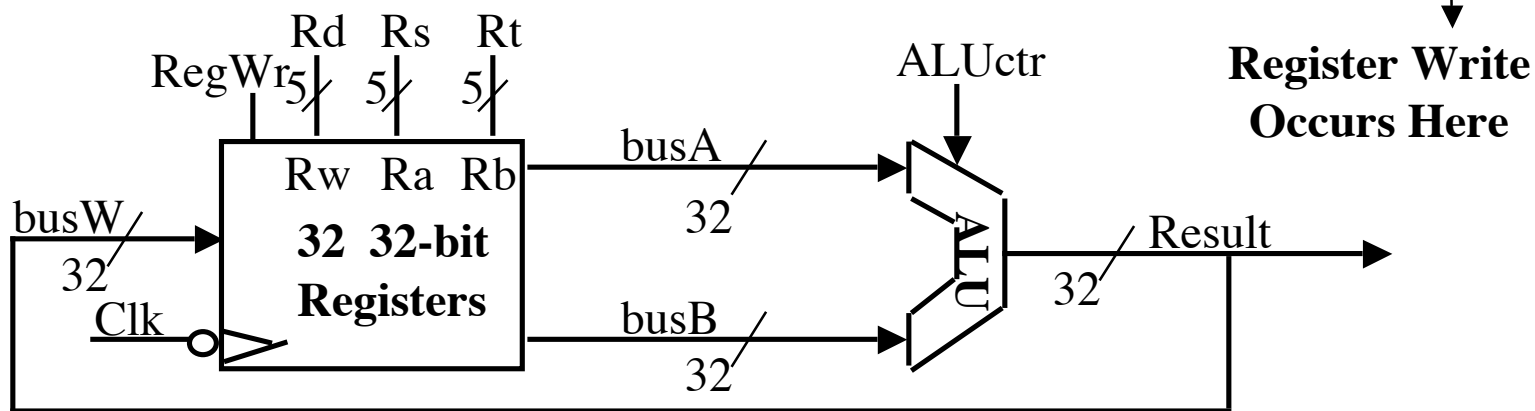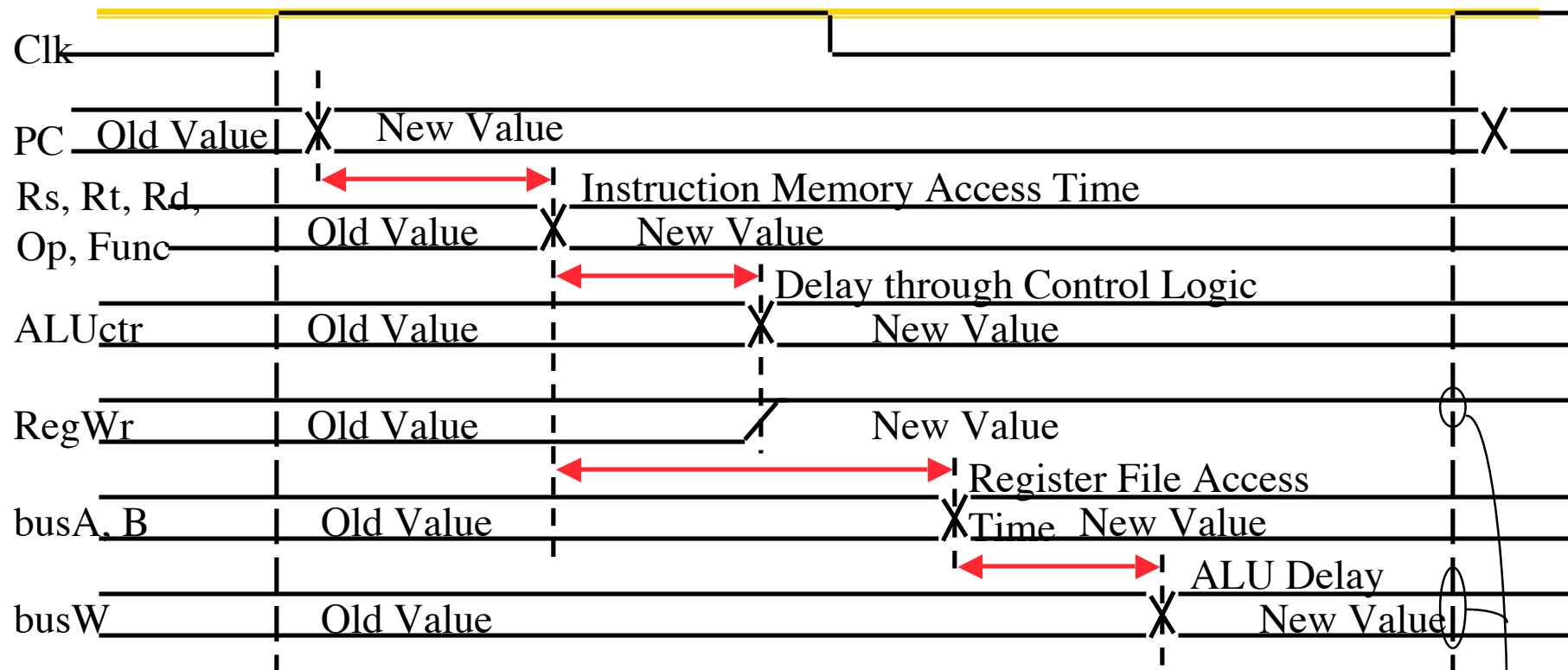Register-Register Timing: One complete cycle




3c: Logical Operations with Immediate

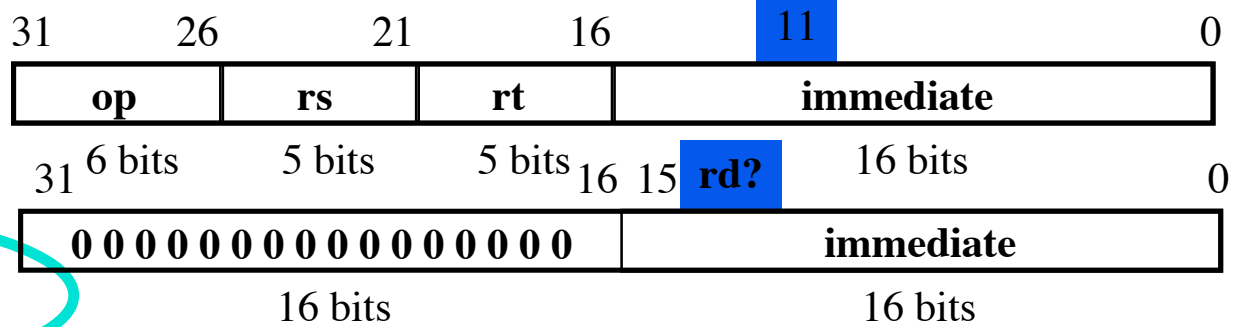- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$





What about Rt register read??

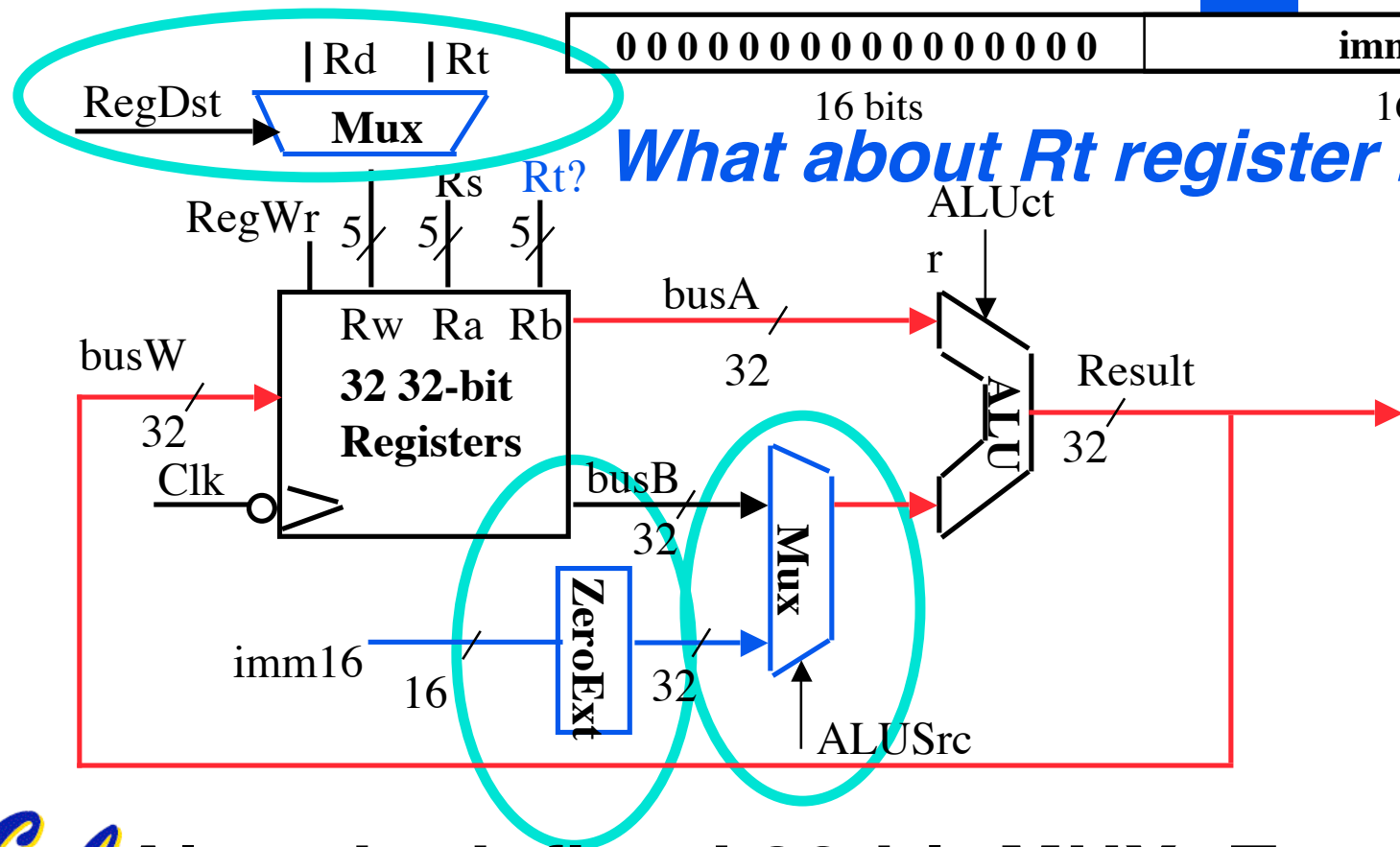

• Already defined 32-bit MUX; Zero Ext?


3d: Load Operations

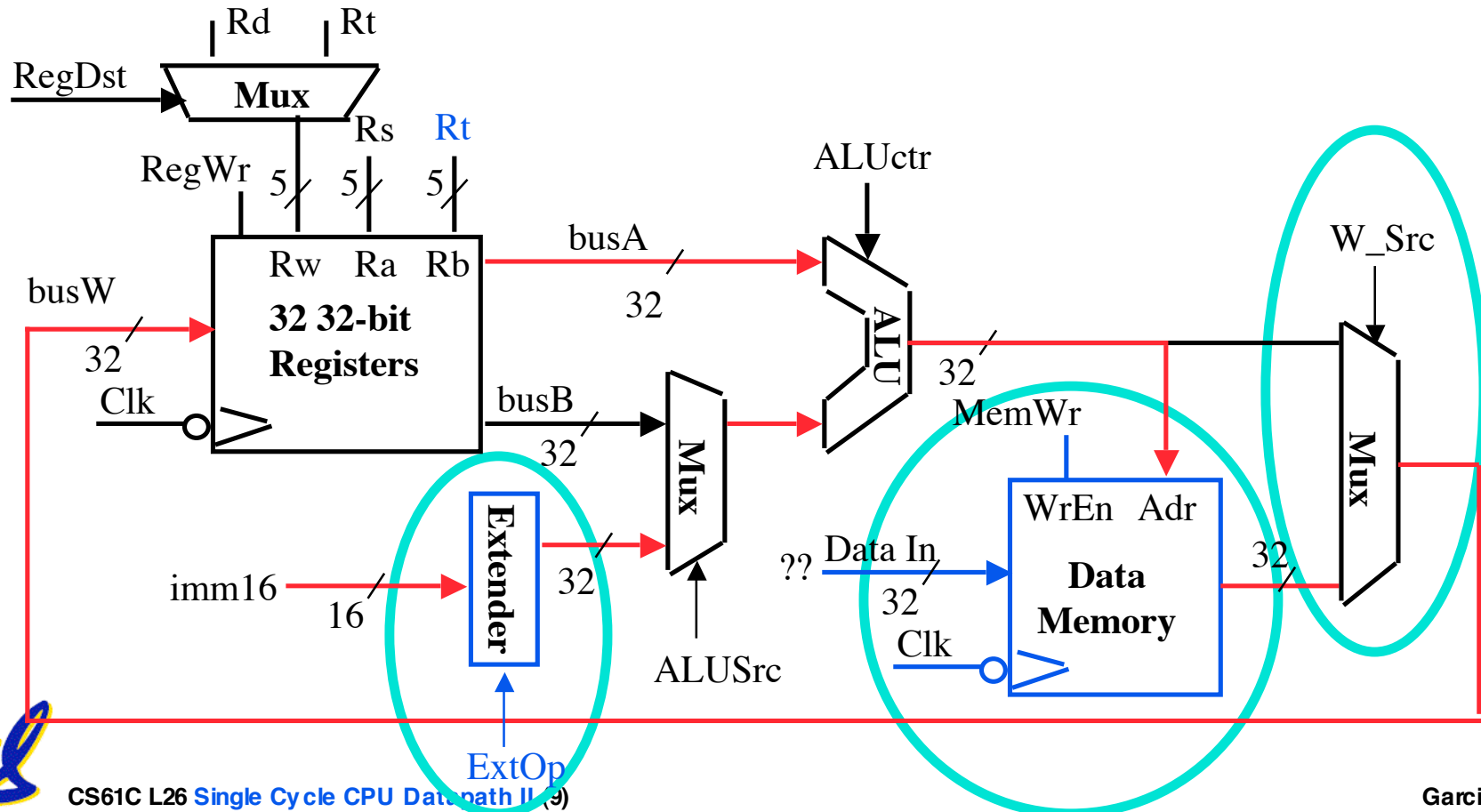 - $R[rt] = Mem[R[rs] + SignExt[imm16]]$
Example: `lw rt, rs, imm16`




3e: Store Operations

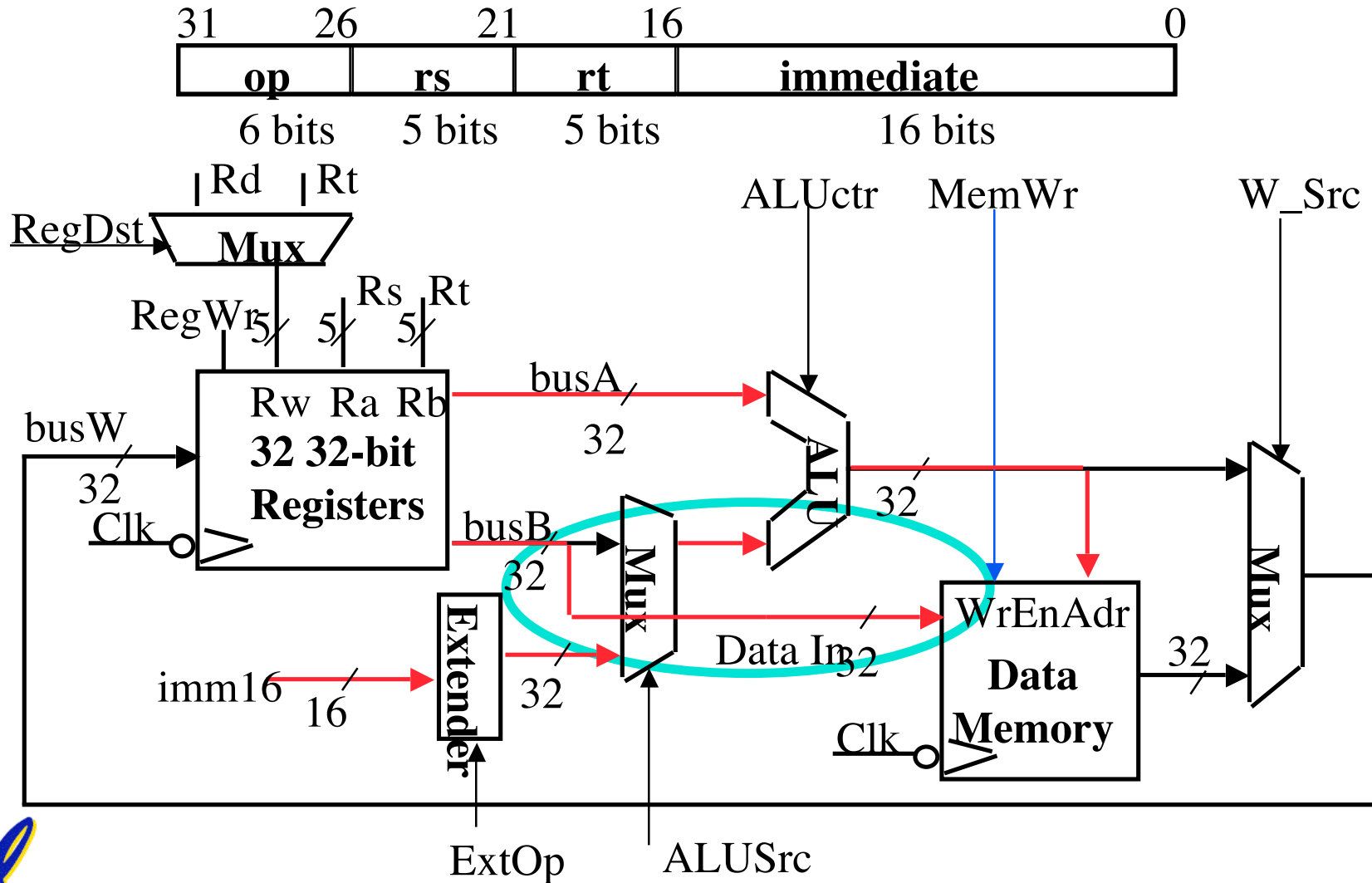- $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$
 Ex.: `sw rt, rs, imm16`



3f: The Branch Instruction

 



- **beq rs, rt, imm16**
 - **mem[PC]** Fetch the instruction from memory
 - **Equal = R[rs] == R[rt]** Calculate branch condition
 - **if (Equal)** Calculate the next instruction's address
 - **PC = PC + 4 + (SignExt(imm16) x 4)**
 - else**
 - **PC = PC + 4**



Datapath for Branch Operations

- **beq** rs, rt, imm16


Datapath generates condition (equal)

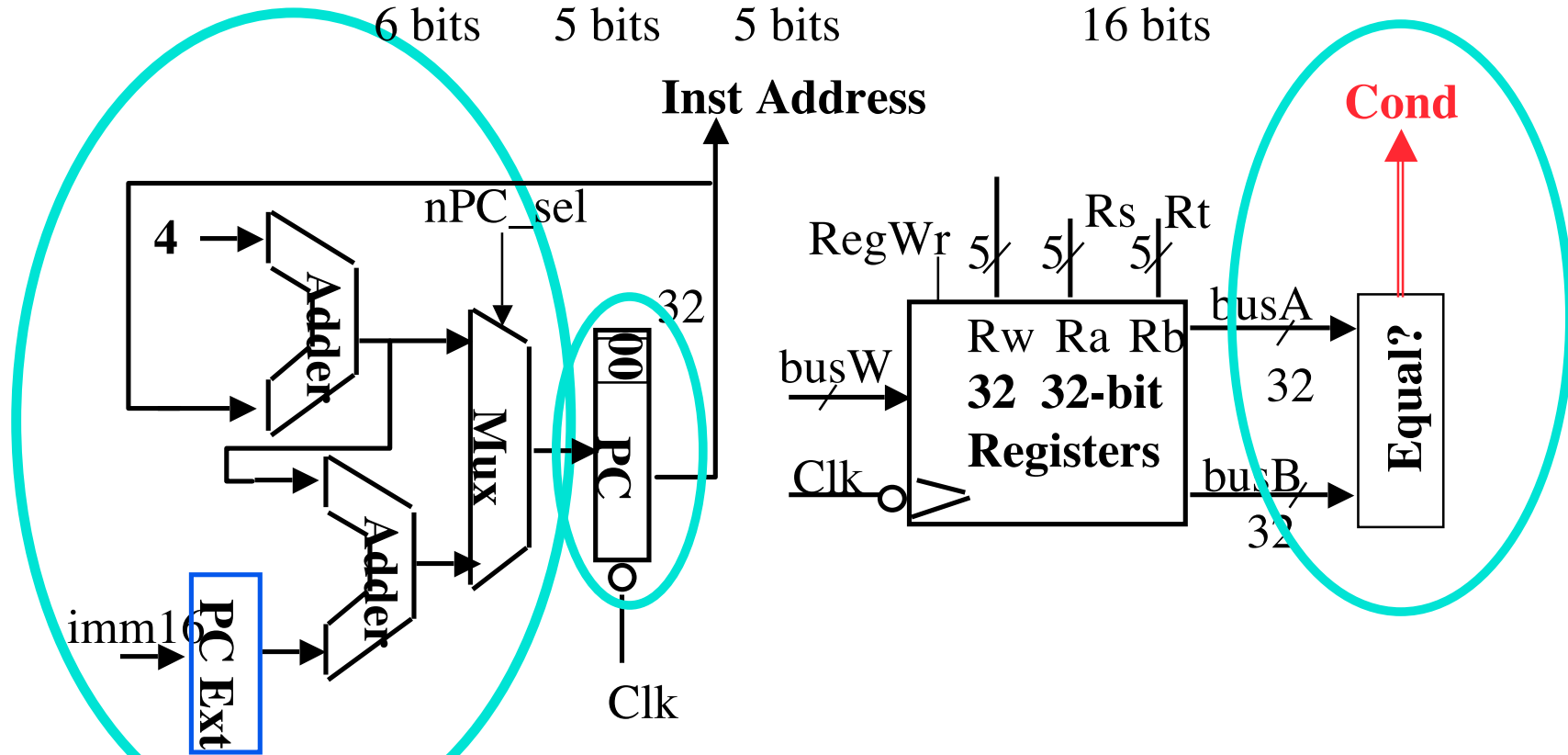 


• **Already MUX, adder, sign extend, zero**



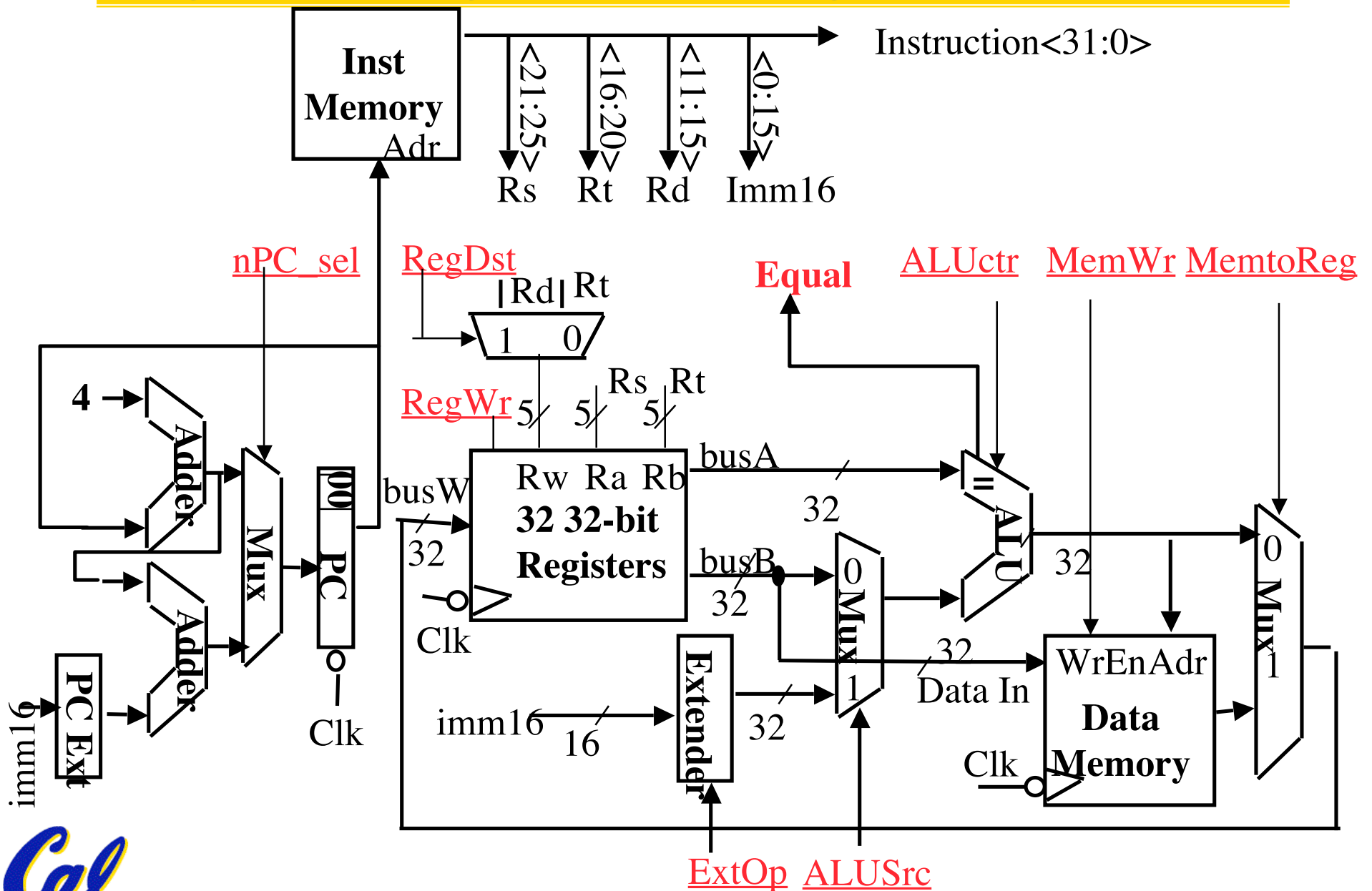Putting it All Together: A Single Cycle Datapath



An Abstract View of the Implementation

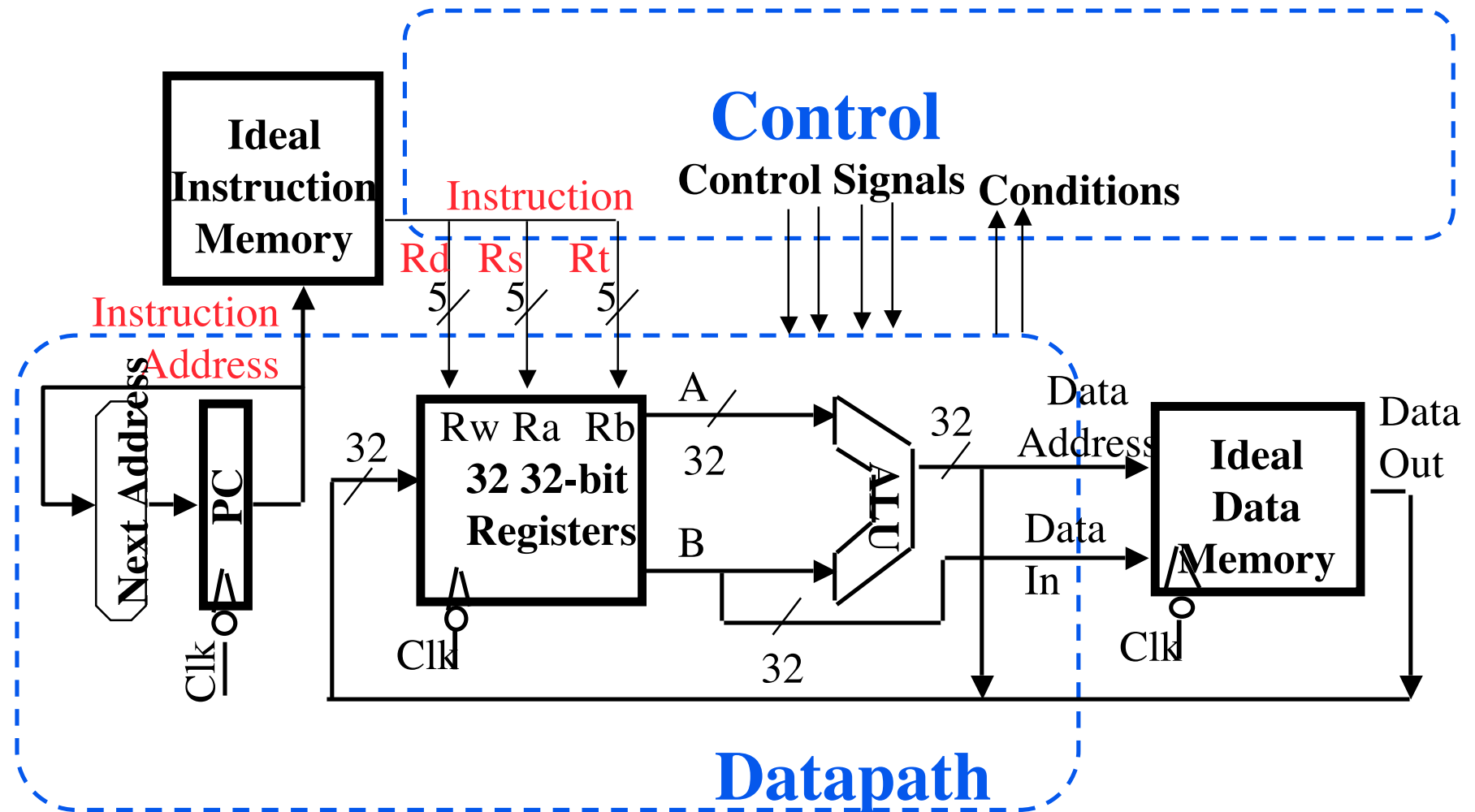

Peer Instruction

- A. Our **ALU** is a synchronous device
- B. We **could** have used **tri-state devices** instead of a MUX to feed busW, the register write data line
- C. The **ALU is inactive** for memory reads or writes.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Summary: Single cycle datapath

- **5 steps to design a processor**
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic
- **Control is the hard part**
- **Next time!**

