

**Lecture 27 –
 Single Cycle CPU Control I**



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia


Brain-computer interfaces! ⇒

Paralyzed people can now control artificial limbs! There are two brain connection techniques, implants requiring significant surgery (& brain inflammation) and the non-invasive “swimming cap”. You adapt to either.



Summary: A Single Cycle Datapath

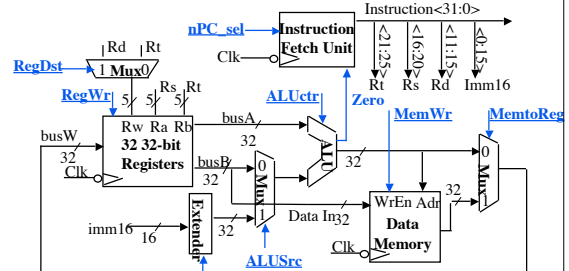
- Rs, Rt, Rd, Imed16 connected to datapath
- We have everything except **control signals**



An Abstract View of the Critical Path


- This affects how much you can overclock your PC!

 Critical Path (Load Operation) =
 Delay clock through PC (FFs) +
 Instruction Memory's Access Time +
 Register File's Access Time, +
 ALU to Perform a 32-bit Add +
 Data Memory Access Time +
 Stable Time for Register File Write




Recap: Meaning of the Control Signals

 - **nPC_MUX_sel:** 0 ⇒ PC ← PC + 4
 1 ⇒ PC ← PC + 4 + {SignExt(Im16), 00}
 “n”=next
- Later in lecture: higher-level connection between mux and branch cond



Recap: Meaning of the Control Signals

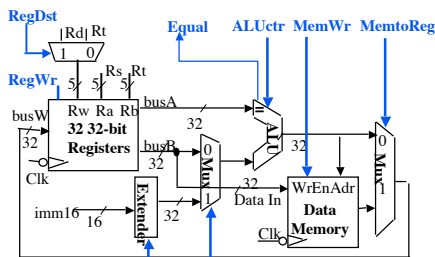
- **ExtOp:** “zero”, “sign”
- **ALUsrc:** 0 ⇒ regB; 1 ⇒ immed
- **ALUctr:** “add”, “sub”, “or”
- **MemWr:** 1 ⇒ write memory
- **MemtoReg:** 0 ⇒ ALU; 1 ⇒ Mem
- **RegDst:** 0 ⇒ “rt”; 1 ⇒ “rd”
- **RegWr:** 1 ⇒ write register



Administrivia

- Steven & Andy moved today’s OH to 11-noon before lecture

RTL: The Add Instruction

 

add rd, rs, rt

- MEM[PC] Fetch the instruction from memory
- R[rd] = R[rs] + R[rt] The actual operation
- PC = PC + 4 Calculate the next instruction's address




CS61C L27 Single Cycle CPU Control (7)

Garcia, Fall 2004 © UCB

Instruction Fetch Unit at the Beginning of Add

Fetch the instruction from Instruction memory: Instruction = MEM[PC]


same for all instructions

 


CS61C L27 Single Cycle CPU Control (8)

Garcia, Fall 2004 © UCB

The Single Cycle Datapath during Add

 

R[rd] = R[rs] + R[rt]

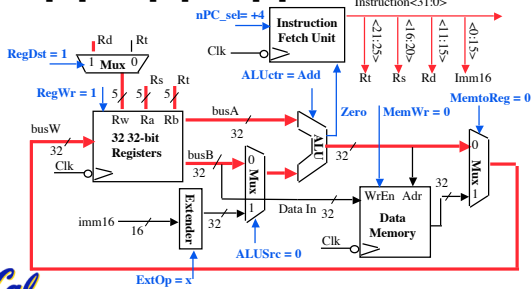


CS61C L27 Single Cycle CPU Control (9)

Garcia, Fall 2004 © UCB

Instruction Fetch Unit at the End of Add

PC = PC + 4

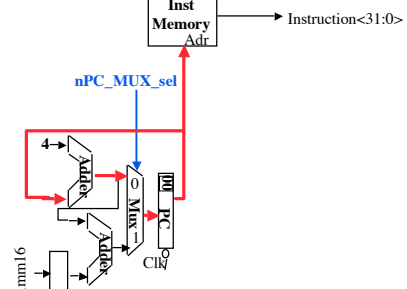
This is the same for all instructions except: Branch and Jump




CS61C L27 Single Cycle CPU Control (10)

Garcia, Fall 2004 © UCB

 Single Cycle Datapath during Or Immediate?




R[rt] = R[rs] OR ZeroExt[Imm16]

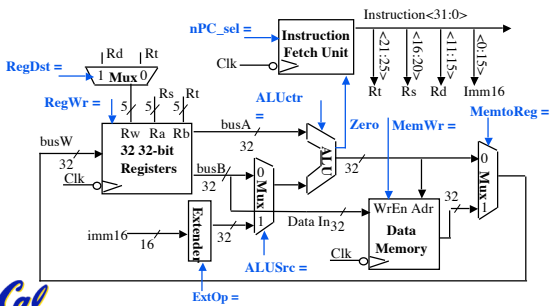


CS61C L27 Single Cycle CPU Control (11)

Garcia, Fall 2004 © UCB

 Single Cycle Datapath during Or Immediate?




R[rt] = R[rs] OR ZeroExt[Imm16]

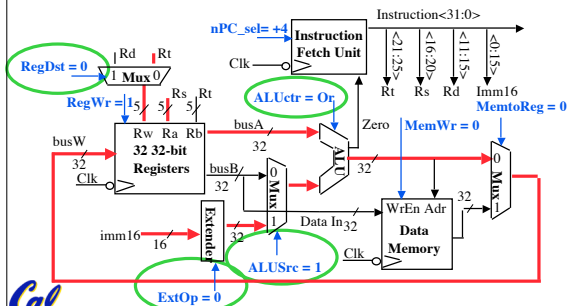


CS61C L27 Single Cycle CPU Control (12)

Garcia, Fall 2004 © UCB


The Single Cycle Datapath during Load?

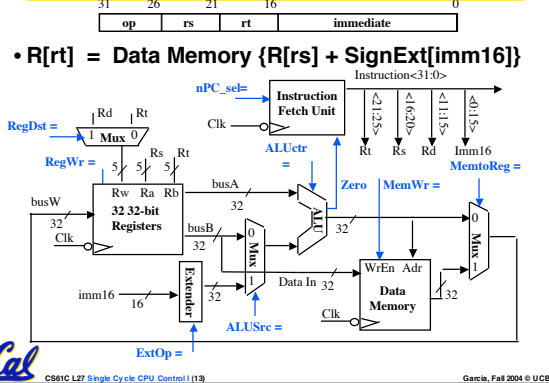


The Single Cycle Datapath during Load

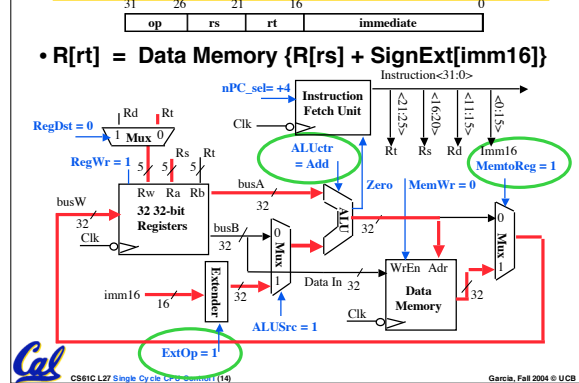


The Single Cycle Datapath during Store?

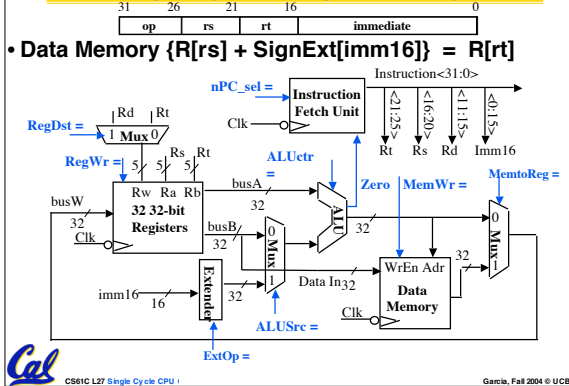


The Single Cycle Datapath during Store

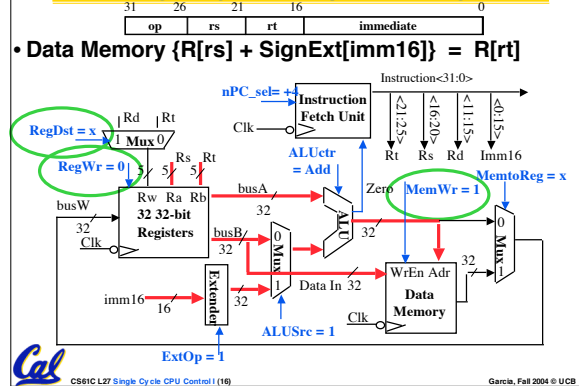


The Single Cycle Datapath during Branch?

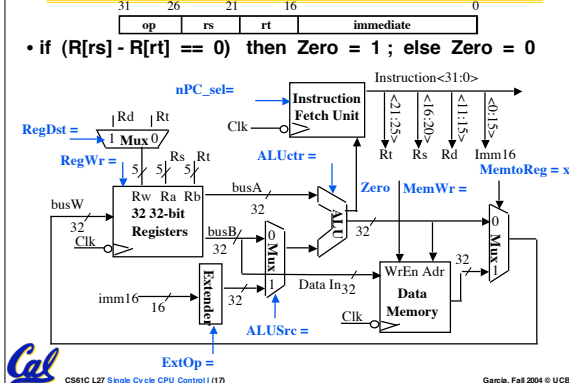


The Single Cycle Datapath during Branch

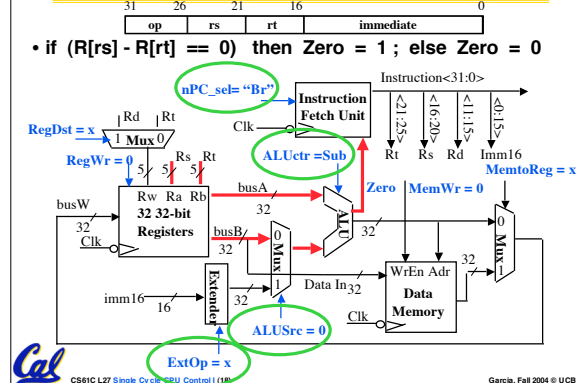

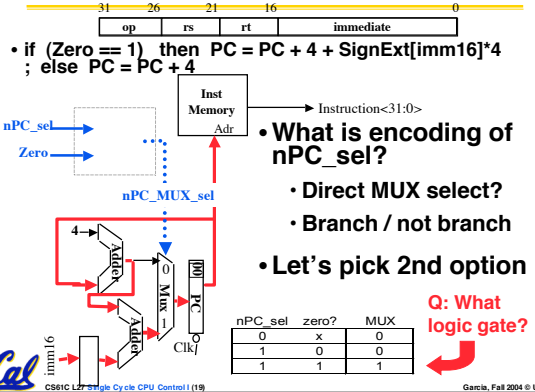Instruction Fetch Unit at the End of Branch



Step 4: Given Datapath: RTL -> Control

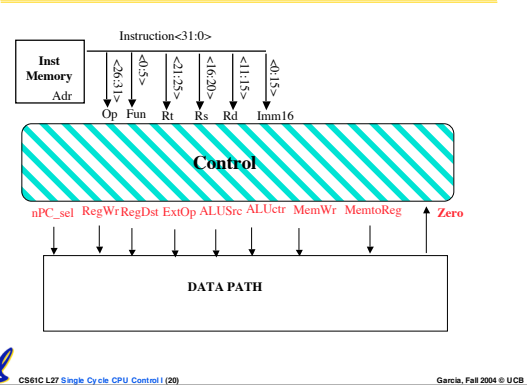

A Summary of the Control Signals (1/2)

inst. Register Transfer

ADD R[rd] ← R[rs] + R[rt]; PC ← PC + 4
ALUSrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"

SUB R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ALUSrc = RegB, ALUctr = "sub", RegDst = rd, RegWr, nPC_sel = "+4"

ORI R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4
ALUSrc = Im, Extop = "Z", ALUctr = "or", RegDst = rt, RegWr, nPC_sel = "+4"

LOAD R[rt] ← MEM[R[rs] + sign_ext(Imm16)]; PC ← PC + 4
ALUSrc = Im, Extop = "Sn", ALUctr = "add", MemtoReg, RegDst = rt, RegWr, nPC_sel = "+4"

STORE MEM[R[rs] + sign_ext(Imm16)] ← R[rs]; PC ← PC + 4
ALUSrc = Im, Extop = "Sn", ALUctr = "add", MemWr, nPC_sel = "+4"

BEQ if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) || 00 else PC ← PC + 4
nPC_sel = "Br", ALUctr = "sub"

A Summary of the Control Signals (2/2)

See Appendix A

func	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
add	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
sub							
ori							
lw							
sw							
beq							
jump							
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	0
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx

R-type: op rs rt rd shamt funct add, sub
I-type: op rs rt immediate ori, lw, sw, beq
J-type: op target address jump

Peer Instruction

- A. Our ALU is a synchronous device
- B. We could have used tri-state devices instead of a MUX to feed busW, the register write data line
- C. The ALU is inactive for memory reads or writes.

ABC
1: FFF
2: FFT
3: FTF
4: FTT
5: TFF
6: TFT
7: TTF
8: TTT

Summary: Single cycle datapath

- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic
- Control is the hard part
- MIPS makes that easier
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates

