

inst.eecs.berkeley.edu/~cs61c
CS61C : Machine Structures

**Lecture 27 –
Single Cycle CPU Control I**



Lecturer PSOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia


Brain-computer interfaces! ⇒

Paralyzed people can now control artificial limbs! There are two brain connection techniques, implants requiring significant surgery (& brain inflammation) and the non-invasive “swimming cap”. You adapt to either.



Summary: A Single Cycle Datapath

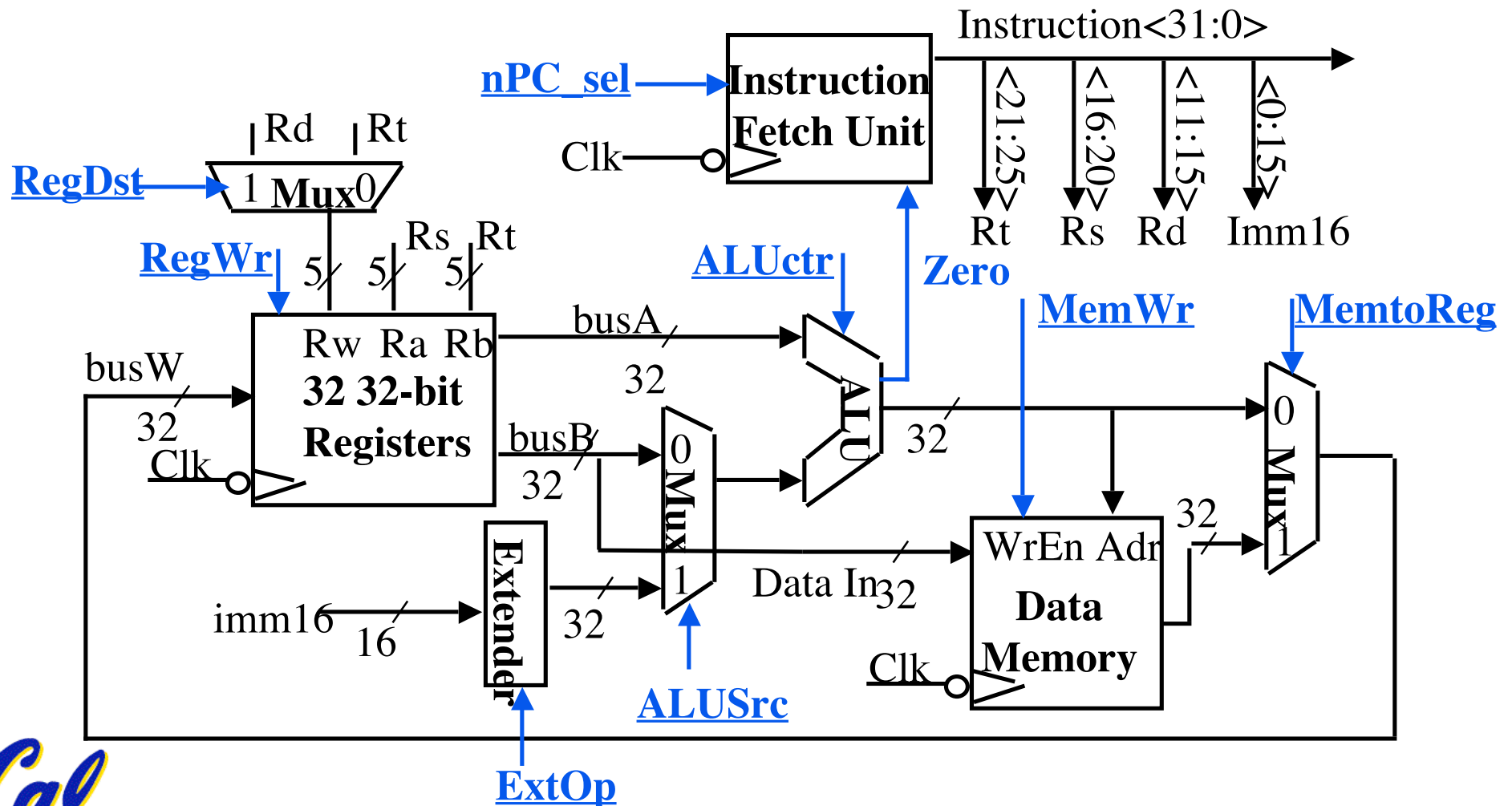
- Rs, Rt, Rd, Imed16 connected to datapath
- We have everything except control signals



An Abstract View of the Critical Path


- This affects how much you can overclock your PC!

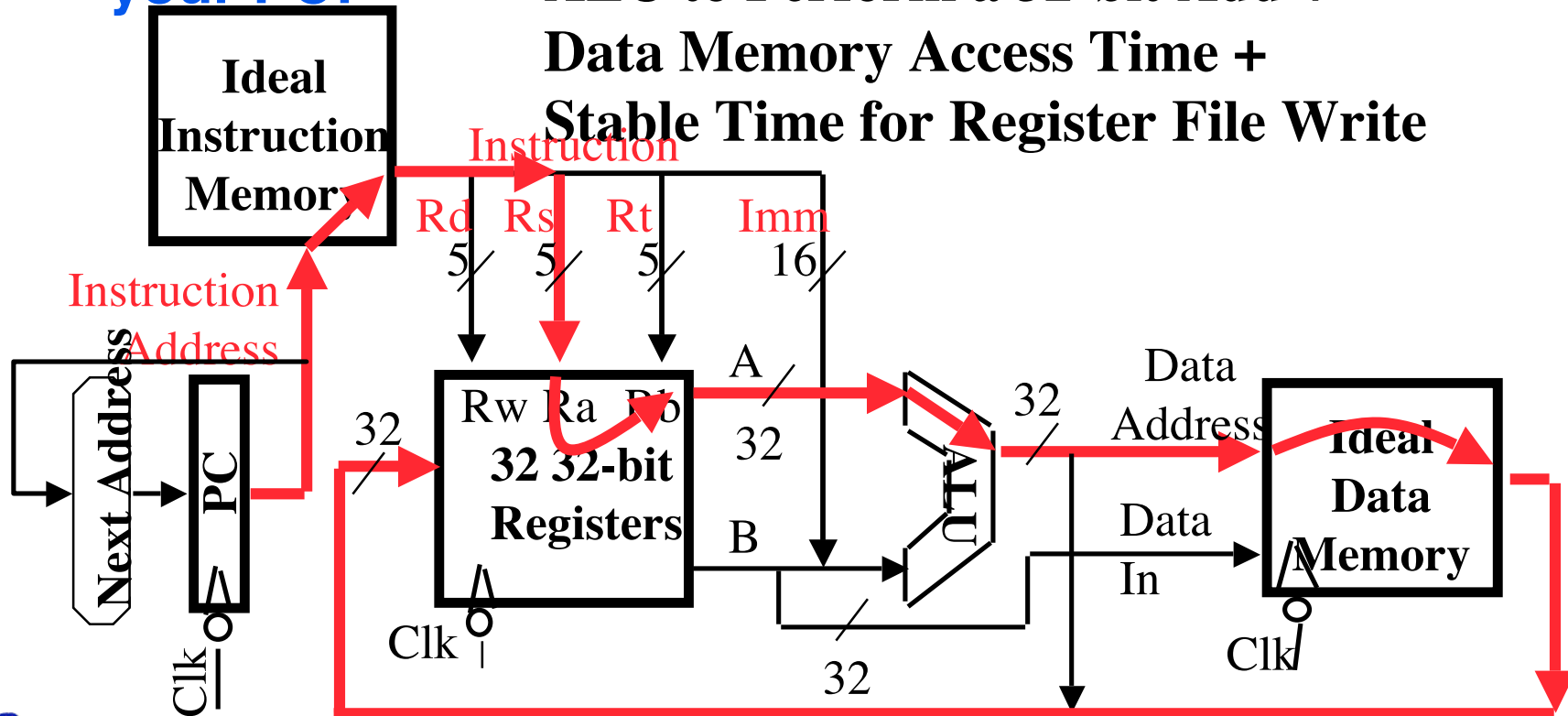Critical Path (Load Operation) =
 Delay clock through PC (FFs) +
 Instruction Memory's Access Time +
 Register File's Access Time, +
 ALU to Perform a 32-bit Add +
 Data Memory Access Time +
 Stable Time for Register File Write




Recap: Meaning of the Control Signals

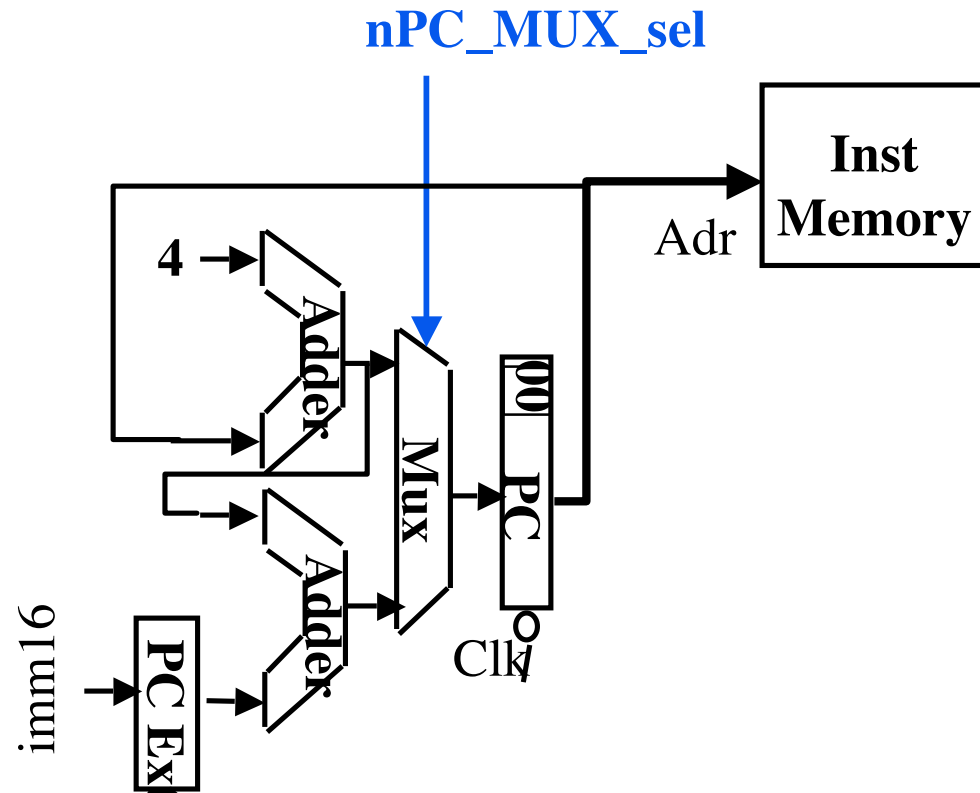- **nPC_MUX_sel:** 0 \Rightarrow PC \leftarrow PC + 4
 1 \Rightarrow PC \leftarrow PC + 4 +
 {SignExt(Im16), 00 }
- Later in lecture: higher-level connection between mux and branch cond



Recap: Meaning of the Control Signals

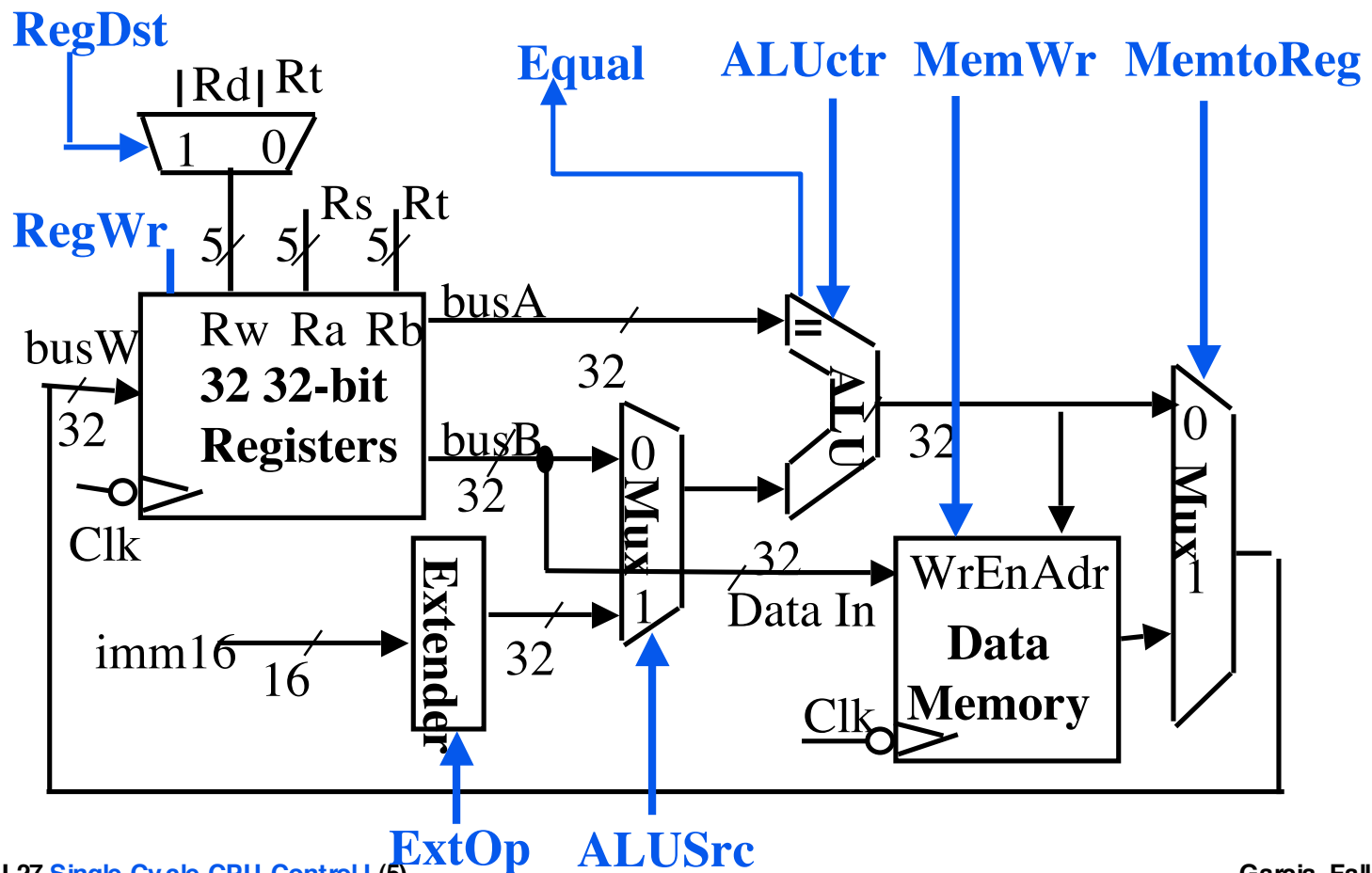- **ExtOp:** “zero”, “sign”
- **ALUsrc:** 0 \Rightarrow regB;
1 \Rightarrow immed
- **ALUctr:** “add”, “sub”, “or”
- **MemWr:** 1 \Rightarrow write memory
- **MemtoReg:** 0 \Rightarrow ALU; 1 \Rightarrow Mem
- **RegDst:** 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- **RegWr:** 1 \Rightarrow write register




Administrivia

- **Steven & Andy moved today's OH to 11-noon before lecture**



RTL: The Add Instruction

 

add rd, rs, rt


- **MEM[PC]** **Fetch the instruction from memory**
- **$R[rd] = R[rs] + R[rt]$** **The actual operation**
- **$PC = PC + 4$** **Calculate the next instruction's address**




Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory: $\text{Instruction} = \text{MEM}[\text{PC}]$


- same for all instructions

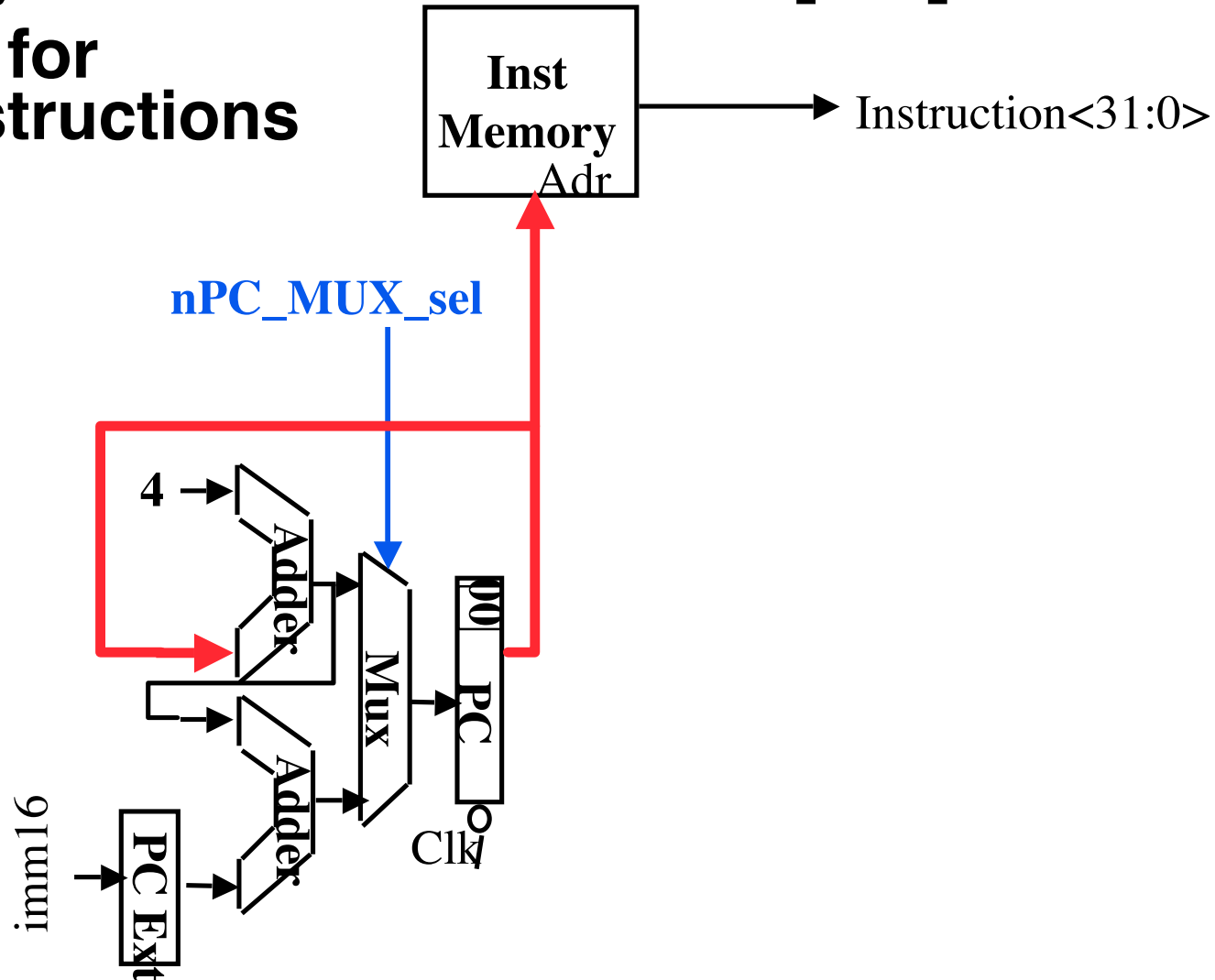

The Single Cycle Datapath during Add

 


• $R[rd] = R[rs] + R[rt]$

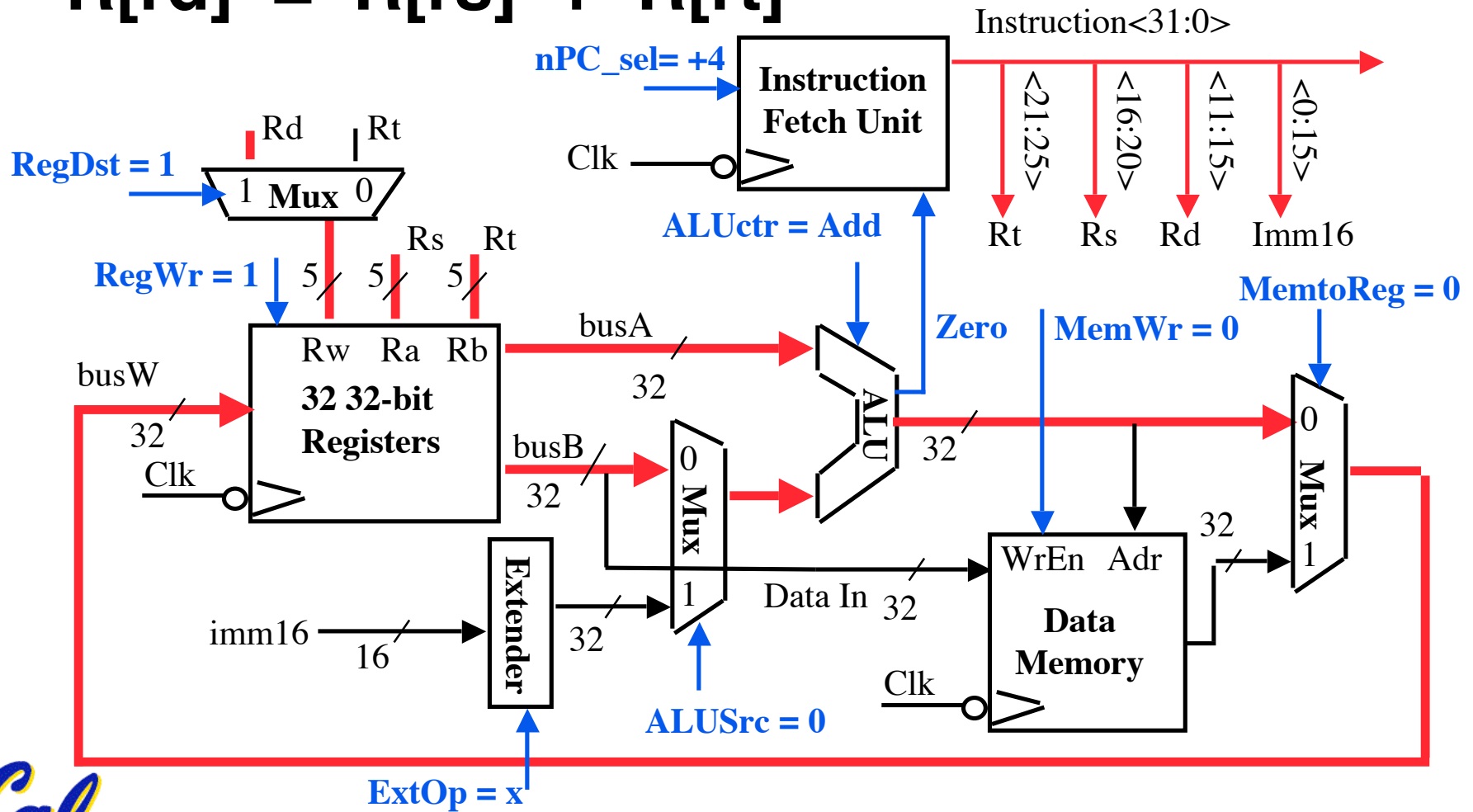


Instruction Fetch Unit at the End of Add

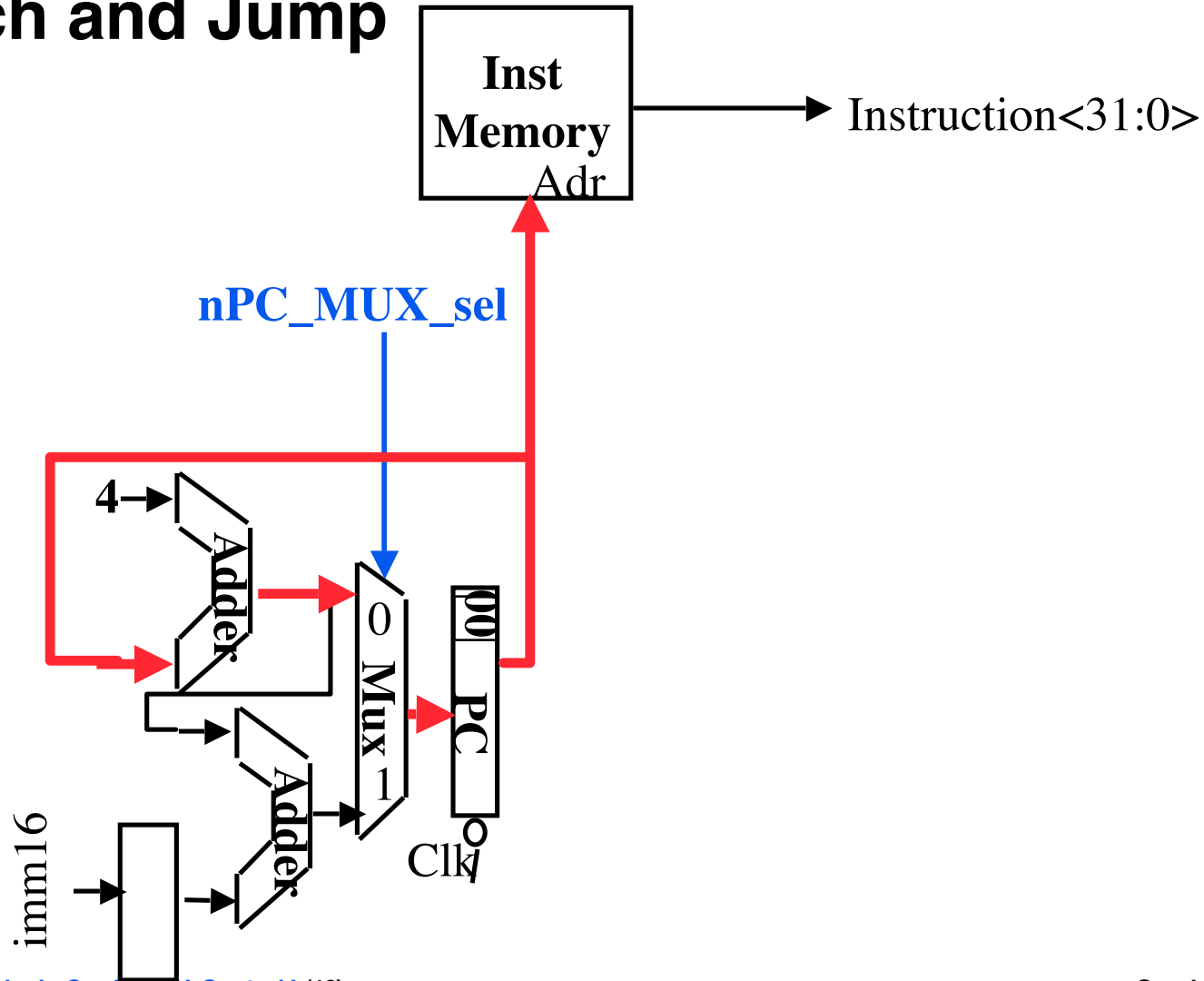
- **PC = PC + 4**
 - This is the same for all instructions except:
Branch and Jump



 
Single Cycle Datapath during Or Immediate?



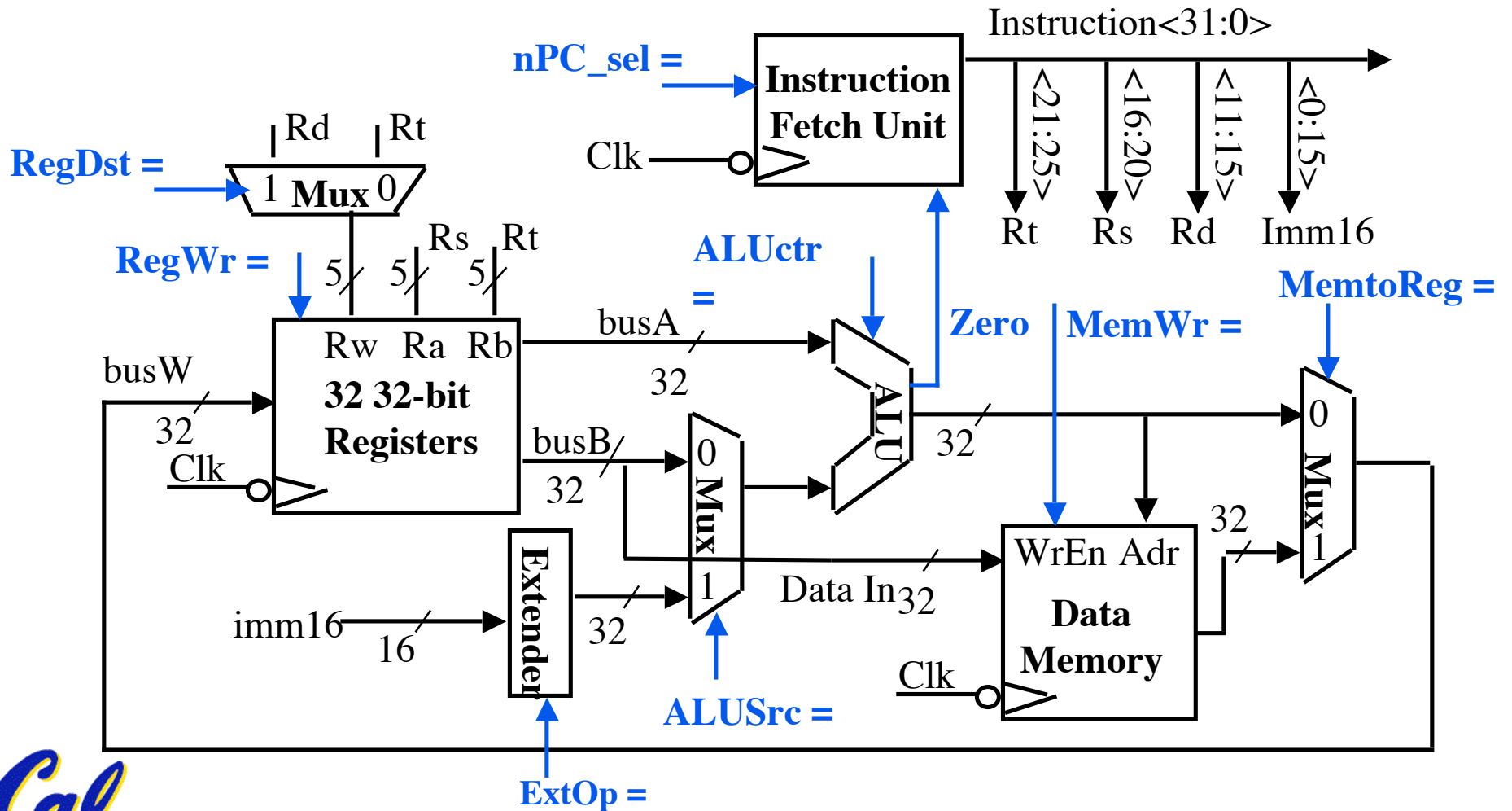
• $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$



 
Single Cycle Datapath during Or Immediate?



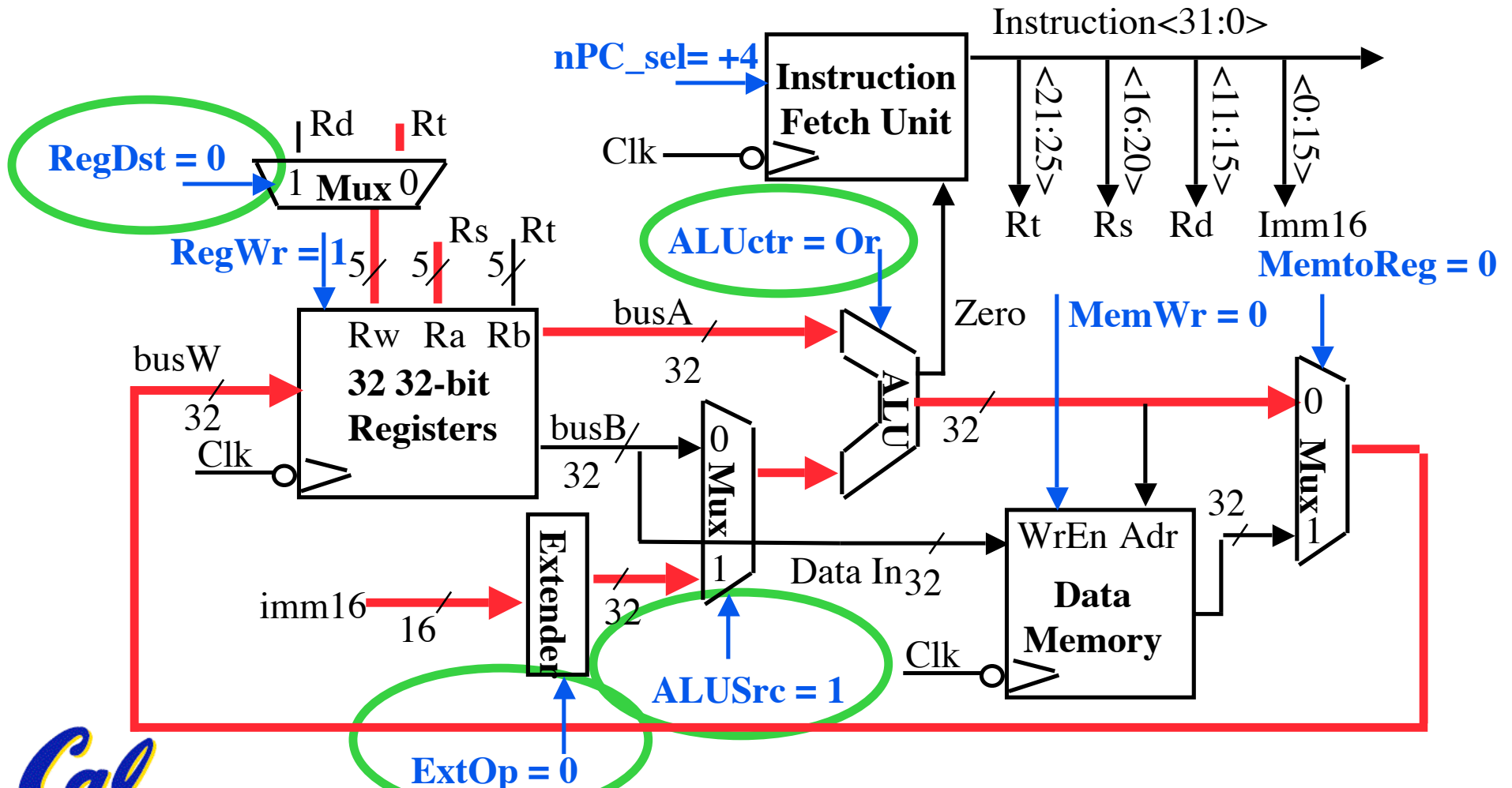
• $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




The Single Cycle Datapath during Load?

 

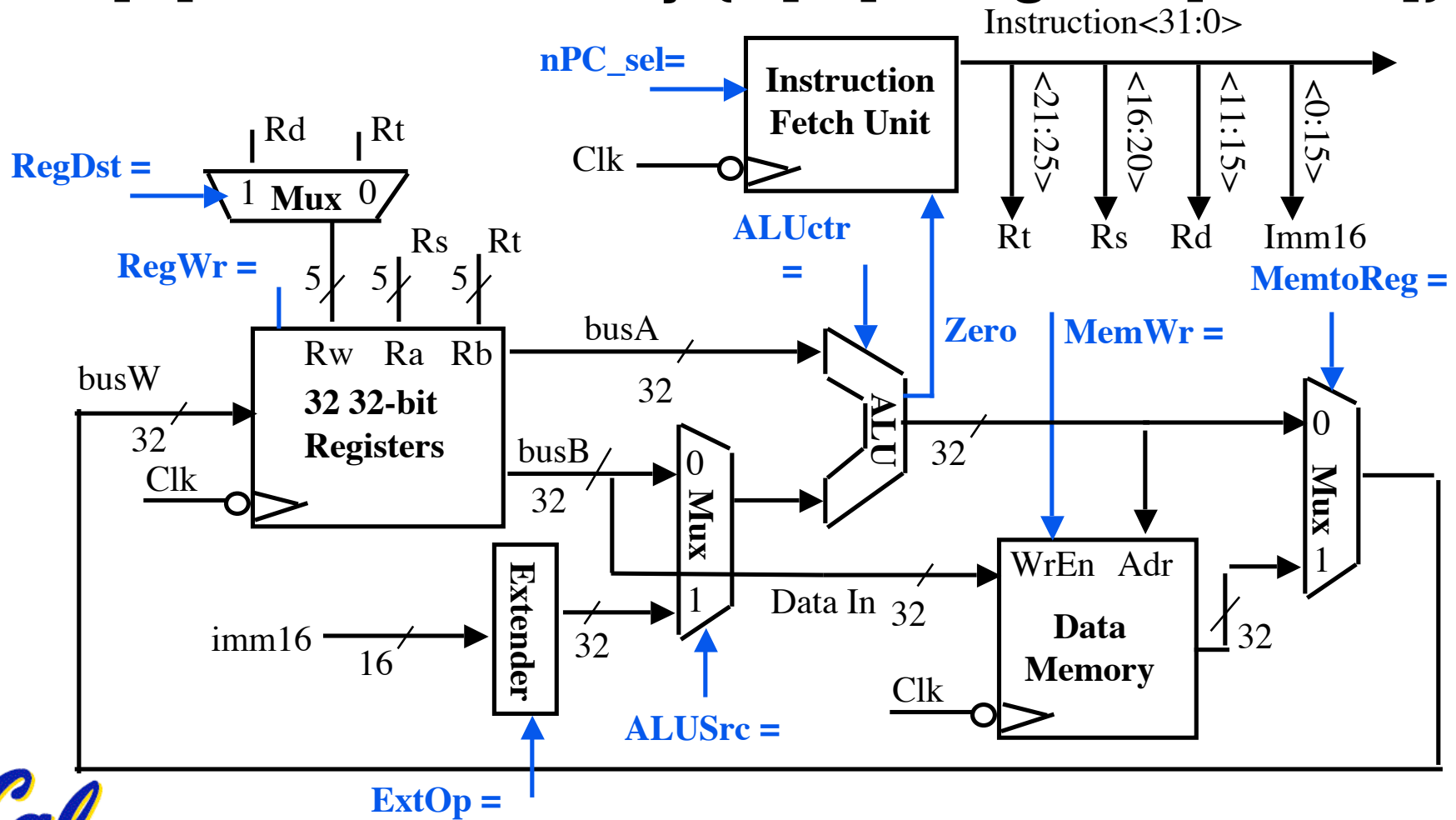
- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[imm16]\}$




The Single Cycle Datapath during Load

 

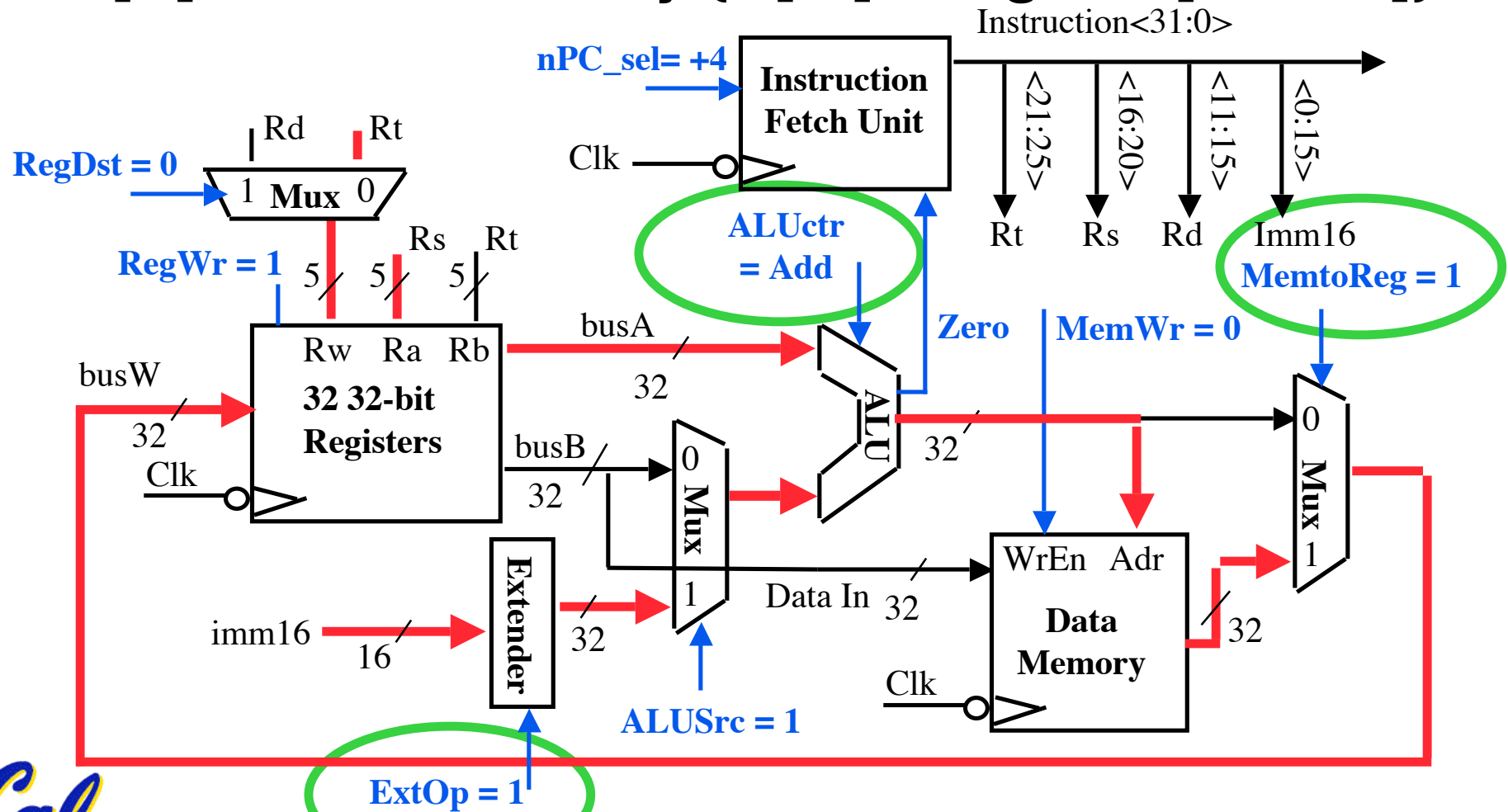
- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




The Single Cycle Datapath during Store?

 

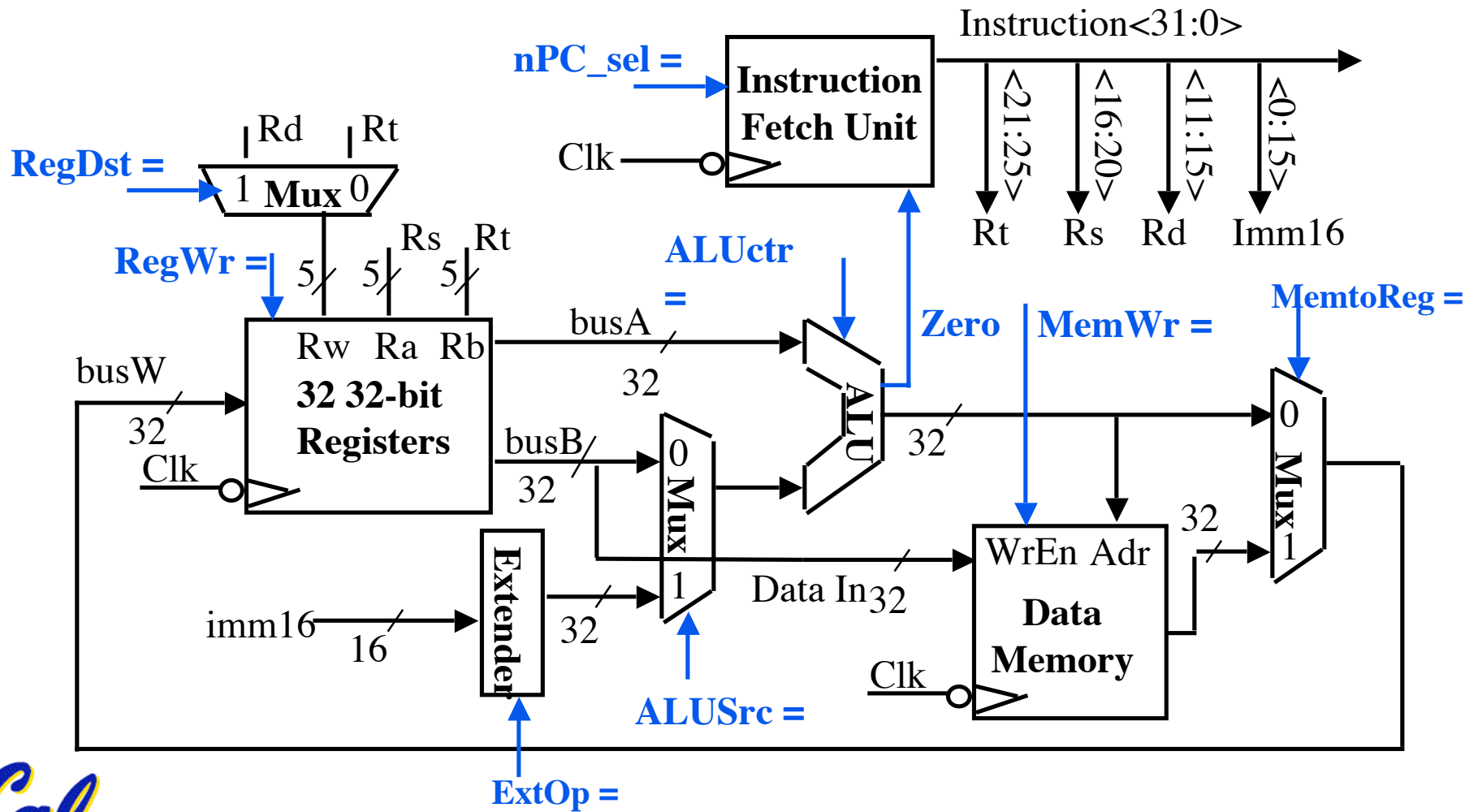
- Data Memory {R[rs] + SignExt[imm16]} = R[rt]




The Single Cycle Datapath during Store

 

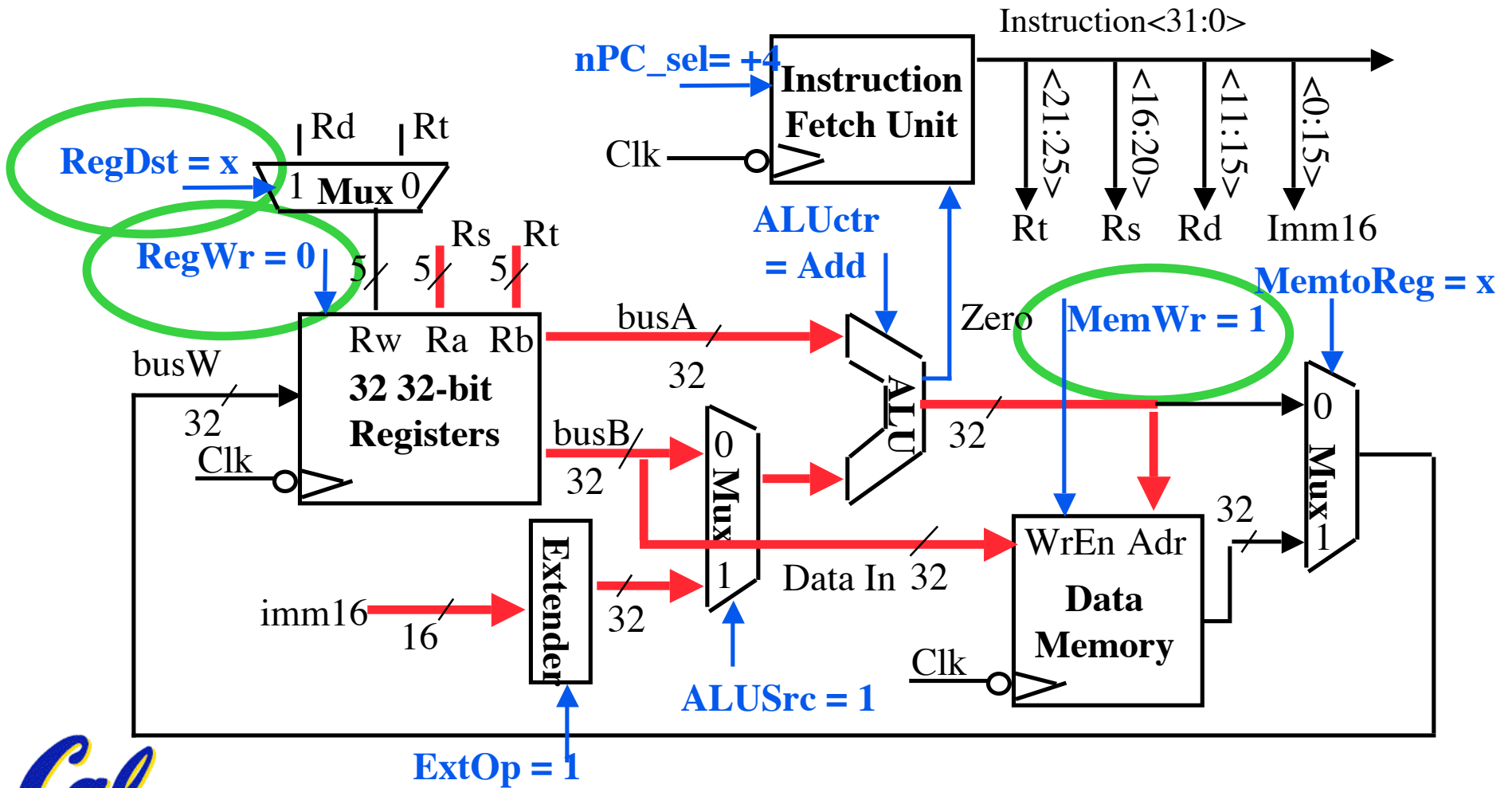
- Data Memory {R[rs] + SignExt[imm16]} = R[rt]




The Single Cycle Datapath during Branch?

 

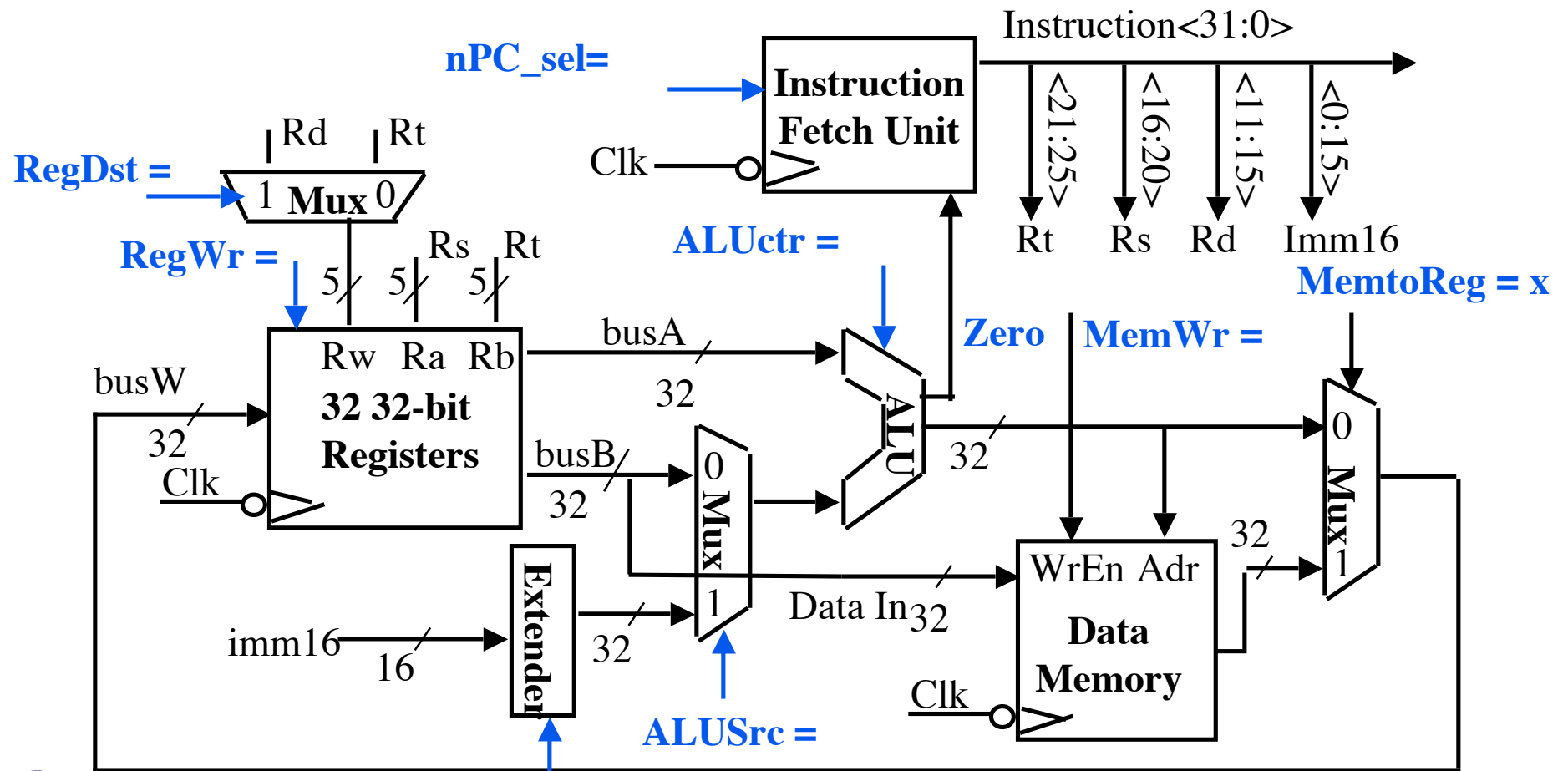
- if $(R[rs] - R[rt] == 0)$ then Zero = 1 ; else Zero = 0




The Single Cycle Datapath during Branch

 

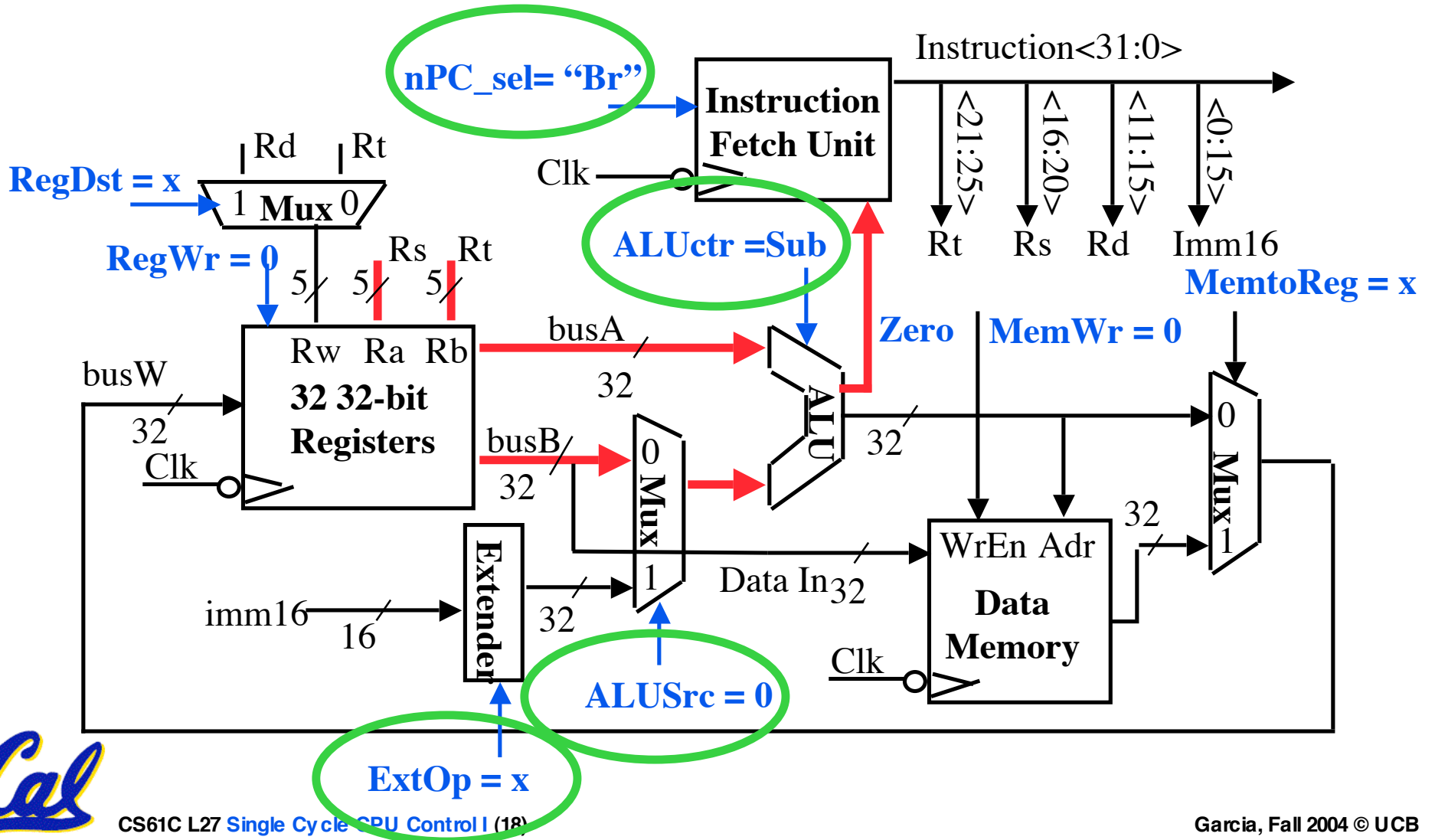
- if $(R[rs] - R[rt] == 0)$ then Zero = 1 ; else Zero = 0



 Instruction Fetch Unit at the End of Branch



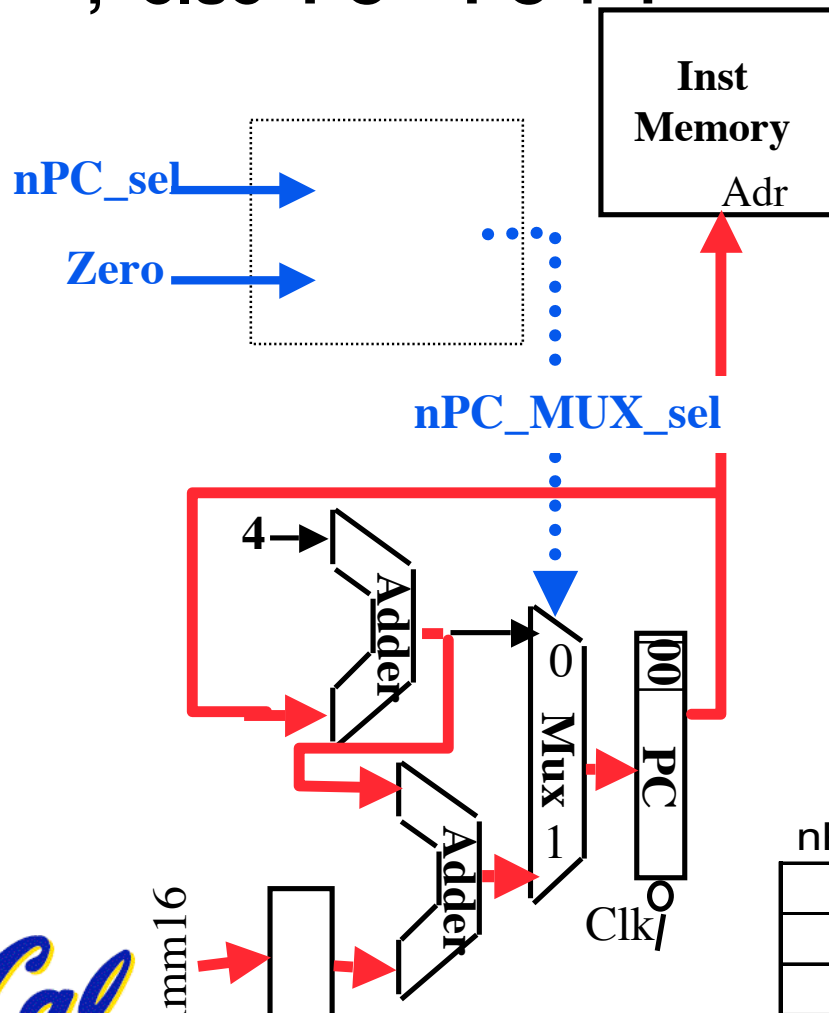- if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$
; else $PC = PC + 4$




- What is encoding of nPC_sel?
 - Direct MUX select?
 - Branch / not branch
- Let's pick 2nd option

Q: What logic gate?

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1



Step 4: Given Datapath: RTL -> Control

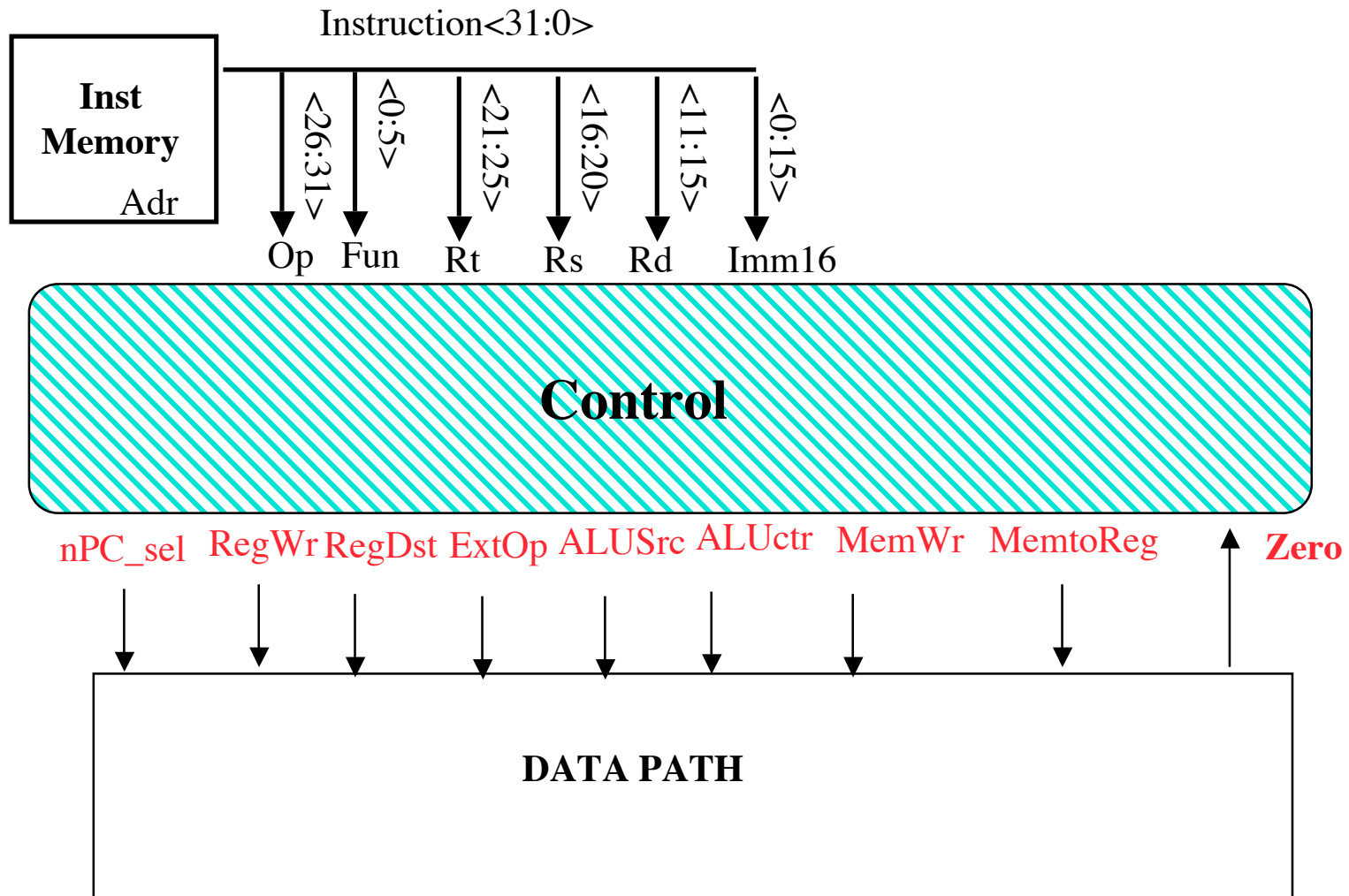

A Summary of the Control Signals (1/2)

inst Register Transfer

ADD $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = “add”, RegDst = rd, RegWr, nPC_sel = “+4”

SUB $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = “sub”, RegDst = rd, RegWr, nPC_sel = “+4”

ORi $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16});$ $PC \leftarrow PC + 4$

ALUsrc = Im, Extop = “Z”, ALUctr = “or”, RegDst = rt, RegWr, nPC_sel = “+4”

LOAD $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = “Sn”, ALUctr = “add”,
MemtoReg, RegDst = rt, RegWr, nPC_sel = “+4”**

STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$ $PC \leftarrow PC + 4$

ALUsrc = Im, Extop = “Sn”, ALUctr = “add”, MemWr, nPC_sel = “+4”

BEQ $\text{if} (R[rs] == R[rt]) \text{ then } PC \leftarrow PC + \text{sign_ext}(\text{Imm16}) \parallel 00 \text{ else } PC \leftarrow PC + 4$


nPC_sel = “Br”, ALUctr = “sub”



A Summary of the Control Signals (2/2)

See Appendix A → **func**
 → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	0
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx

 

Peer Instruction

- A. Our **ALU** is a synchronous device
- B. We **could** have used **tri-state devices** instead of a MUX to feed busW, the register write data line
- C. The **ALU is inactive** for memory reads or writes.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Summary: Single cycle datapath


◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

◦ **Control** is the hard part

◦ MIPS makes that easier

 - Instructions same size
- Source registers always in same place
- Immediates same size, location



Operations always on registers/immediates