

Lecture 28 – Single Cycle CPU Control II



Lecturer PSOE Dan Garcia


www.cs.berkeley.edu/~ddgarcia

DARPA \$s drying up...ouch! ⇒

“I'm worried and depressed,”

– David Patterson, president of the ACM.

 There is a significant shift of \$ from “Blue Sky” research to military contractors. This is a significant shift, mostly for the worse.



www.nytimes.com/2005/04/02/technology/02darpa.html?


Review: Single cycle datapath

- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic

◦ **Control** is the hard part

◦ MIPS makes that easier

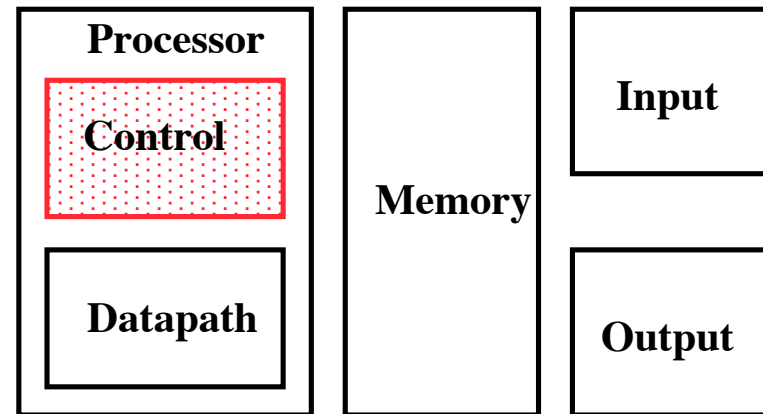- Instructions same size
- Source registers always in same place
- Immediates same size, location



Operations always on registers/immediates

A Summary of the Control Signals (2/2)

See Appendix A → **func**
 → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	0
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x


	31	26	21	16	11	6	0	
R-type	op	rs	rt	rd	shamt	funct		add, sub
I-type	op	rs	rt	immediate				ori, lw, sw, beq
J-type	op	target address						jump



The Single Cycle Datapath during Jump



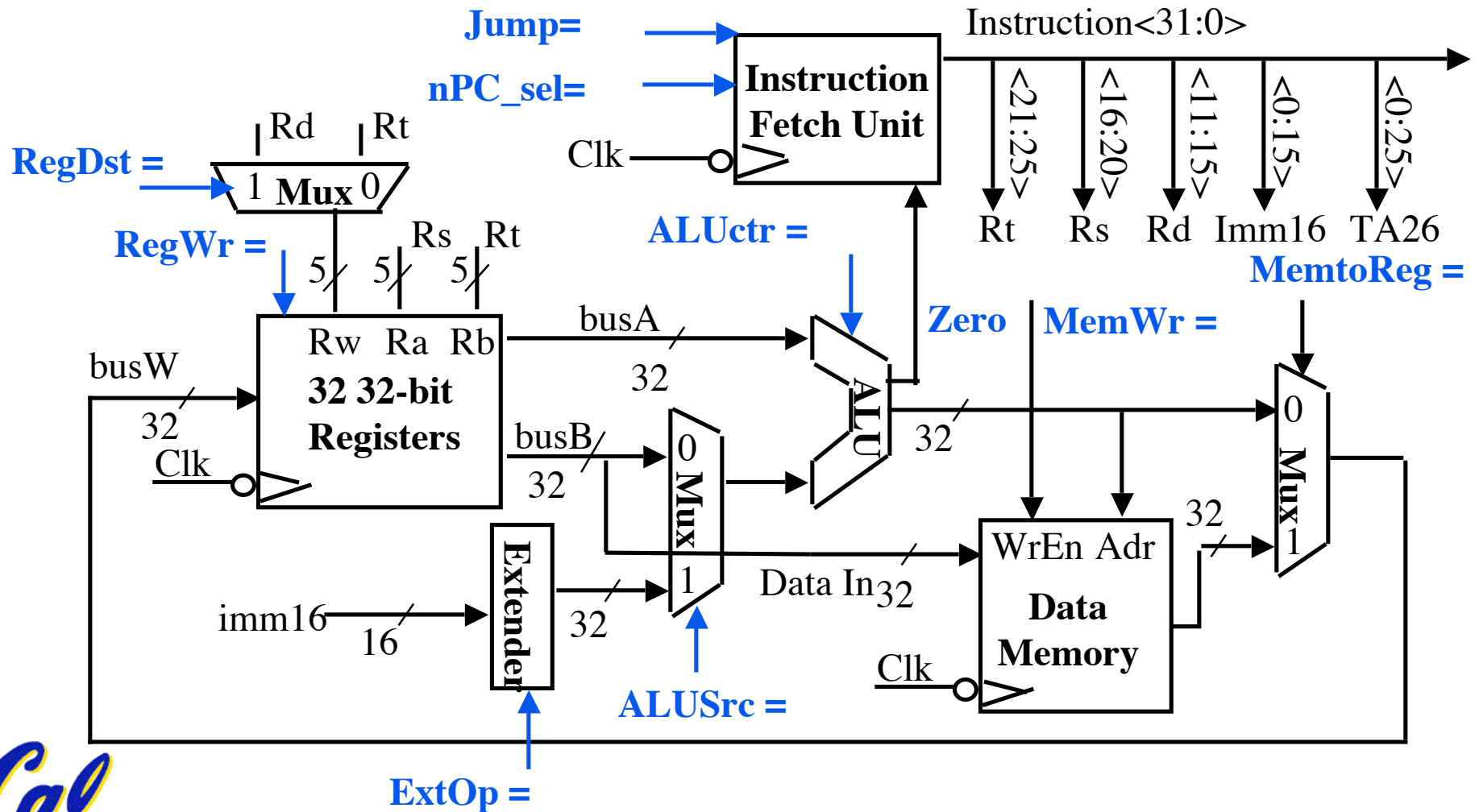
- **New PC = { PC[31..28], target address, 00 }**



The Single Cycle Datapath during Jump




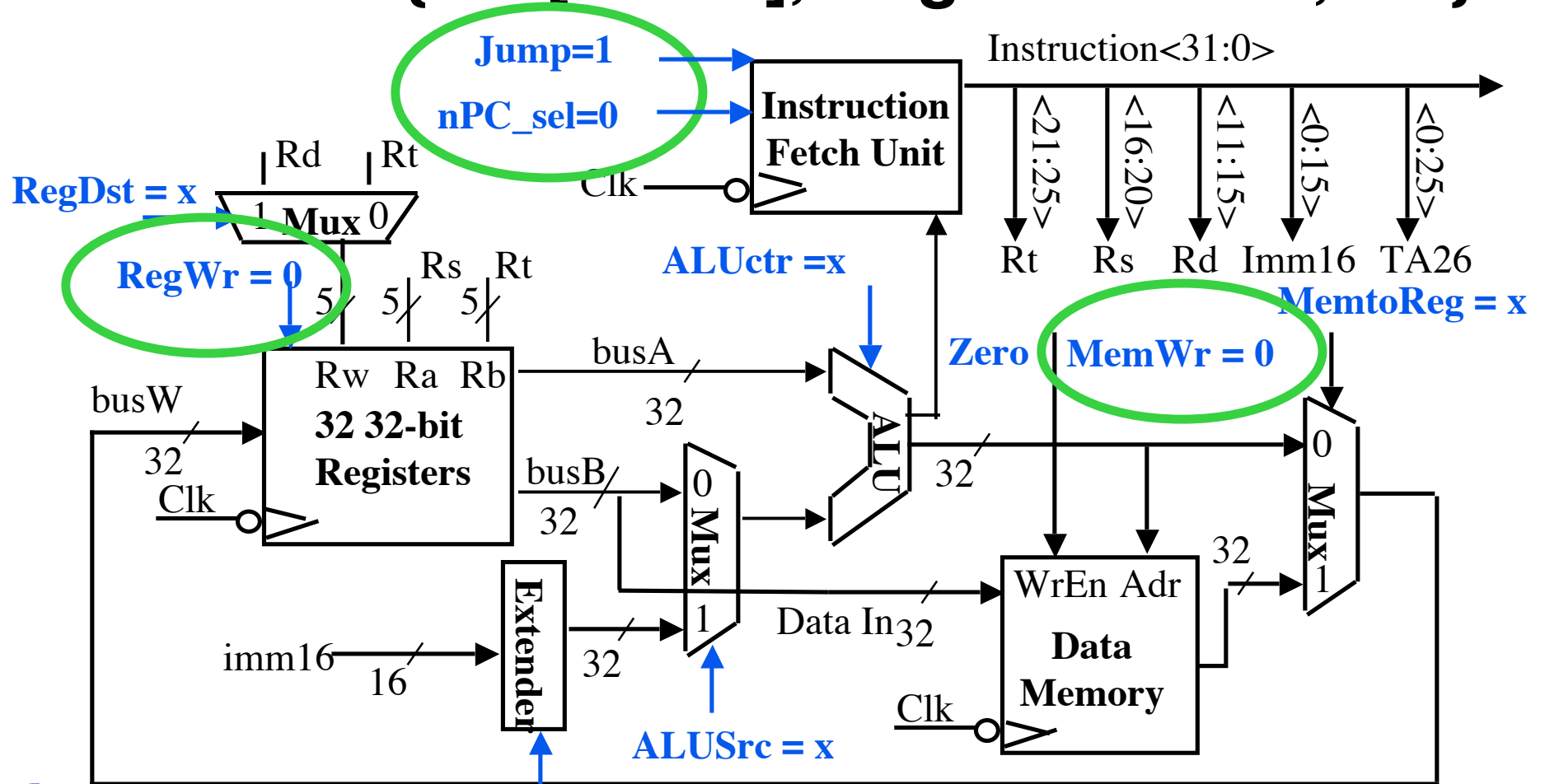
- **New PC = { PC[31..28], target address, 00 }**



Instruction Fetch Unit at the End of Jump



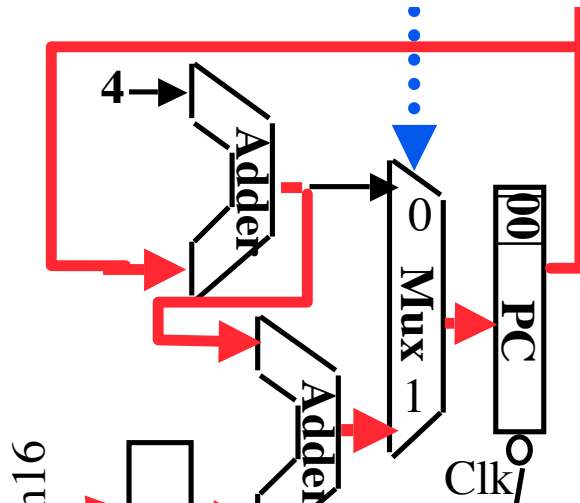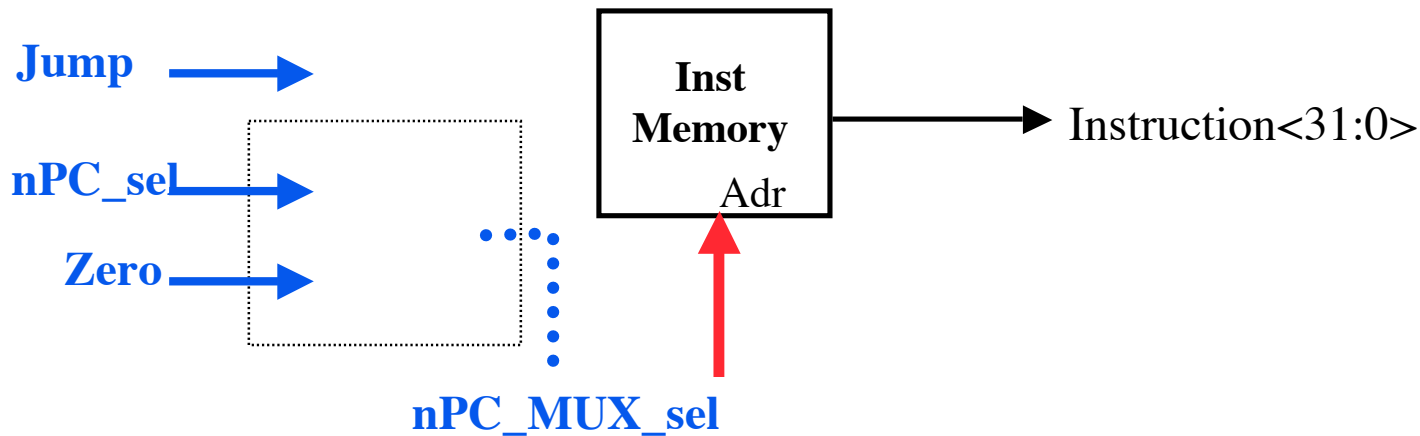• **New PC = { PC[31..28], target address, 00 }**




How do we modify this to account for jumps?



Instruction Fetch Unit at the End of Jump



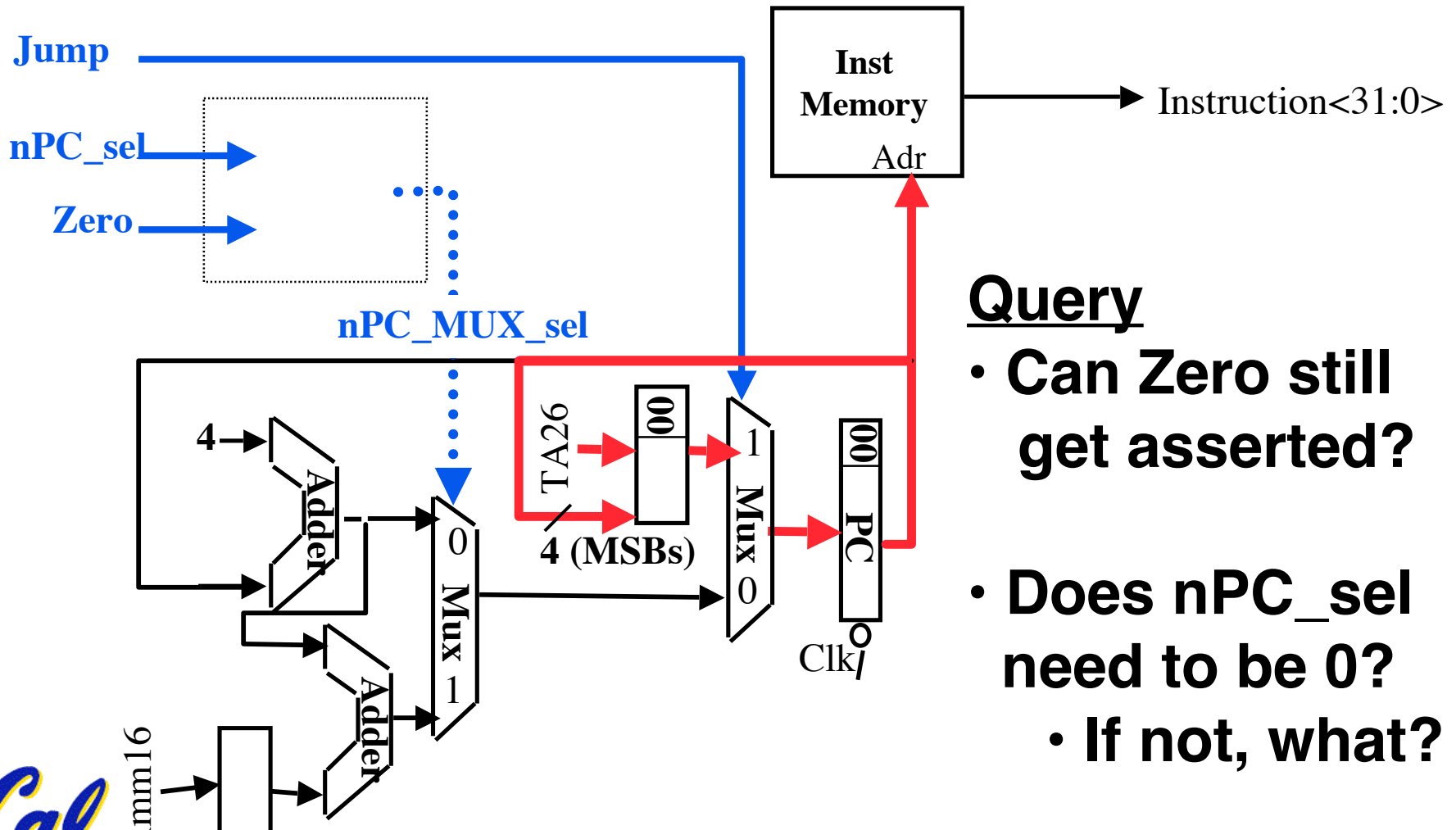• **New PC = { PC[31..28], target address, 00 }**



Query


- Can Zero still get asserted?
- Does nPC_sel need to be 0?
 - If not, what?



Build CL to implement Jump on paper now



Build CL to implement Jump on paper now

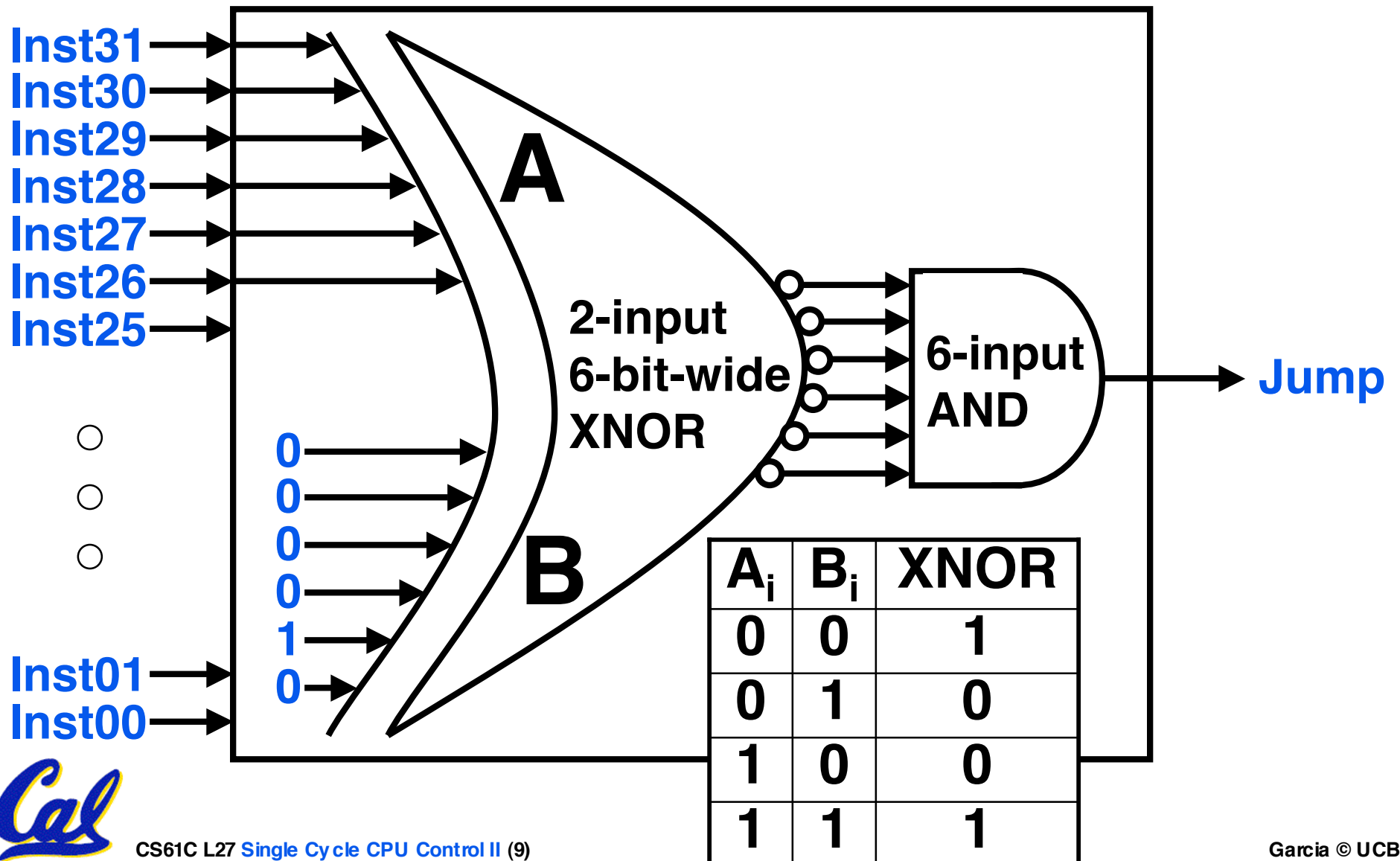



Administrivia

- **HW7 out today, due in a week**



Review: Finite State Machine (FSM)

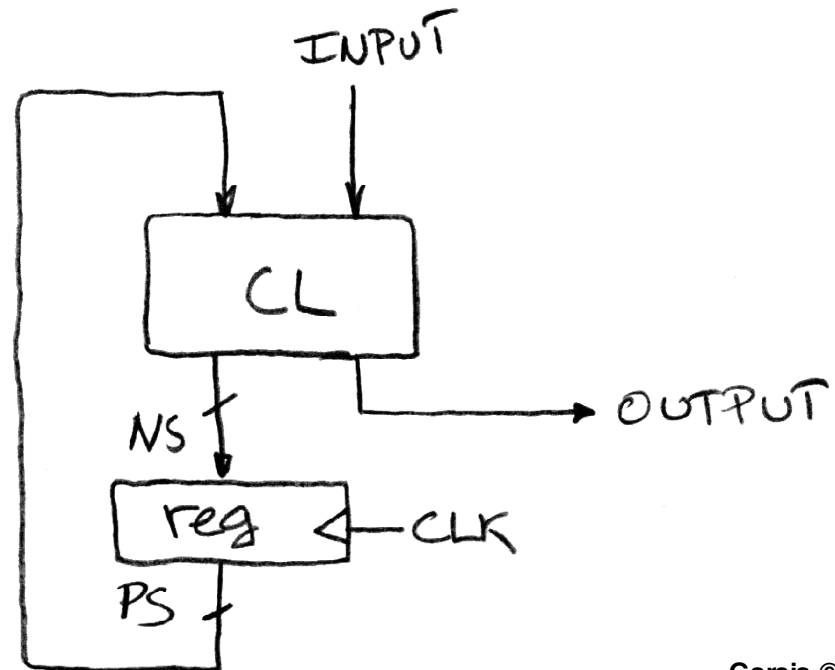 - **States** represent possible output values.
- **Transitions** represent changes between states based on inputs.
- **Implement** with CL and clocked register feedback.



Finite State Machines extremely useful!

- They define
 - How **output signals** respond to input signals and previous state.
 - How we **change states** depending on input signals and previous state
- The output signals could be our familiar **control signals**
 - Some control signals **may only depend on CL, not on state at all...**
- We could implement very detailed FSMs w/**Programmable Logic Arrays**




Taking advantage of sum-of-products

- Since sum-of-products is a convenient notation and way to think about design, offer hardware building blocks that match that notation
- One example is **Programmable Logic Arrays (PLAs)**
- Designed so that can select (program) ands, ors, complements after you get the chip
 - Late in design process, fix errors, figure out what to do later, ...



Programmable Logic Arrays

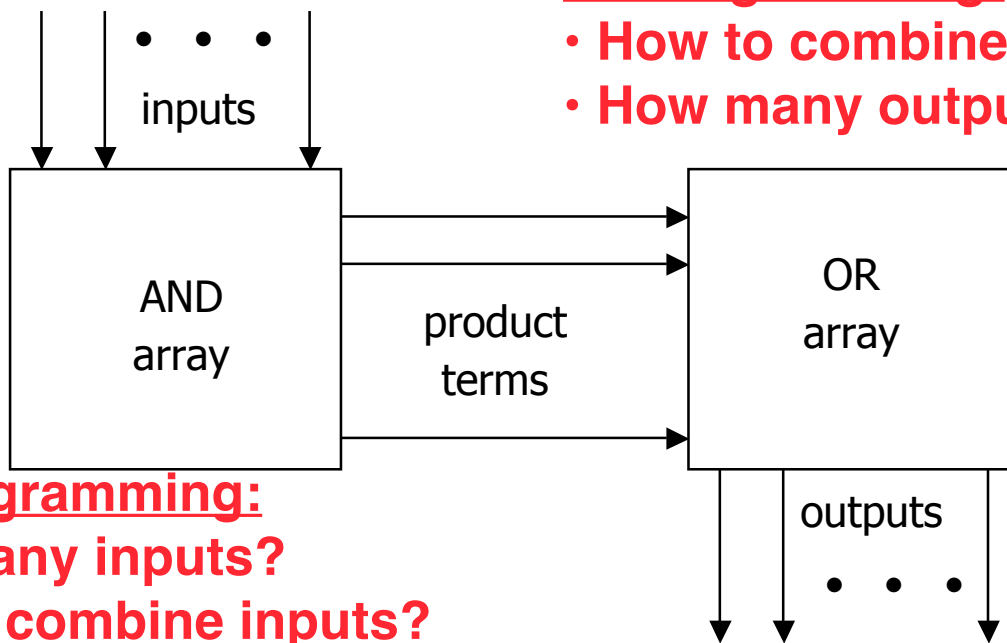- Pre-fabricated building block of many AND/OR gates
 - “Programmed” or “Personalized” by making or breaking connections among gates
 - Programmable array block diagram for sum of products form



Or Programming:

- How to combine product terms?
- How many outputs?

And Programming:

- How many inputs?
- How to combine inputs?
- How many product terms?



Enabling Concept

- Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

input side: 3 inputs

1 = uncomplemented in term
 0 = complemented in term
 - = does not participate

personality matrix

Product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

output side: 4 outputs


1 = term connected to output
 0 = no connection to output

reuse of terms;
 5 product terms




Before Programming

 - All possible connections available before “programming”



After Programming

 - Unwanted connections are "blown"
 - Fuse (normally connected, break unwanted ones)
 - Anti-fuse (normally disconnected, make wanted connections)





Alternate Representation

- Short-hand notation--don't have to draw all the wires
 - X Signifies a connection is present and perpendicular signal is an input to gate


notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

  

Peer Instruction

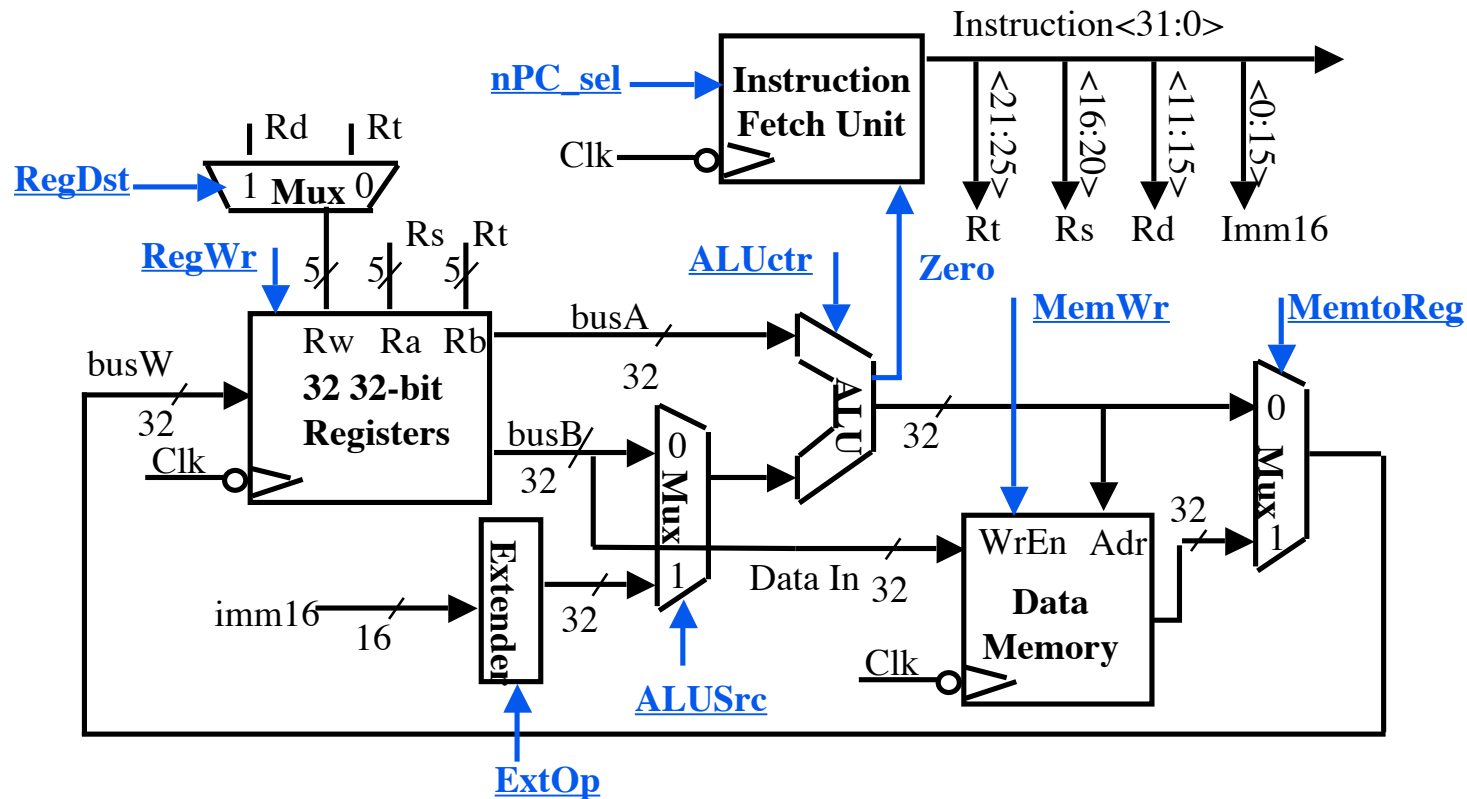

	ABC
1 :	SRF
2 :	SRT
3 :	SEF
4 :	SET
5 :	BRF
6 :	BRT
7 :	BEF
8 :	BET

- A. MemToReg='x' & ALUctr='sub'. **SUB** or **BEQ**?
- B. ALUctr='add'. Which 1 signal is different for all 3 of: ADD, LW, & SW? **RegDst** or **ExtOp**?
- C. "Don't Care" signals are useful because we can simplify our PLA personality matrix. **F** / **T**?



And in Conclusion... Single cycle control


◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

◦ **Control** is the hard part

◦ MIPS makes that easier

 - Instructions same size
- Source registers always in same place
- Immediates same size, location



Operations always on registers/immediates