

`inst.eecs.berkeley.edu/~cs61c/su05`

CS61C : Machine Structures

Lecture #15: Combinational Logic Blocks



2005-07-14

Andy Carle



CS 61C L15 Blocks (1)

A Carle, Summer 2005 © UCB


Outline

- **CL Blocks**
- **Latches & Flip Flops – A Closer Look**




Review (1/3)

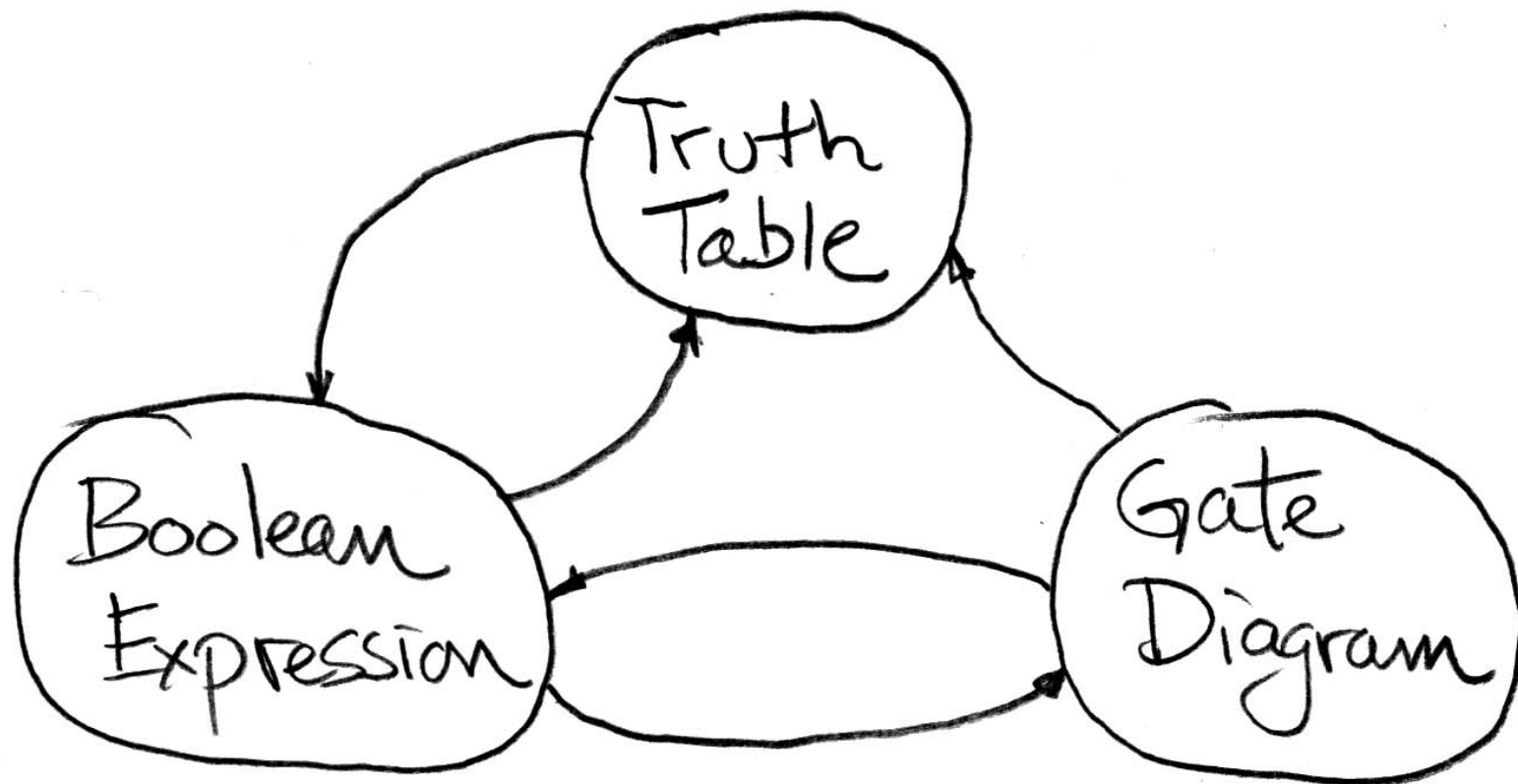- Use this table and techniques we learned to transform from 1 to another



 (2/3): Circuit & Algebraic Simplification




original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

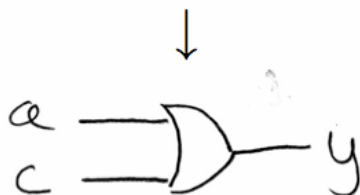

simplified circuit



(3/3):Laws of Boolean Algebra

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

complementarity
laws of 0's and 1's
identities
idempotent law
commutativity
associativity
distribution
uniting theorem
DeMorgan's Law




CL Blocks


- **Let's use our skills to build some CL blocks:**
 - **Multiplexer (mux)**
 - **Adder**
 - **ALU**



 Data Multiplexor (here 2-to-1, n-bit-wide)



N instances of 1-bit-wide mux

 


s	ab	c
0	00	0
0	01	0
0	10	1
0	11	1
1	00	0
1	01	1
1	10	0
1	11	1

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$




How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 


4-to-1 Multiplexor?

 

$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$

An Alternative Approach

 


Hierarchically!



Arithmetic and Logic Unit

 
- Most processors contain a logic block called “Arithmetic/Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR



when $S=00$, $R=A+B$
when $S=01$, $R=A-B$
when $S=10$, $R=A \text{ AND } B$
when $S=11$, $R=A \text{ OR } B$



Our simple ALU

 


Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer



N 1-bit adders \Rightarrow 1 N-bit adder

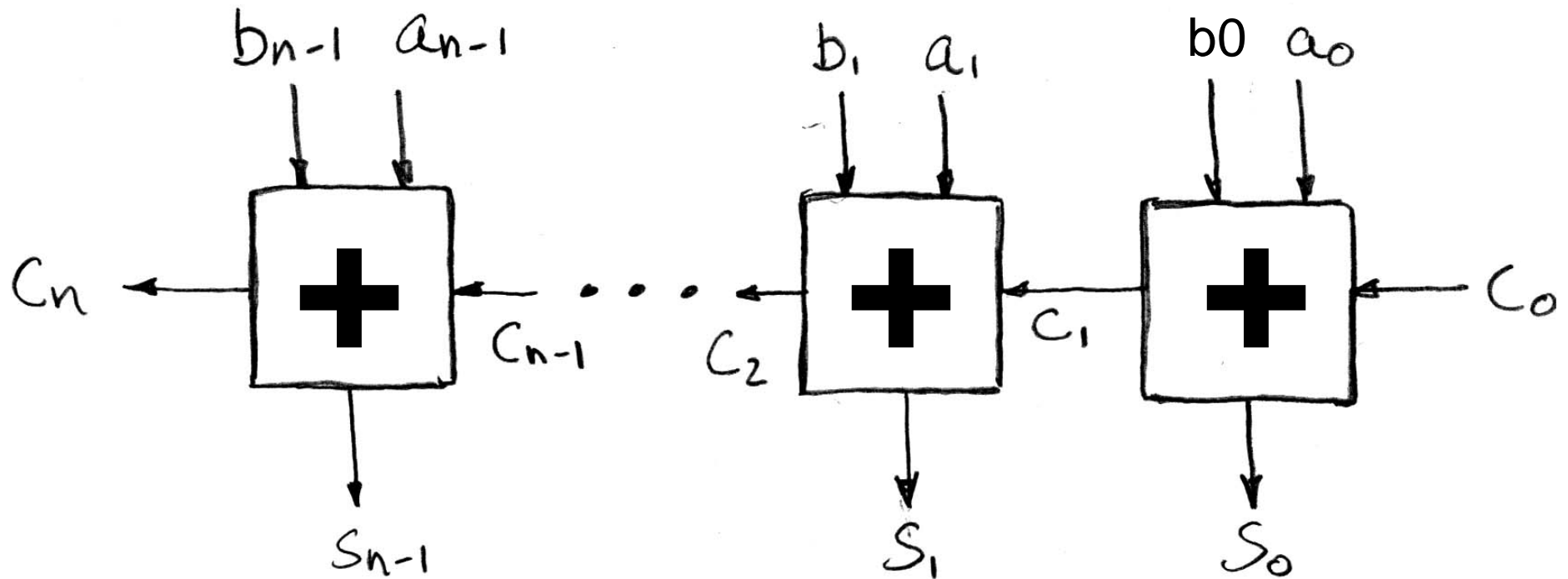

Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{cccc} & a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline s_3 & s_2 & s_1 & s_0 \end{array}$$

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



Adder/Subtractor – One-bit adder (1/2)...



$$\begin{array}{rcccc}
 & a_3 & a_2 & a_1 & a_0 \\
 + & b_3 & b_2 & b_1 & b_0 \\
 \hline
 s_3 & s_2 & s_1 & s_0 &
 \end{array}$$

a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 s_i &= \\
 c_{i+1} &=
 \end{aligned}$$



  Adder/Subtractor – One-bit adder (2/2)...




$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

What about overflow?

- Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



- Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow \text{NO overflow!}$

What
op?

- C_{in} , and $C_{out} \Rightarrow \text{NO overflow!}$

- C_{in} , but no $C_{out} \Rightarrow A, B \text{ both } > 0, \text{ overflow!}$


- C_{out} , but no $C_{in} \Rightarrow A, B \text{ both } < 0, \text{ overflow!}$



What about overflow?

- Consider a 2-bit signed # & overflow:

10 = -2
11 = -1
00 = 0
01 = 1

 


- Overflows when...

- C_{in} , but no $C_{out} \Rightarrow A, B$ both > 0 , overflow!
- C_{out} , but no $C_{in} \Rightarrow A, B$ both < 0 , overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$

Extremely Clever Subtractor

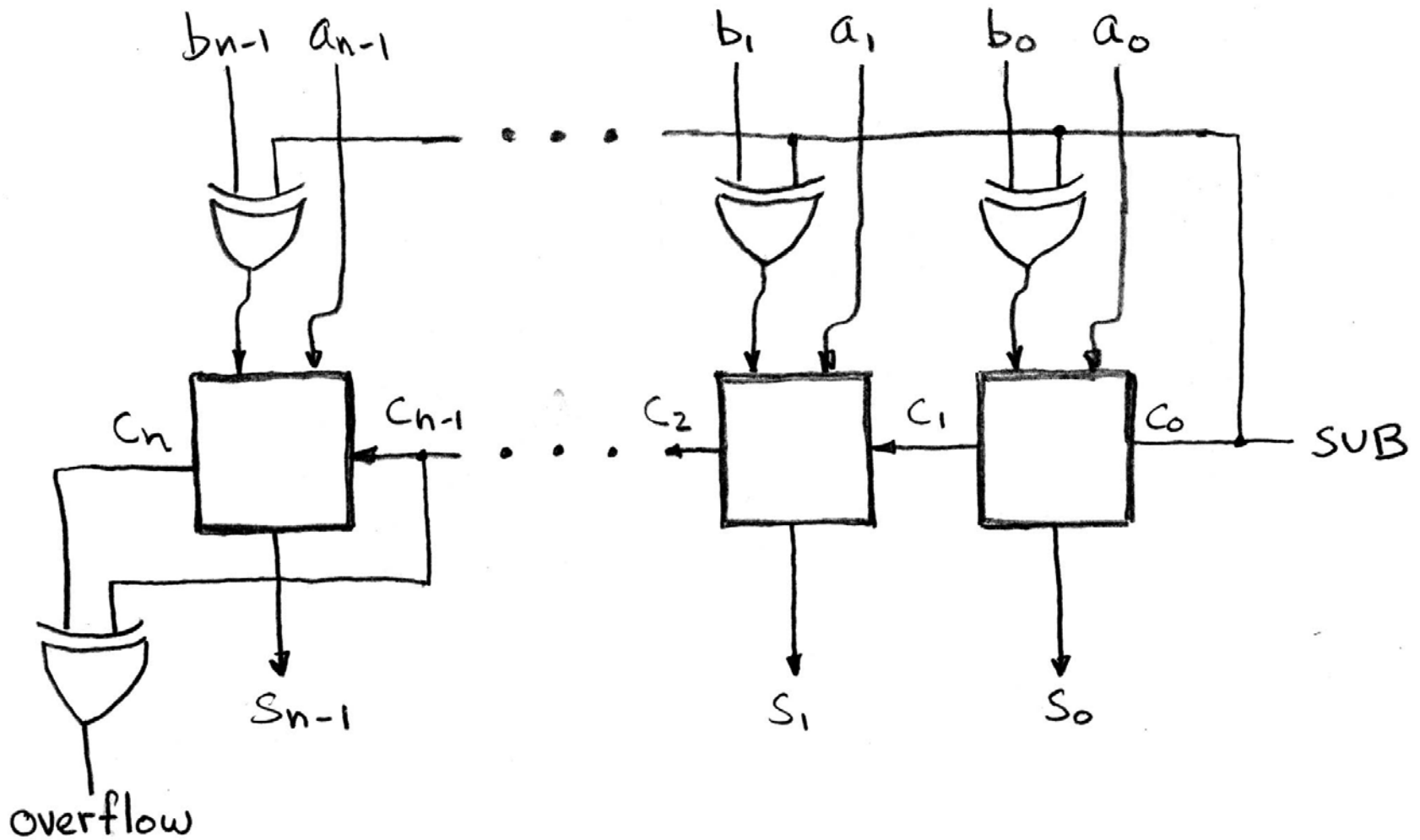

Administrivia


- **We're now halfway through the semester... yikes**
- **HW 45 Due Monday**
- **Proj2 coming...**

- **Logisim!**



State Circuits Overview

- State circuits have **feedback**, e.g.

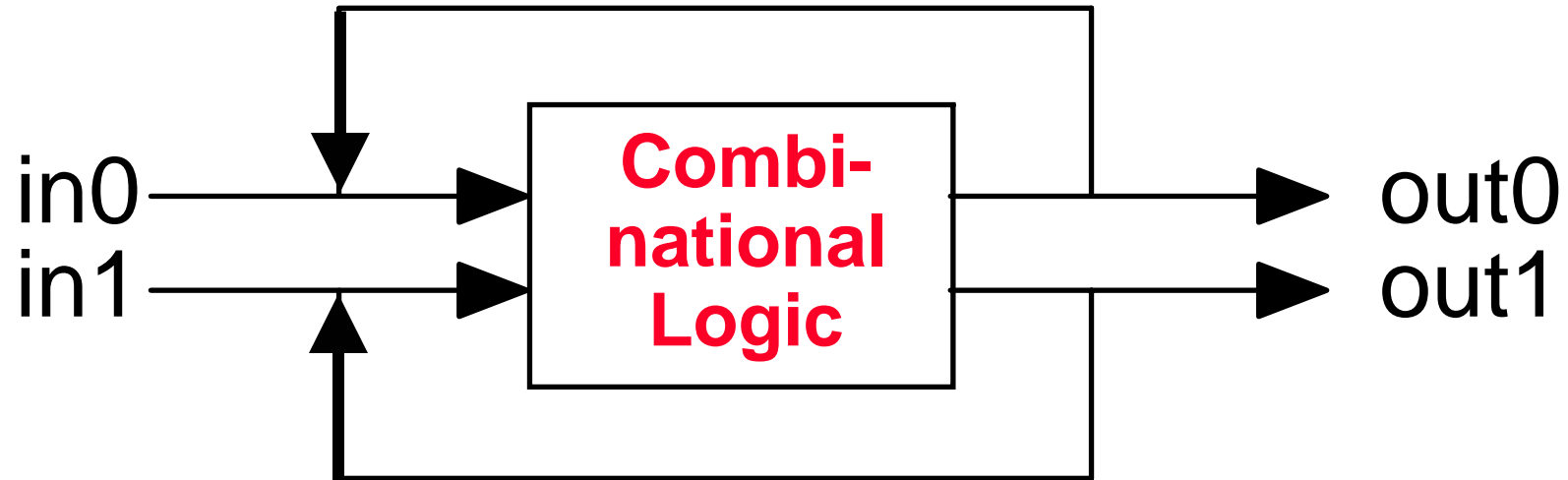


- Output is function of inputs + fed-back signals.
- Feedback signals are the circuit's **state**.
- What aspects of this circuit might cause complications?




An R-S latch (cross-coupled NOR gates)

- **S** means “set” (to 1),
R means “reset” (to 0).

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 

- Adding Q' gives standard RS-latch:

 


Truth table

S	R	Q
0	0	hold (keep value)
0	1	0
1	0	1
1	1	unstable



An R-S latch (in detail)

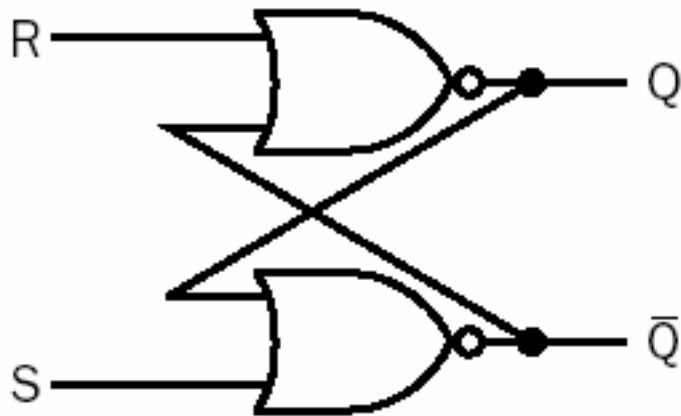

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Truth table

S	R	\bar{Q}	Q	Q (t+ Δt)	
0	0	0	1	0	hold
0	0	1	0	1	hold
0	1	0	1	0	reset
0	1	1	0	0	reset
1	0	0	1	1	set
1	0	1	0	1	set
1	1	0	x	x	unstable
1	1	1	x	x	unstable



Controlling R-S latch with a clock

- Can't change R and S while clock is active.


A B NOR

0 0 1

0 1 0

1 0 0

1 1 0

 


- Clocked latches are called *flip-flops*.



D flip-flop are what we really use



- Inputs C (clock) and D.
- When C is 1, latch open, output = D (even if it changes, “transparent latch”)
- When C is 0, latch closed, output = stored value.

C	D	AND
0	0	0
0	1	0
1	0	0
1	1	1

 


D flip-flop details

  - We don't like transparent latches
- We can build them so that the latch is only open for an instant, on the **rising edge of a clock** (as it goes from 0⇒1)



Timing Diagram

Edge Detection

 

- This is a “rising-edge D Flip-Flop”
 - When the CLK transitions from 0 to 1 (rising edge) ...
 - $Q \leftarrow D$; $Q_{\text{bar}} \leftarrow \text{not } D$
 - All other times: $Q \leftarrow Q$; $Q_{\text{bar}} \leftarrow Q_{\text{bar}}$

Peer Instruction

- A. Truth table for mux with 4 control signals has 2^4 rows**
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl**
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T**



“And In conclusion...”

- **Use muxes to select among input**
 - **S input bits selects 2^S inputs**
 - **Each input can be n-bits wide, indep of S**
- **Implement muxes hierarchically**
- **ALU can be implemented using a mux**
 - **Coupled with basic block elements**
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - **XOR serves as conditional inverter**

