 


CS61C : Machine Structures

Lecture #15: State 2 and Blocks



2006-07-24

Andy Carle




Outline

- Review
- Clocks
- FSMs
- Combinational Logic Blocks




Review (1/3)

 - Use this table and techniques we learned to transform from 1 to another



 (2/3): Circuit & Algebraic Simplification



original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$= ab + a + c$$

algebraic simplification

$$= a(b + 1) + c$$

$$= a(1) + c$$


$$= a + c$$

$$y = a + c$$

simplified circuit



Review (3/3)

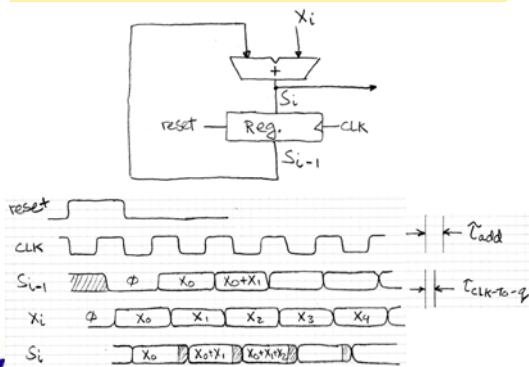

Clocks

- Need a regular oscillator:




- Wire up three inverters in feedback?...

- Not stable enough
- 1->0 and 0->1 transitions not symmetric.

- Solution: Base oscillation on a natural resonance. But of what?



Clocks

 


- Controller puts AC across crystal:
 - At anything but resonant freqs → destructive interference
 - Resonant freq → CONSTRUCTIVE!

Cal

CS 61C L15 State & Blocks (7)

A Carls, Summer 2006 © UCB

Signals and Waveforms: Clocks

 


Cal

CS 61C L15 State & Blocks (8)

A Carls, Summer 2006 © UCB

FSMs

 - With state elements, we can build circuits whose output is a function of inputs and current state.




- State transitions will occur on clock edges.

Cal

CS 61C L15 State & Blocks (9)

A Carls, Summer 2006 © UCB

Finite State Machines Introduction

 

Cal


CS 61C L15 State & Blocks (10)

A Carls, Summer 2006 © UCB

Finite State Machine Example: 3 ones...



Draw the FSM...

 


PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

Cal

CS 61C L15 State & Blocks (11)

A Carls, Summer 2006 © UCB

Hardware Implementation of FSM

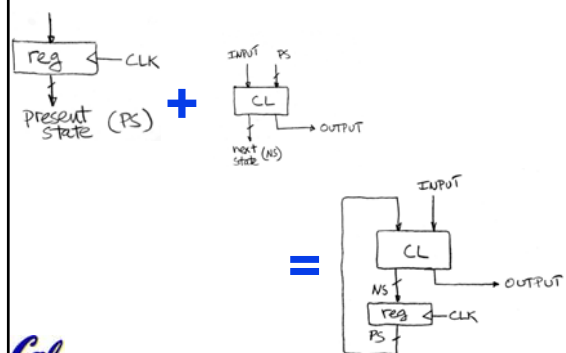


Cal

CS 61C L15 State & Blocks (12)

A Carls, Summer 2006 © UCB

General Model for Synchronous Systems

 

Cal

CS 61C L15 State & Blocks (13)

A Carlo, Summer 2006 © UCB

Peer Instruction 1

• Two bit counter:

- 4 States: 0, 1, 2, 3
- When input c is high, go to next state
 - (3->0)
- When input is low, don't change state
- On the transition from state 3 to state 0, output a 1. At all other times, output 0.

Cal

CS 61C L15 State & Blocks (14)

A Carlo, Summer 2006 © UCB

CL Blocks

• Let's use our skills to build some CL blocks:


- Multiplexer (mux)
- Adder
- ALU

Cal

CS 61C L15 State & Blocks (15)

A Carlo, Summer 2006 © UCB

 Data Multiplexor (here 2-to-1, n-bit-wide)




Cal

CS 61C L15 State & Blocks (16)

A Carlo, Summer 2006 © UCB

N instances of 1-bit-wide mux

 

s	ab	c
0	00	0
0	01	0
0	10	1
0	11	1
1	00	0
1	01	1
1	10	0
1	11	1


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

Cal

CS 61C L15 State & Blocks (17)

A Carlo, Summer 2006 © UCB

How do we build a 1-bit-wide mux?

 

Cal

CS 61C L15 State & Blocks (18)

A Carlo, Summer 2006 © UCB

4-to-1 Multiplexor?

$e = \overline{s_1} \overline{s_0} a + \overline{s_1} s_0 b + s_1 \overline{s_0} c + s_1 s_0 d$

CS 61C L15 State & Blocks (19) A Carlo, Summer 2006 © UC Berkeley

An Alternative Approach

Hierarchically!

CS 61C L15 State & Blocks (20) A Carlo, Summer 2006 © UC Berkeley

Arithmetic and Logic Unit

- Most processors contain a logic block called "Arithmetic/Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR

when $S=00$, $R=A+B$
 when $S=01$, $R=A-B$
 when $S=10$, $R=A \text{ AND } B$
 when $S=11$, $R=A \text{ OR } B$

CS 61C L15 State & Blocks (21) A Carlo, Summer 2006 © UC Berkeley

Our simple ALU

CS 61C L15 State & Blocks (22) A Carlo, Summer 2006 © UC Berkeley

Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

CS 61C L15 State & Blocks (23) A Carlo, Summer 2006 © UC Berkeley

N 1-bit adders \Rightarrow 1 N-bit adder

CS 61C L15 State & Blocks (24) A Carlo, Summer 2006 © UC Berkeley

Adder/Subtractor – One-bit adder LSB...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



Adder/Subtractor – One-bit adder (1/2)...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0


a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$



 Adder/Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$


$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$



What about overflow?

Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What op?


- C_{in} , and $C_{out} \Rightarrow$ NO overflow!
- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!



What about overflow?

Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

 


Overflows when...

- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$



Extremely Clever Subtractor

 

Peer Instruction

- A. Truth table for mux with 4 control signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for srl, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T




"And In conclusion..."

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter



State Circuits Overview (Extra Slides)


- State circuits have **feedback**, e.g.

 


- Output is function of inputs + fed-back signals.
- Feedback signals are the circuit's **state**.
- What aspects of this circuit might cause complications?



A simpler state circuit: two inverters

 

 - When started up, it's **internally stable**.
- Provide an **or gate** for coordination:




- What's the result? **How do we set to 0?**




An R-S latch (cross-coupled NOR gates)

 - S means "set" (to 1),
- R means "reset" (to 0).



A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0


- Adding Q' gives standard RS-latch:

 

S	R	Q
0	0	hold (keep value)
0	1	0
1	0	1
1	1	unstable



An R-S latch (in detail)

 

Truth table


S	R	Q	Q'	Q(t+Δt)
0	0	1	0	hold
0	0	0	1	hold
0	1	0	1	reset
0	1	1	0	reset
1	0	0	1	set
1	0	1	0	set
1	1	x	x	unstable
1	1	x	x	unstable

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0



Controlling R-S latch with a clock

 - Can't change R and S while clock is active.



- Clocked latches are called *flip-flops*.


Cal

CS 61C L15 State & Blocks (07)

A Carls, Summer 2006 © UCB

D flip-flop are what we really use

 - Inputs C (clock) and D.
- When C is 1, latch open, output = D (even if it changes, "transparent latch")
- When C is 0, latch closed, output = stored value.




Cal

CS 61C L15 State & Blocks (08)

A Carls, Summer 2006 © UCB

D flip-flop details

 - We don't like transparent latches
- We can build them so that the latch is only open for an instant, on the **rising edge of a clock** (as it goes from 0 \Rightarrow 1)




Cal

CS 61C L15 State & Blocks (09)

A Carls, Summer 2006 © UCB

Edge Detection

 

- This is a "rising-edge D Flip-Flop"

- When the CLK transitions from 0 to 1 (rising edge) ...
 - $Q \leftarrow D$; $Qbar \leftarrow \text{not } D$
- All other times: $Q \leftarrow Q$; $Qbar \leftarrow Qbar$

Cal

CS 61C L15 State & Blocks (40)

A Carls, Summer 2006 © UCB